

**Elektor  
Electronics**




02


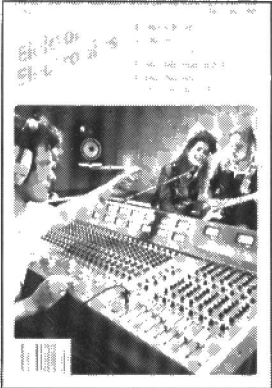
## Theme of the month in March will be Components

Also in the March issue:

- Sinewave inverter
- Bucket brigade memories
- Surge plug
- Pause switch for cam-corders
- Low-cost V/I display module
- SAVE decoder: Part 2
- Temperature compensation for LCD modules



### Front cover

New singers and musicians, like Kathy and Ian shown here, can now set up their own home recording studio, using the 16-track console developed by Remix to professional standards but at a non-professional price.

The Remix has proved attractive not only to bands, composers and song-writers who want to mix and record at home, but also to smaller, mid-priced commercial music and film studios.

Features include: 6 auxiliary sends, separate tape inputs, peak and status LEDs, +4 dB to -10 dB selectable, 8 bus with 16-track monitoring, 8 effects returns, 100 mm smooth action faders, direct outputs on all channels, send and return patch points throughout, and monitoring with equalization.

## LEADER

- 11 Launch of the digital communications era

## AUDIO & HI-FI

- 23 Calsod now even more versatile  
A review  
34 **PROJECT:** Feedback killer  
by T. Giffard

## AUTOMOTIVE ELECTRONICS

- 22 **PROJECT:** Car theft deterrent  
by David Butler

## COMPONENTS

- 24 Introducing the OP-series opamps  
by J. Ruffell  
44 AC-DC current sensors

## COMPUTERS & MICROPROCESSORS

- 14 **PROJECT:** Initialization aid for printers  
by A. Rigby

## DESIGN IDEAS

- 32 Waveform modulation of the mains voltage  
by A.M. Karailiev

## GENERAL INTEREST

- 53 **PROJECT:** The digital model train - Part 11  
by T. Wigmore  
62 **PROJECT:** Dark-room clock  
by A. Rigby

## INTERMEDIATE PROJECT

- 57 Part 8: Reflex MW AM receiver  
by J. Bareford

## RADIO & TELEVISION

- 27 **PROJECT:** SAVE decoder - Part 1  
by P.N.P. Wintergreen  
38 **PROJECT:** PC Radio  
an ELV design  
47 **PROJECT:** Video mixer - Part 2  
by A. Rigby

## TEST & MEASUREMENT


- 18 **PROJECT:** Capacitance meter  
by D. Folger

## MISCELLANEOUS INFORMATION


News 12 & 13; New books 46; Events 51; Corrections 59;  
Readers' Forum (letters & switchboard) 60; Readers services 67  
Buyers guide 74; Classified ads 74; Index of advertisers 74
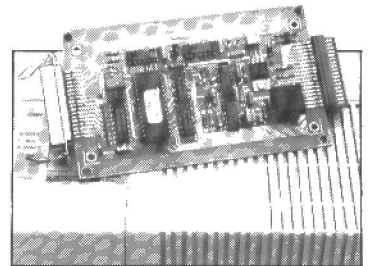
## CORRECTION


In the description of the photograph on the front cover of the December 1989 issue of *Elektor Electronics*, we stated that the 4.5 m dia. antenna had won a 1989 Queen's Award for Technological Achievement. This was based on wrong information. In fact, Precision Metal Ltd, the designers and manufacturers of the antenna, received a 1989 Queen's Award for Export Achievement.



Initialization aid for printers  
p. 14

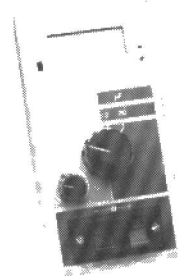

Capacitance meter, p. 18

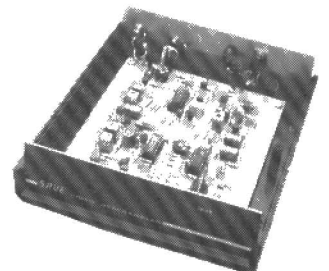

SAVE decoder, p. 27



# LAUNCH OF THE DIGITAL COMMUNICATIONS ERA

**Editor/publisher:** Len Seymour  
**Technical Editor:** J. Buiting  
**Editorial Offices:**  
 Down House  
 Broomhill Road  
 LONDON SW18 4JQ  
 England  
**Telephone:** 01-877 1688 (*National*)  
 or +44 1877 1688 (*International*)  
**Telex:** 917003 (LPC G)  
**Fax:** 01-874 9153 (*National*)  
 or +44 1874 9153 (*International*)  
**Advertising:** PRB Limited  
 3 Wolseley Terrace  
 CHELTENHAM GL50 1TH  
**Telephone:** (0242) 510760  
**Fax:** (0242) 226626  
**European Offices:**  
**Postbus 75**  
**6190 AB BEEK**  
**The Netherlands**  
**Telephone:** +31 4490 89444  
**Telex:** 56617 (elekt nl)  
**Fax:** +31 4490 70161  
**Managing Director:** M.M.J. Landman

## Overseas editions:

### FEDERAL GERMANY

Elektor Verlag GmbH  
 Süsterfeld Straße 25  
 5100 Aachen

**Editor:** E.J.A. Krempelsauer

### FRANCE

Elektor sarl  
 Route Nationale; Le Seau  
 B.P. 53; 59270 Bailleul

**Editors:** D.R.S. Meyer

G.C.P. Raedersdorf

### GREECE

Elektor EPE  
 Kariskaki 14  
 16673 Voula - Athena

**Editor:** E. Xanthoulis

### INDIA

Elektor Electronics PVT Ltd  
 Chhotani Building  
 52C, Proctor Road, Grant Road (E)  
 Bombay 400 007

**Editor:** Surendra Iyer

### NETHERLANDS

Elektuur BV  
 Peter Treckpoelstraat 2-4  
 6191 VK Beek

**Editor:** P.E.L. Kersemakers

### PAKISTAN

Electro-shop  
 35 Naseem Plaza  
 Lasbella Chawk

Karachi 5

**Editor:** Zain Ahmed

### PORTUGAL

Ferreira & Bento Lda.  
 R.D. Estefani, 32-1°  
 1000 Lisboa

**Editor:** Jeremias Sequeira

### SPAIN

Ingelek S.A.  
 Plaza República Ecuador  
 2-28016 Madrid

### SWEDEN

Electronic Press AB  
 Box 5505  
 14105 Huddinge

**Editor:** Bill Cedrum

## Distribution:

SEYMOUR  
 1270 London Road  
 LONDON SW16 4DH

Written and composed on Apple and  
 IBM corporate publishing systems by  
 Elektor Electronics (Publishing)

Printed in the Netherlands by NDB,  
 Zoeterwoude

Copyright © 1990 Elektuur BV

**ABC**

MEMBER OF THE AUDIT  
 BUREAU OF CIRCULATIONS

Plans for the digital communications era of the future – paving the way for even more high-tech applications, such as the picture phone, ultra-fast fax and high speed data transfer – have been unveiled by British Telecom. The company has launched a new advanced service to carry voice, data and pictures, called British Telecom ISDN2.

The new service—the first ISDN service in the world to conform to the latest international standards now being adopted worldwide—could become, by the mid 1990s, the standard exchange line service for all customers who want two or more connexions. It enables a broad spectrum of British Telecom customers to take advantage of information technology (IT) services previously available only to large businesses. In so doing, it will accelerate the introduction of the information society.

ISDN2 will provide high-speed digital services to branch offices of large companies as well as to small and medium businesses. Such services have until recently been available only to large business sites. ISDN2 started as a test market at the end of last November and will become a fully public commercial service from the end of April.

The launch of ISDN2 follows a £23 million order with STC Telecommunications for equipment to provide up to 90 000 lines of network-capacity. This is equivalent to 180 000 ordinary phone connexions.

The new service allows British Telecom's public network to meet customers' communication needs for data, text, fax, graphics, and video over a single high-speed digital connexion. It combines the power of advanced private networks with the simplicity and universality of the ordinary telephone.

ISDN2 provides customers with two high-speed digital exchange connexions on one pair of wires. Customers can use the new service to make national and international phone calls in the ordinary way and at the same cost. In addition, they are able to make data, video and other digital services calls within the UK, and to France, Japan and the USA. More international links are planned.

ISDN2 offers many benefits over existing services, including:

- even better quality basic telephone service with faster call set-up, clearer speech, and fewer data transmission errors;
- greater flexibility and efficiency, allowing customers to use their lines for data and speech at will;
- lower cost data calls because of higher speed operation;
- identification of callers on incoming calls and of called lines on outgoing calls on digital end-to-end connexions;
- setting up of wide-area quasi private networks over the public network;
- support for true integrated-services worksta-

tions combining voice and data to achieve improved communications;

- longer term lower cost for ordinary telephone connexions because ISDN2 should eventually prove cheaper than two separate lines.

It is expected that call charges for inland calls will follow the principle adopted by British Telecom for its other ISDN services: the cost of high-speed data and voice calls over digital links will be the same as inland telephone calls over ordinary lines.

Connexion and rental charges have not yet been announced. Initially, they will be at a premium compared to charges for ordinary analogue exchange lines, but because call charges form the larger part of most business customers' phone costs, the benefits of ISDN2 will be available for no more than a small increase in users' bills.

The initial network capacity of up to 90 000 digital connexions will be rolled out over 18 months. This will enable British Telecom to offer an ISDN2 service from all its System X digital exchanges—currently totalling more than 2000—by the end of next year. This will cover all business centres and recognized high streets in the United Kingdom. Service will also be made available in the near future on British Telecom's AXE 10 exchanges.

British Telecom has been working closely with industry to encourage development of terminals that customers can connect to ISDN2. These are expected to become available from a number of suppliers at about this time. Initially, they are likely to be the normal industry-standard personal computers found in offices today, but equipped with ISDN communication cards for data/voice conferencing, file transfer and distributed processing. They will still be able to perform word processing and other office IT applications, as well as operating as ISDN terminals. Later, integrated key systems and small private branch exchanges are expected to be introduced.

ISDN2 will be able to carry many of the applications now being run on private long-distance networks and local area networks. These could include EPOS (electronic data transfer at the point of sale), mortgage and insurance quotations, and retrieval of the financial and commercial data many businesses use for their day-to-day activities.

In the next few years even more imaginative applications should appear, such as the view-phone, high-speed fax, and the transfer of coloured maps and diagrams originating from optical disc stores. Such applications would be especially useful to small-to-medium businesses and branch offices: firms such as estate agents, advertising agents, designers, and other graphics arts companies, publishers and consumer goods suppliers.



## NEWS

### SWITCH OF EUTELSAT SERVICES

EUTELSAT, the European Telecommunications Satellite Organization, has switched some services from EUTELSAT I-F1 at 16° E to EUTELSAT I-F2 at 7° E and vice versa. Transferred from F1 are full-time leases while in return telephony, European Broadcasting Union (EBU) transmissions and some occasional-use traffic is transferred from F2 to F1.

The changes are carried out to guarantee complete continuity of all services on EUTELSAT satellites. EUTELSAT I-F1 is now entering inclined orbit after almost seven operational years. All telephony and most EBU traffic can be carried by a satellite in inclined orbit since transmission and reception are conducted via gateway earth stations that track satellites in space with great precision.


### THE ATV COMPENDIUM

The British Amateur Television Club has recently published the latest issue of its magazine CQ - TV. This includes as usual a varied and interesting selection of articles, ranging from general topics such as "Using oscilloscopes" by Mike Wooding, G6IQM, and "Broadcast band DX-TV reception" by Gary Smith and Keith Hamer to more technical articles such as "Camera tubes explained" by Peter Delaney, G8KZG. CQ - TV is a must for all those who are interested in this stimulating branch of amateur radio. You can obtain this issue and much more by joining the British Amateur Television Club. For details write (enclosing a SAE) to Mr D. Lawton, "Grenehurst", Pinewood Road, High Wycombe HP12 4DD.

### NEW SWITCHMODE ICS

Siliconix has introduced two new switchmode power-control ICs, the Si9112 and Si9120, which include the first device capable of operating in 'universal-input' power supplies from either 110 V or 220 V AC power lines.

The new devices allow the design of

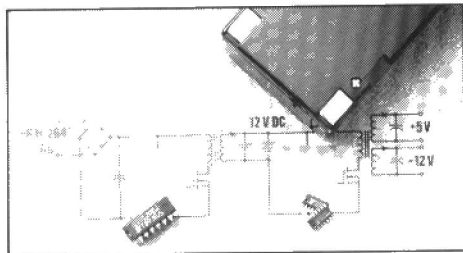

highly efficient (greater than 80%) power converters with fewer components than other semiconductor solutions, so that designers can improve system performance

while reducing board space and component costs.

### CUSTOMER REVOLUTION IN TELECOMMUNICATIONS

British Telecom has implemented one of the world's most challenging computer projects to transform its services to customers.



The project, known as Customer Service Systems, draws together all the main elements of the customer services British Telecom provides. All 23 million customers of British Telecom are now able to benefit from its advantages.

Basically, it is state-of-the-art information technology in action, ensuring that customers get the best possible response to their needs.

### FIRST COMPUTER MUSIC LEARNING CENTRE IN THE UK

Equipped with a wide range of the latest MIDI instruments, video and computers, EMR's Computer Music Learning Centre (CMLC) is based in Southend, Essex, and offers a unique opportunity to gain first-hand experience of using EMR's extensive music software and hardware.

The CMLC will initially provide one-day courses for beginners and more experienced users during holiday periods and at weekends, as well as training for teachers and dealers.

The centre has been in the pipeline for two years, with EMR providing more and more seminars to education and user groups in the UK and Europe, particularly on the Archimedes, although they have produced systems for the Spectrum, Commodore, Amstrad, MSX and BBC Micro since the company started in 1983.

The courses are under the direction of Mike Beecher, LRAM, GRSM, whose music

demonstrations at exhibitions will be well known to many of our readers. His past experience as director of a large Essex music school and first London synthesizer school, creator of *Electronics & Music Maker* (now *Music Technology*) and *Home Studio Recording* magazines and frequent lecturer in Europe should make your day a worthwhile event—he has also designed the software you'll be using with his team of programmers, so you'll be finding out new ways of making music with your computer.

Full details from EMR CMLC, Suite 1-3, 50 Hamlet Court Road, WESTCLIFF-ON-SEA SS0 7LX, Telephone (0702) 335747.

### US TAKE-OVER BOOSTS RACAL'S CAE PRESENCE

Britain's Racal Electronics Group, already dominant in computer-aided design (CAD) systems for printed-circuit boards, has strengthened its presence in computer-aided engineering (CAE) with a £12 million take-over of the American HHB Systems simulation software company.

HHB Systems, based in Mahwah, New Jersey, was set up in 1977 to develop and sell high-performance logic and fault simulation software for use in the design and test of complex electronic circuits. Since then, the company has gained over 200 customers worldwide with sales worth \$12 million a year and its products have become established as industry standards.

The two companies have a working relationship dating back to 1984, and HHB's products are already fully integrated within Racal-Redac's workstation-based electronic design automation (EDA) system, Visula Plus. At present, the combination of Visula Plus and CADAT is the only proven and commercially available system that can design and simulate application specific integrated circuits (ASICs) in the context of their target systems.

### POWERFUL WEAPON AGAINST CANCER

A new computer developed by the Active Memory Technology (AMT) company of Reading is contributing to what has been described as one of the greatest scientific adventures in human history: to map and identify all human genes.

The aim of the project is to decipher the complete set of biological instructions used by nature to make a human being. The resulting "Book of man" may provide the basis for preventing or treating most human diseases in the next century. Its target completion date is the year 2000.

The human genome consists of chemical beads twisted into the famous double helix of the deoxyribonucleic acid (DNA) molecule. There are four types of bead,






known scientifically as bases. They are the four chemical letters of the genetic code (A, G, T and C) discovered by James Watson and Francis Crick at Cambridge University in 1953. Watson is one of the leaders of the human genome project in the United States.
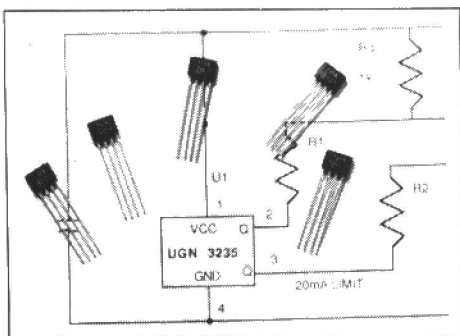
### DUAL-OUTPUT HALL EFFECT SWITCHES

Industry's first family of dual-output Hall effect switches with outputs that are independently activated by magnetic fields of opposite polarity is available from the Sprague Semiconductor Group.



The UGN3235K and UGS3235K Hall effect sensors are bipolar ICs designed for commutation of brushless DC motors and other applications that use multi-pole ring magnets in industrial and automotive environments.

### MORE HEADACHES FOR IBM

Shortly after the news that IBM's trade figures were "disappointing" and that the company was consequently laying off 10 000 employees, it was announced that the US Navy is to impose an indefinite ban on doing business with IBM.

The Navy decided on the ban after it had come to light during a House Government Operation Committee hearing that IBM had defrauded the US Navy by selling it used computer equipment as new.

As if that was not enough, a group of clone makers\* have defined their EISA 32 bit bus standard, which is compatible with the ISA—Industry Standard Architecture—system. IBM had hoped to keep the clone makers out of the 32-bit market by keeping their 32-bit (with data path) standard—Microchannel Architecture,

MCA—to itself. It seems, however, that IBM has seriously underestimated the strength of the clone makers.

\*AST Research, Compaq, Epson, Hewlett-Packard, NEC, Olivetti, Tandy, Wise, Zenith.

### SATELLITE ACCESS SYSTEM TO BEAT TV PIRATES

A new British Telecom satellite management system will allow broadcasters to keep track of their customers and avoid piracy of TV entertainment services. It can also prevent pictures being received in specified areas.


The BT Vision system uses transmission and encryption technology to ensure that only authorized subscribers can receive satellite TV programming, and offers programme providers the technology to control transmission of potentially offensive satellite broadcast material.

The system effectively prevents piracy by securely encrypting the programme signal with the aid of a complex algorithm before it is uplinked to the satellite. A stream of authorization messages is sent out along with the television pictures, authorizing subscribers' set-top decoders to accept the programming signal.

A very useful feature of the system is its ability to black out pictures in specific locations. This means that TV broadcasts will not be received in countries where the distribution rights have not been agreed or where the broadcasting control body considers their content unacceptable (so much for those who thought that the age of censorship was over!).
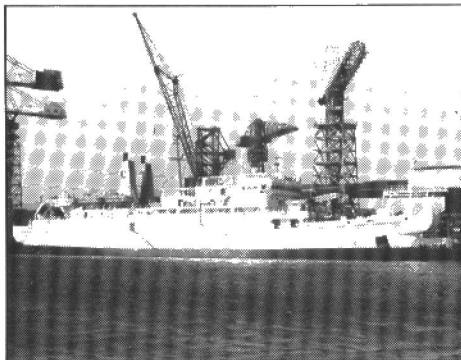
### NEW SUPPORT SHIP FOR TRANSATLANTIC CABLE

Cable & Wireless Marine's new cable ship, the *Sir Eric Sharp*, is said to be the most technically advanced vessel of its kind in the world. It has to be, because it is designed to service and maintain the world's first private trans-ocean fibre optic link between Britain and the United States. This is the PTAT-1 system, part of Cable & Wireless Marine's global digital high-




way linking the major financial centres of the world. The vessel will also be used to maintain existing analogue coaxial cables.

To enable the vessel to pick up and lay cable in the most efficient manner, it is the first of its type to be equipped permanently with a submersible remotely operated vehicle (ROV).
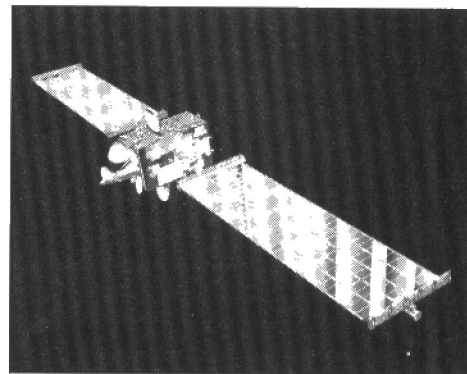
### EARTH STATION FOR OLYMPUS LINK

One of the two £750,000 mobile earth stations designed and built by British Aerospace under contract to the European Space Agency has been handed over to one of Britain's leading academic institutions for communications technology and educational broadcasting, Polytechnic South West in Plymouth.



The station, known as TDS 4, will be used for demonstration purposes. It will enable the polytechnic to communicate via Olympus, the world's most powerful civil communications satellite, which was also built by British Aerospace.

The TDS 4 earth station is mounted on a 12-metre long articulated trailer and incorporates its own auxiliary diesel generator. In operation, it will transmit in the 13.00–13.25 GHz and the 14.00–14.30 GHz bands, and receive signals in the 12.50–12.75 GHz band. The antenna fitted is a 3.5 metre design with hinged sides that can be folded down for ease of transport.

### EEC MEASURES TO LIMIT ADVERTISING ON TELEVISION

Britain is supporting the proposed EEC measures to limit the amount of advertising on TV and the number of American programmes shown. The new measures were agreed at a recent meeting of EEC foreign ministers.

Under the new rules, no advertisement will be allowed during news, religious or children's programmes under half an hour long. Advertisements will be allowed during films after the first 45 minutes.

The decision is unlikely to have much effect in the UK where standards are among the strictest in Europe. ■



# INITIALIZATION AID FOR PRINTERS

A. Rigby

**Many computer users have difficulty in changing printer settings without the help of a manual or handbook. The circuit presented here allows one of sixteen pre-programmed printer settings to be called up at the flick of a switch. Very useful for a good many computer programs that lack a real printer driver, the initialization aid is a low-cost and simple-to-build circuit.**

You are working hard on a BASIC program which is almost finished, and hard copy on paper is required to do the final debugging. Since the program is fairly long, you think it wise to set the printer to condensed characters at 8 lines per inch. The printer manual is consulted and the following command is typed in the direct command mode of GWBASIC:

```
LPRINT CHR$(15);CHR$(27);"0";
```

We think you will agree that pushing a small button on the printer initialization aid is a lot easier than having to look up eight or so ASCII characters, and typing them into the computer whilst observing the correct order, brackets and delimiters.

In the above example, BASIC fortunately allows the printer to be set to the required mode, albeit in a rather complex way prone to many errors. There are, however, many programs that lack even the most rudimentary means to set the printer to a particular character or paper format. For such programs, the initialization aid is a useful peripheral, provided its setting is not overridden by a printer initialization string prefixed to each printable file by the program in question.

## Basic operation

The flowchart in Fig. 1 illustrates the basic operation of the circuit, which is inserted between the computer's Centronics port and the parallel input of the printer. The diagram shows the functional blocks in the circuit as well as the interrelated timing at which these blocks operate.

At power-on, the circuit is reset and forms a straight 36-way connection between the computer's Centronics port and the Centronics input on the printer. No change is made to the previously established printer setting, and the computer can send printer files as before.

When S<sub>2</sub> is pressed, data buffer ICs block the datastream from the computer. The circuit actuates the BUSY line to force the computer to stop sending data. Meanwhile, the data outputs of the EPROM, IC<sub>7</sub>, are enabled, so that the byte at the currently addressed location in the EPROM is sent to the printer. A strobe pulse is generated to signal to the printer that a byte is held ready for transmission. Since the start of the first strobe pulse coincides with the moment the EPROM datalines are enabled, the strobe pulse is delayed by about one microsecond to en-

sure stable levels on the datalines. After the STROBE output line is actuated, the circuit enters a wait loop to allow the printer to process the databyte. Depending on the position of jumper JP<sub>1</sub>, the circuit waits for a negative pulse transition on the BUSY or  $\overline{\text{ACK}}$  handshaking line from the printer. When the transition arrives, the EPROM address counter is incremented by one. The counter starts at the lowest address, nil, by virtue of the power-on reset, and the fact that the circuit stops automatically when the counter reaches nil. In the latter case, the "all 16 bytes sent?" loop in the flowchart is left via the "yes" exit, and the circuit forms a straight connection between the computer and the printer until S<sub>2</sub> is pressed again.


All 16 bytes stored in the EPROM are to the printer under the control of strobe pulses, which are started with the aid of the delayed BUSY or  $\overline{\text{ACK}}$  printer signal. The delay allows some time for the address counter to reach the next higher output state. When all bytes have been sent, the same delay is used to reset the circuit to its start configuration.

## 16x16 in control

A part of the circuit drawn in Fig. 2 consist of a set of printed-circuit board tracks called the control bus. This bus takes all Centronics control signals not used by the initialization aid from the input- to the output connector. Two lines, C18 and C35, form an exception, because they may be used to power the circuit. Whether or not they can be used for this purpose depends on the printer used. Diodes D<sub>2</sub>, D<sub>3</sub> and D<sub>4</sub> form an OR function that allows the circuit to be powered by different supplies. In case the printer lacks a +5 V output on its Centronics connector, the circuit is powered by a 9 VDC mains adapter via D<sub>2</sub> and voltage regulator IC<sub>9</sub>. If the printer supplies +5 V via line C18, the circuit is powered via D<sub>3</sub>. If +5 V is available on line C35, D<sub>4</sub> is used for the same purpose. The current consumption of the circuit does not exceed 50 mA.

As already discussed, the circuit is reset automatically the moment the supply voltage is present. Bistable FF<sub>2</sub> is reset by R<sub>9</sub>-C<sub>2</sub>, and in turn clears address counter IC<sub>5</sub>. Bistable FF<sub>1</sub> is configured as

ELEKTOR ELECTRONICS FEBRUARY 1990

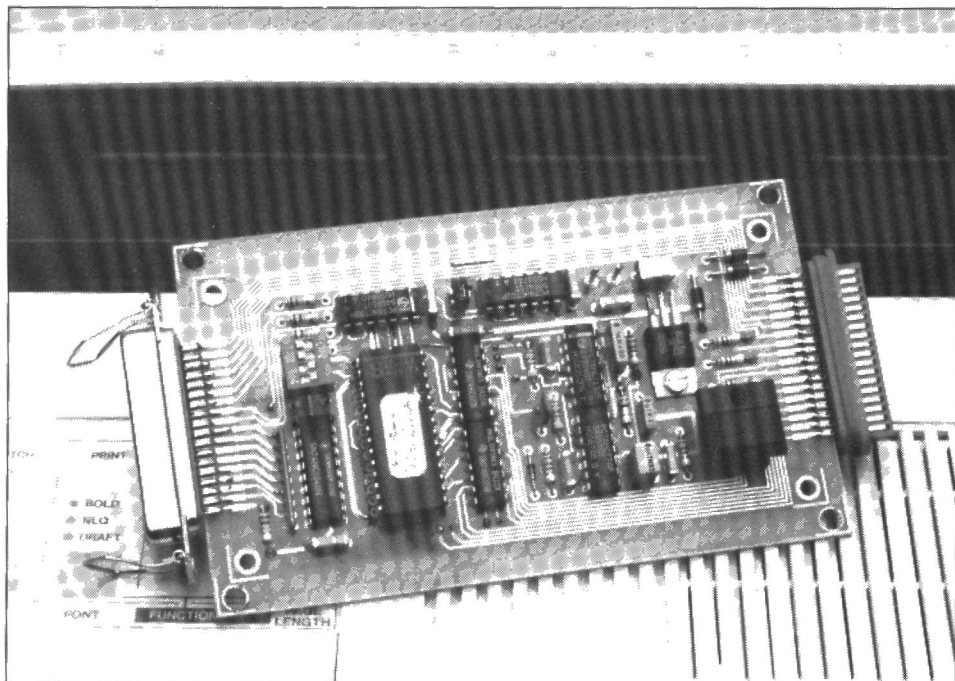



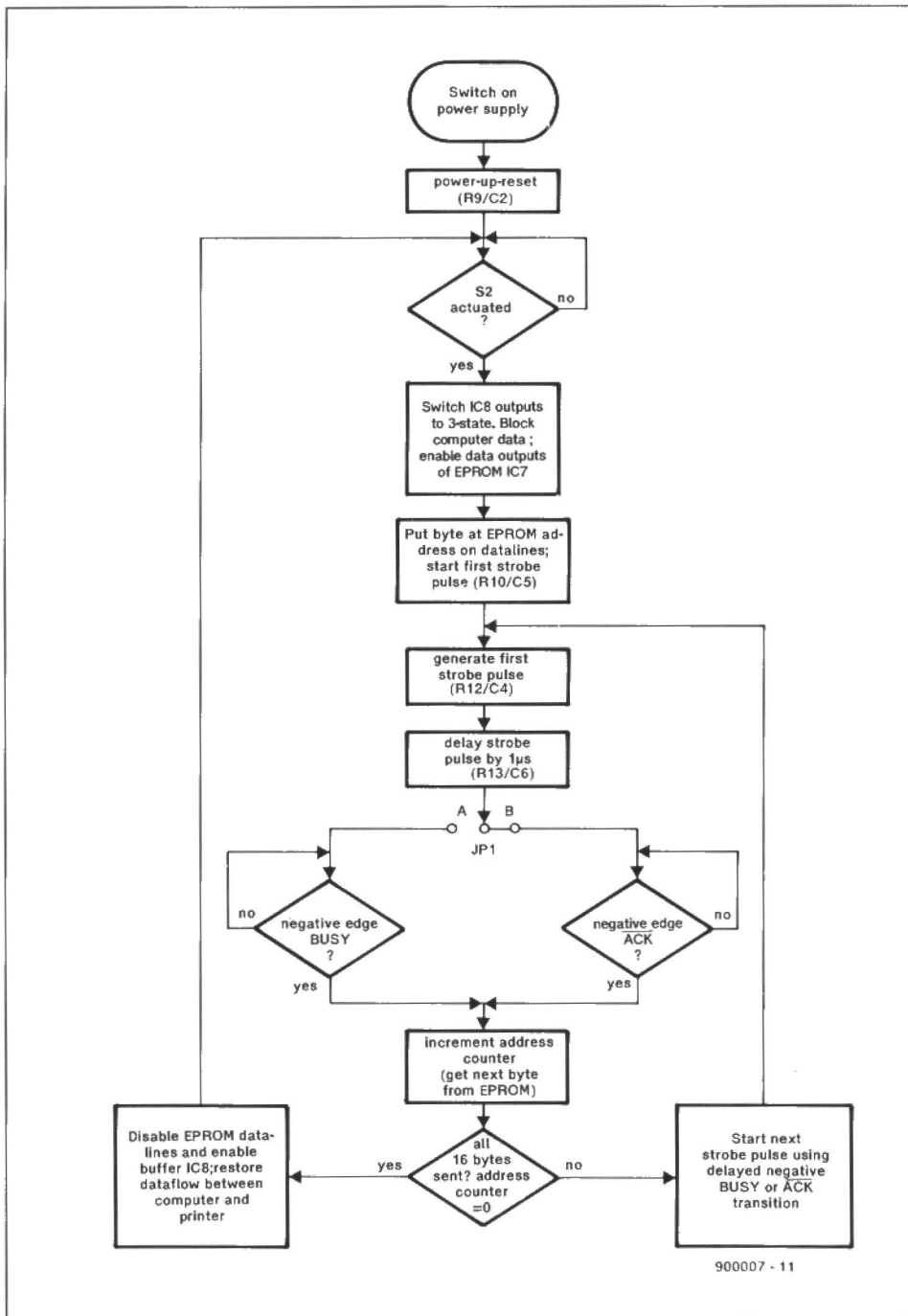


Fig. 1. This flowchart illustrates both the structure of the circuit and the pertinent timing.

a monostable multivibrator (MMV) and does not require a power-on reset because it goes to the stand-by state on its own. At this stage, the circuit functions as a 36-way connection between the computer at the input (K1) and the printer at the output (K2). The two devices are connected via three-state inverter/buffer IC8, inverters N9-N16 and the gates inserted in handshake lines BUSY, STROBE and ACK.

When S2 is pressed, its contact noise is eliminated by debounce network R7-C1. The short pulse generated by C1-R8 prevents the initialization sequence being restarted on completion if the switch has not been released in the mean time. Actuation of S2 causes FF2 to be set. The resultant high level at the Q output of FF2 causes the outputs of three-state buffer IC8 to be switched to the high-impedance state, and the BUSY and ACK inputs of the computer

to be taken high by N1-N17 and N2-N18 respectively. The low level at the Q output of FF2 enables the databuffers in EPROM IC7, and ends the reset state of counter IC5. The first strobe pulse is generated by FF1 which receives at its S (set) input a short pulse from the Q output of FF2 via network R10-C5. The length of the strobe pulse is determined by R12-C4. Capacitor C4 slowly discharges after FF1 has been set, and resets the bistable. Consequently, output Q goes high, so that C4 is rapidly charged again via D1. This ensures that FF1 is ready to generate the next strobe pulse.

The strobe pulse is delayed by about one microsecond in network R13-C6 to allow sufficient time for the EPROM data to reach output connector K2. Gates N8 and N19 feed the strobe pulse to the printer.

S1	address range initialization data
0 0 0 0	00 ... 0F
0 0 0 1	10 ... 1F
0 0 1 0	20 ... 2F
0 0 1 1	30 ... 3F
0 1 0 0	40 ... 4F
0 1 0 1	50 ... 5F
0 1 1 0	60 ... 6F
0 1 1 1	70 ... 7F
1 0 0 0	80 ... 8F
1 0 0 1	90 ... 9F
1 0 1 0	A0 ... AF
1 0 1 1	B0 ... BF
1 1 0 0	C0 ... CF
1 1 0 1	D0 ... DF
1 1 1 0	E0 ... EF
1 1 1 1	F0 ... FF

0=switch closed  
1=switch open

900007 - T1

Table 1. DIP switch settings.

The circuit waits until the printer is ready to accept a new command by monitoring either BUSY or ACK. The selection between these handshaking signals is made by the user with jumper JP1; the two are equally suitable, provided the printer supplies the relevant signal. Whatever signal is used, the negative pulse edge signals readiness to accept a new character. The pulse edge clocks address counter IC5 and causes a new strobe pulse to be generated. The start of the strobe pulse is, however, delayed by R11-C3 to prevent another pulse being generated when the 16th (last) byte has been sent to the printer. This delay is used by the circuit to block FF1 before it receives a new clock pulse. The end of the printer initialization sequence is marked by output QD of the address counter going low when count 16 is passed. The change from 16 to 0 causes FF2 to be clocked, so that FF1 is blocked — hence, the clock pulse generated in the mean time by R11-C3 has no effect. The toggling of FF2 also resets the circuit to its initial state.

The circuit is fully compatible with the Centronics interface on the computer as well as on the printer by virtue of pull-up resistors and open-collector TTL drivers respectively. DIP switch block S1 selects one of 16 printer initialization strings which have been pre-programmed in the EPROM. The selected address ranges in the EPROM are listed in Table 1. If frequent changes are expected in the setting of this switch, it may be replaced with a more ergonomic type or a set of switches, e.g., four miniature SPST types or a thumbwheel switch.

## Construction

The construction of the circuit on the double-sided, through-plated printed-cir-



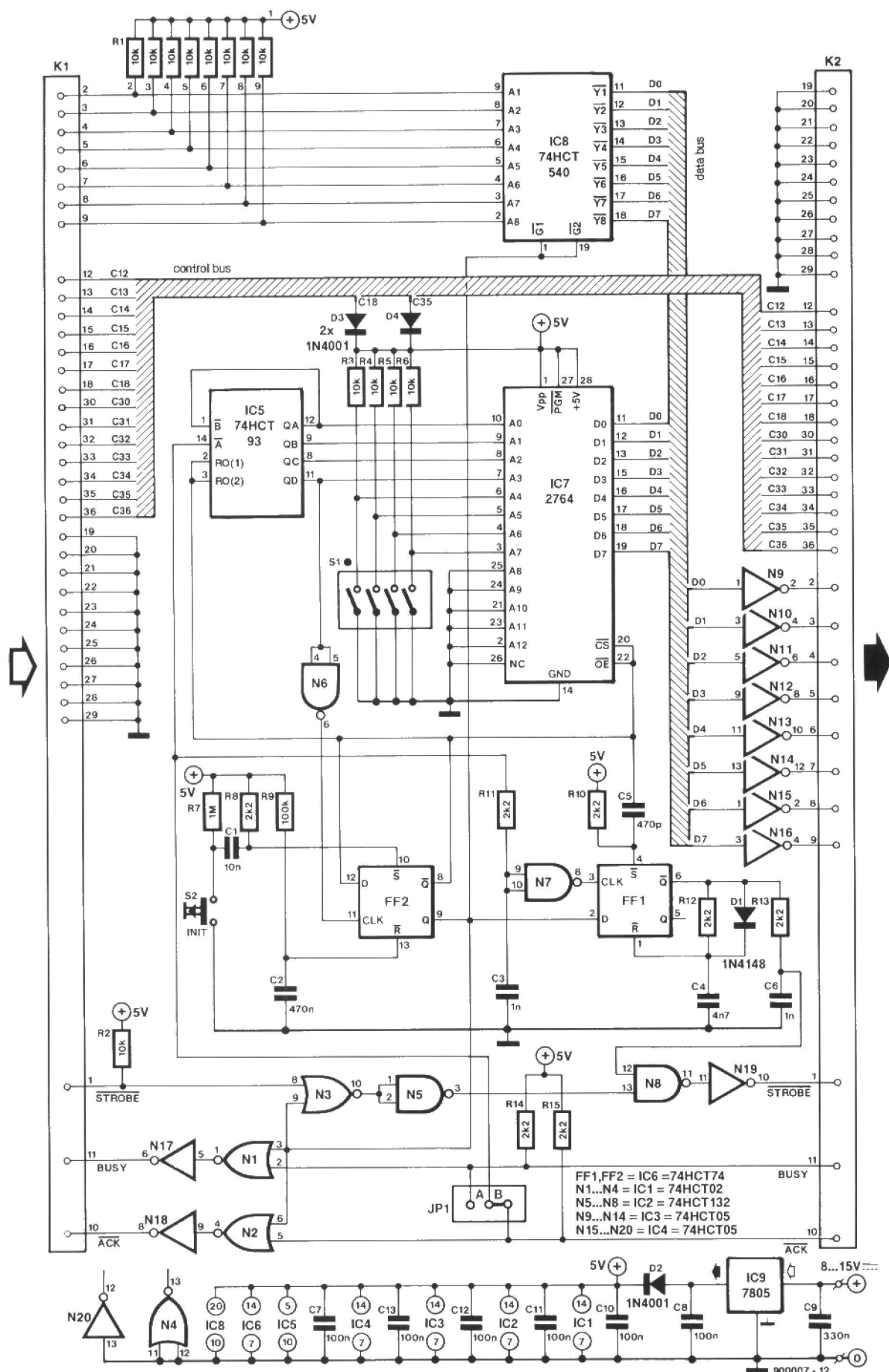


Fig. 2. Circuit diagram of the printer initialisation aid, a very useful peripheral device for advanced computer users.



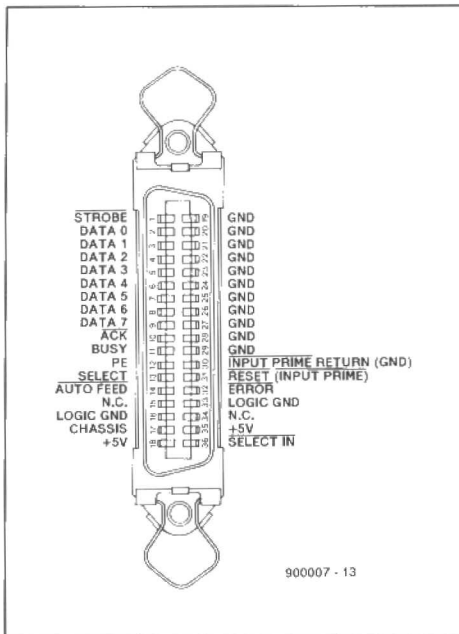


Fig. 3. Centronics connector pinning.

circuit board shown in Fig. 4 is straightforward. The pins of the Centronics connectors are simply pushed over the relevant copper fingers at the edges of the board

(mind the position of pin 1 of each connector). Next, solder the fingers to the pins, taking good care to avoid short-circuits between adjacent pins. Bolt the voltage regulator direct on to the board — a heat-sink is not required.

### Printer command strings

Upon completion of the board, the EPROM must be loaded with data. The manual supplied with your printer should give ample information on command strings to achieve the settings you require. The circuit allows a maximum of 16 command strings to be programmed, each with a fixed length of 16 bytes. The mini EPROM programmer described in Ref. 1 is suitable for loading the 256 bytes. If the required initialization sequence is shorter than 16 bytes, the remainder must provide null characters (00), or any other character which is ignored by the printer (again, consult your manual).

The sequence of commands to be programmed in the EPROM Type 2764 is first tested 'on line' with the aid of, say, GWBASIC. Document the final versions of the command strings. Next, compile the

```

10 RESTORE
12 OPEN "1pt1:" FOR OUTPUT AS #1
20 FOR N=1 TO 16
30 READ X
40 PRINT #1,CHR$(X);
50 NEXT N
55 CLOSE
60 DATA &H54,&H45,&H53,&H54
65 DATA &H00,&H00,&H00,&H00
70 DATA &H54,&H45,&H53,&H54
75 DATA &H00,&H00,&H00,&H00

```

900007 - 14

Fig. 5. GWBASIC test program listing.

databytes to be programmed from

databyte = 255 - data.

This inverts each byte to negate the inversion in the output buffers.

### Reference:

1. Mini EPROM programmer. *Elektor Electronics* January 1990.

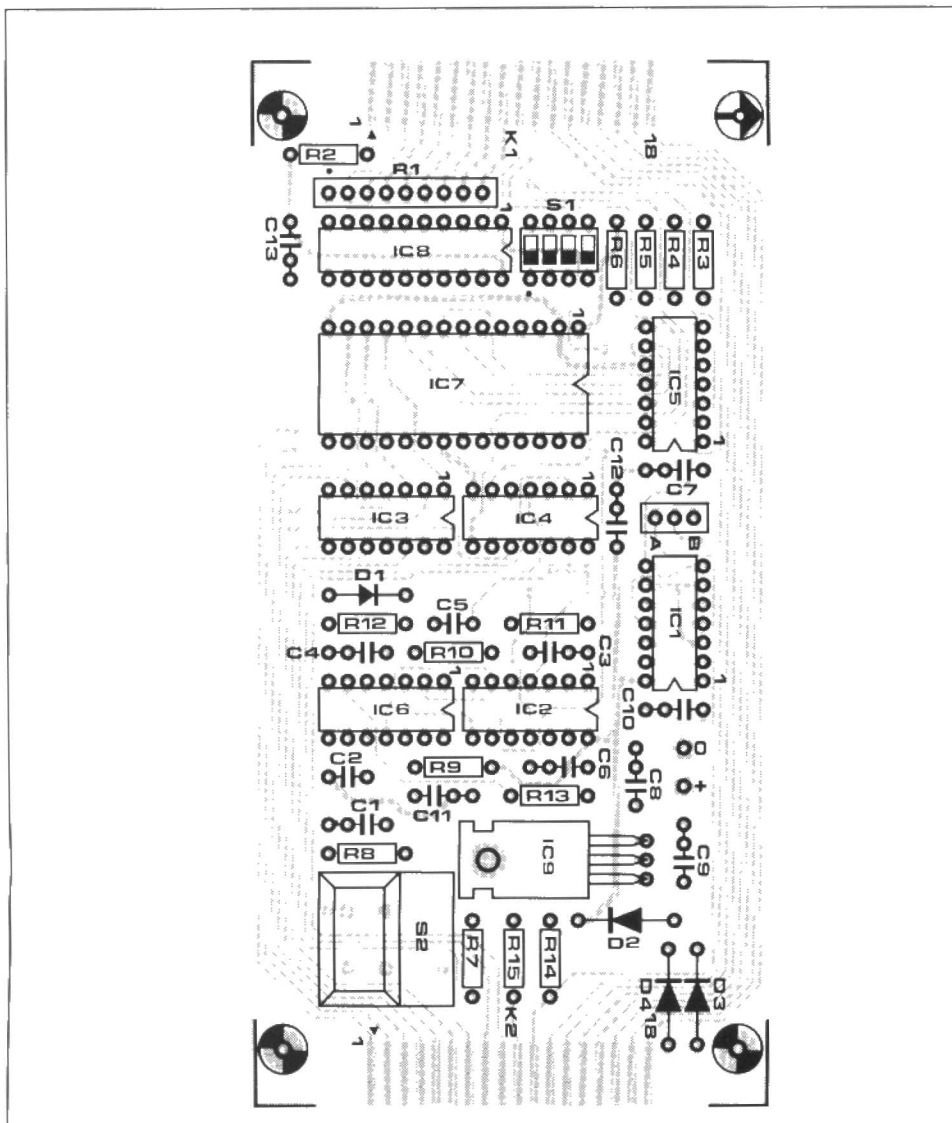


Fig. 4. Component mounting plan for the double-sided, through-plated circuit board.

### Parts list

#### Resistors:

R1 = SIL resistor array 8x10k  
R2 - R6 = 10k  
R7 = 1M0  
R8, R10, R11 - R15 = 2k2  
R9 = 100k

#### Capacitors:

C1 = 10n  
C2 = 470n  
C3, C6 = 1n0  
C4 = 4n7  
C5 = 470p  
C7, C8, C10 - C13 = 100n  
C9 = 330n

#### Semiconductors:

D1 = 1N4148  
D2, D3, D4 = 1N4001  
IC1 = 74HCT02  
IC2 = 74HCT132  
IC3, IC4 = 74HCT05  
IC5 = 74HCT93  
IC6 = 74HCT74  
IC7 = 2764 or 27C64(A)  
IC8 = 74HCT540  
IC9 = 7805

#### Miscellaneous:

K1 = 36-way female Centronics connector with straight pins.  
K2 = 36-way male Centronics connector with straight pins.  
S1 = 4-way DIP switch block.  
S2 = ITW Dataswitch push-button.  
3-way pin header.  
Jumper.  
PCB Type 900007 (double-sided; through-plated; see Readers Services page).



# CAPACITANCE METER

D. Folger

**A capacitance meter is indispensable for checking capacitors with illegible or incomprehensible values printed on them, and for matching capacitors in, for instance, higher-order filters. The instrument presented here is based on a simple circuit, has a handy size and five measurement ranges.**

To own a capacitance meter with a maximum error of 1% and a capacitance range of 1 pF to 1 F is wishful thinking for many electronics enthusiasts because such an instrument is not affordable, if it is at all available. Fortunately, not many applications require a capacitance meter with such impressive specifications. Consider, for instance, the selection of capacitors for a higher-order audio filter: here, the relative difference is much more important than the absolute value, and a simple capacitance meter may be used with impunity to select matching capacitors from an available lot.

## Measurement principle

The measurement principle used is fairly standard — see Fig. 1. The heart of the circuit is formed by a time-base which triggers a monostable multivibrator (MMV). The time constant,  $t$ , of the time base is set to a value that exceeds the maximum monostable delay. The MMV output changes from low to high on the negative edge of the time-base signal. The time it takes for the MMV to revert to the start state,  $t_w$ , is proportional to the value of the capacitor under test,  $C_x$ . Since the duration of the measurement cycle is determined by  $t$ , an integrator may be used to provide a voltage which is proportional to the value of  $C_x$ .

## Circuit description

In spite of the relatively simple measurement principle described above, the practical circuit presents a number of possible problems related to the translation of the unknown capacitance into an accurately determined numerical value.

The time-base is formed by a 1-MHz quartz crystal and an oscillator/divider, IC<sub>2</sub>. Output Q13 supplies a frequency of 1 MHz/16,384 = 61.035 Hz. This signal triggers IC<sub>3b</sub>, one of two MMVs contained in the Type TLC555 LinCMOS dual timer. The choice of the oscillator frequency is a compromise between the stability of the read-out and acceptable current consumption when relatively large capacitances are measured.

Given a time constant

$$t = 1/61.035 = 16.4 \text{ ms,}$$



### MAIN SPECIFICATIONS

Measurement ranges:	2 nF; 20 nF; 200 nF; 2 μF; 20 μF with overflow indication
Max. resolution:	1 pF
Max. error:	≤5%
Display:	3½ digit LCD
Scale factor:	nF/μF
Power supply:	9-V PP3 battery
Current consumption:	10–20 mA

a maximum monostable time of 10.5 ms and a maximum capacitance of 20 μF, the resistor  $R$  in the  $RC$  delay network is

simple to calculate from

$$t_w = 1.1RC$$

$$R = 10.5/(1.1 \times 20 \mu\text{F}) = 477 \Omega$$

A practical value of 475 Ω (1%) is used since this is available in the E96 series. The other measurement ranges are created by multiplying the basic value of  $R$  by the capacitance range factor, i.e., 10:  $R = 4k75$  for the 2 μF range;  $R = 47k5$  for the 200 nF range;  $R = 475k$  for the 20 nF range;  $R = 4M75$  for the 2 nF range.

The output signal of IC<sub>3b</sub> has a duty factor  $t_w/t$  and requires averaging to obtain a direct voltage proportional to the duty factor and, therefore, to the value of  $C_x$ . Integration capacitor  $C_{12}$  is charged via potential divider  $R_{14}$ - $P_3$ - $R_{15}$  if the MMV output is high, and discharged if the MMV output is low. This arrangement produces an average voltage,

$$U_2 = U_{1(H)}(t_w/t)$$

Note, however, that because of the adjustable potential divider the high level,  $U_{1(H)}$ , is lower than the high output level provided by the MMV. The maximum value of  $U_2$  is not reached immediately, but after a delay of about 600 ms, which corresponds roughly to the time constant of the integration network.

The 150 pF capacitor connected in parallel with  $C_x$  is required as a minimum capacitance in the external  $RC$  network of the LinCMOS timer. Without  $C_8$ , the MMV may not be triggered reliably if small capacitors (in the pF range) are tested. The resultant off-set is compensated with the aid of a second MMV, IC<sub>3a</sub>, of which the external configuration is almost identical to that of IC<sub>3b</sub>.

The low voltage,  $U_L$ , at the output of the second integrator is used as a reference for  $U_H$ . Capacitors  $C_7$  and  $C_8$  and resistors  $R_4$ - $R_{12}$  determine the time delays set with the MMV, and must, therefore, be close-tolerance types.

Spurious triggering and incorrect capacitance indications may occur if measured values exceed the maximum of a particular range. Each measurement cycle is, therefore, stopped after 12 ms. As shown in Fig. 3, the remaining 4 ms are used to discharge the capacitor under test via FET  $T_2$ . The timing of the discharge


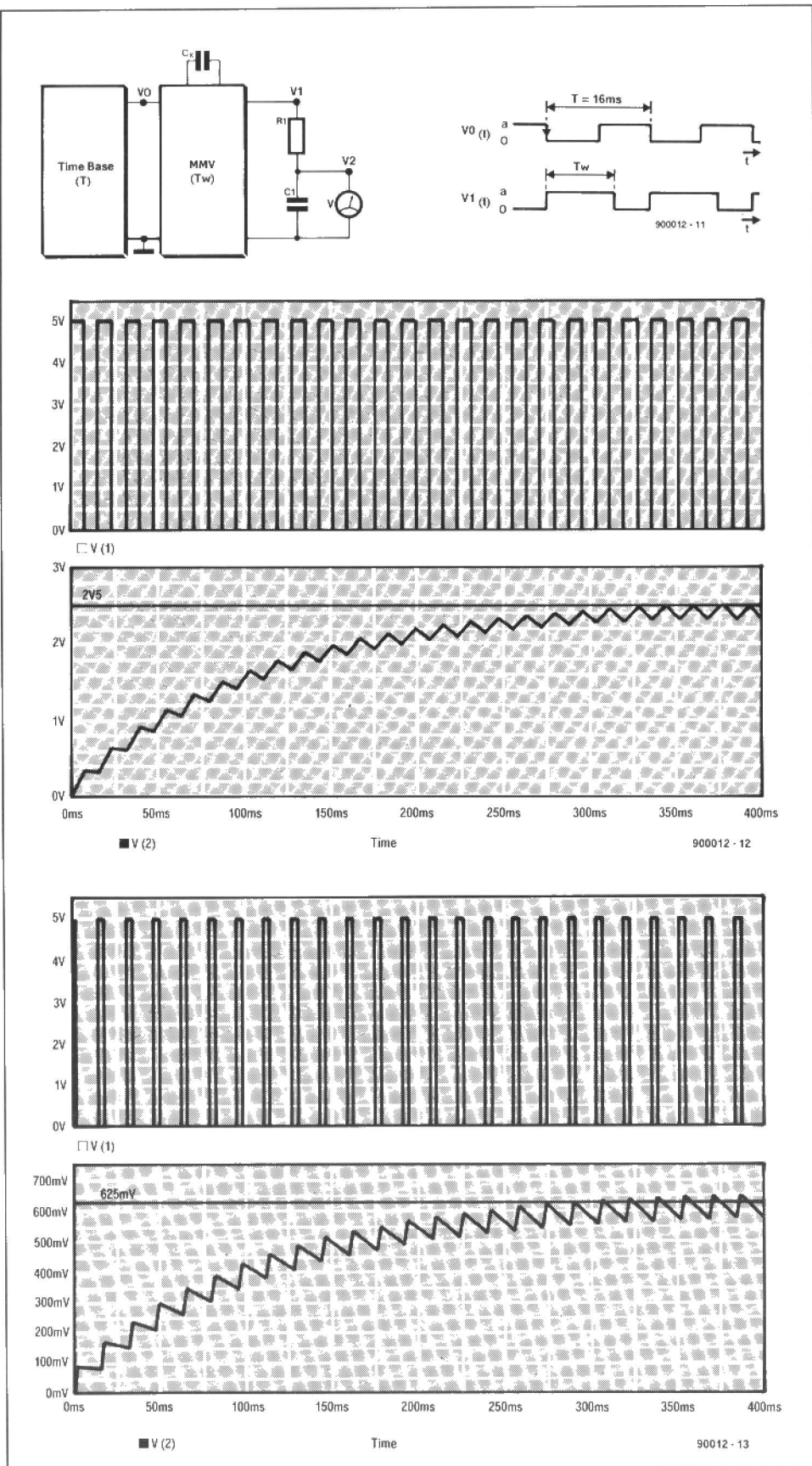


Fig. 1. Measurement principle and graphs to illustrate the operation of the R-C integrator.

period is arranged by the AND diode configuration of D<sub>3</sub> and D<sub>4</sub> at the Q12- and Q13-outputs of IC<sub>2</sub>. These diodes cause the MMV output to remain permanently high when a too large capacitor is connected. In this condition, the voltage at the two MMV outputs causes the LC display to indicate '1'. The measurement error in-

troduced by T<sub>2</sub> is compensated by its counterpart, T<sub>1</sub>, in the other MMV circuit.

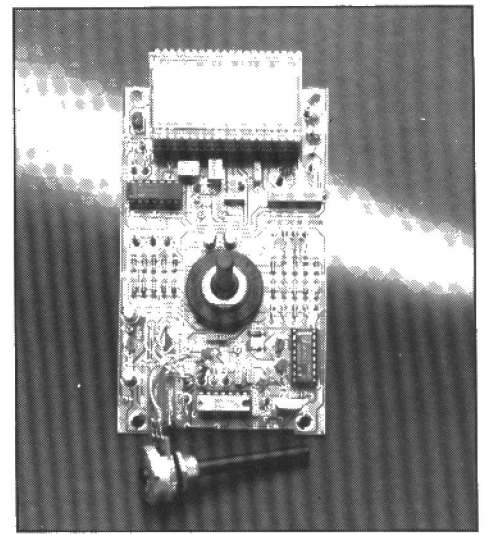The display circuit is based on the well-known Type ICL7106 A-D (analogue-to-digital) converter with integrated 3½-digit LCD (liquid crystal display) driver. The ICL7106 is used in a standard application circuit with the decimal point



switching arranged by S<sub>2b</sub>, D<sub>15</sub>-D<sub>19</sub> and N<sub>1</sub>-N<sub>4</sub>. The scale factor (nF or μF) indicators, D<sub>1</sub> and D<sub>2</sub>, are driven by a diode circuit, D<sub>20</sub>-D<sub>24</sub>.

The power supply of the circuit is of a less usual configuration: a Type 79L05 voltage regulator is inserted in the negative supply line to create a supply with +5 V and -4 V outputs. The non-regulated negative voltage is applied as bias to the ADC in the ICL7106, which requires that the voltage at the V<sub>-</sub> input (pin 26) is always 1 V below that at IN HI.

The circuit around T<sub>3</sub> controls the LOW BAT symbol on the display. With R<sub>19</sub>=220k, this circuit is actuated when the battery voltage drops below about 8 V.

## Construction and adjustment

The complete circuit is built on a printed-circuit board that fits into an ABS, standard-size hand-held enclosure with integral battery compartment. The circuit to the right of the dashed line in the circuit diagram, and diodes D<sub>15</sub>-D<sub>24</sub>, may be omitted if the capacitance meter is used in conjunction with a digital multimeter that assumes the display function.

The population of the PCB should not present problems. The high-value 1% resistors, R<sub>8</sub> and R<sub>12</sub> (4.75 MΩ), may be difficult to obtain in small quantities. They may, however, be selected from a batch of 4.7 MΩ 5% types with the aid of a DMM.

Fit two four- or five-way terminal blocks on to the front panel of the enclosure for connecting the capacitors to be tested. Be sure to use high-quality terminals to avoid problems with wear and tear of the contacts. A two-way loudspeaker terminal block for wire insertion is a fine alternative to multi-way blocks since it provides fairly wide contacts which allow capacitors with different terminal spacings to be inserted.

Large capacitors of which the wires can not be inserted into the terminal blocks on the instrument must be connected with test leads. Do not use these leads for small capacitors, since the wire capacitance will make the indicated value worthless. P<sub>1</sub> is



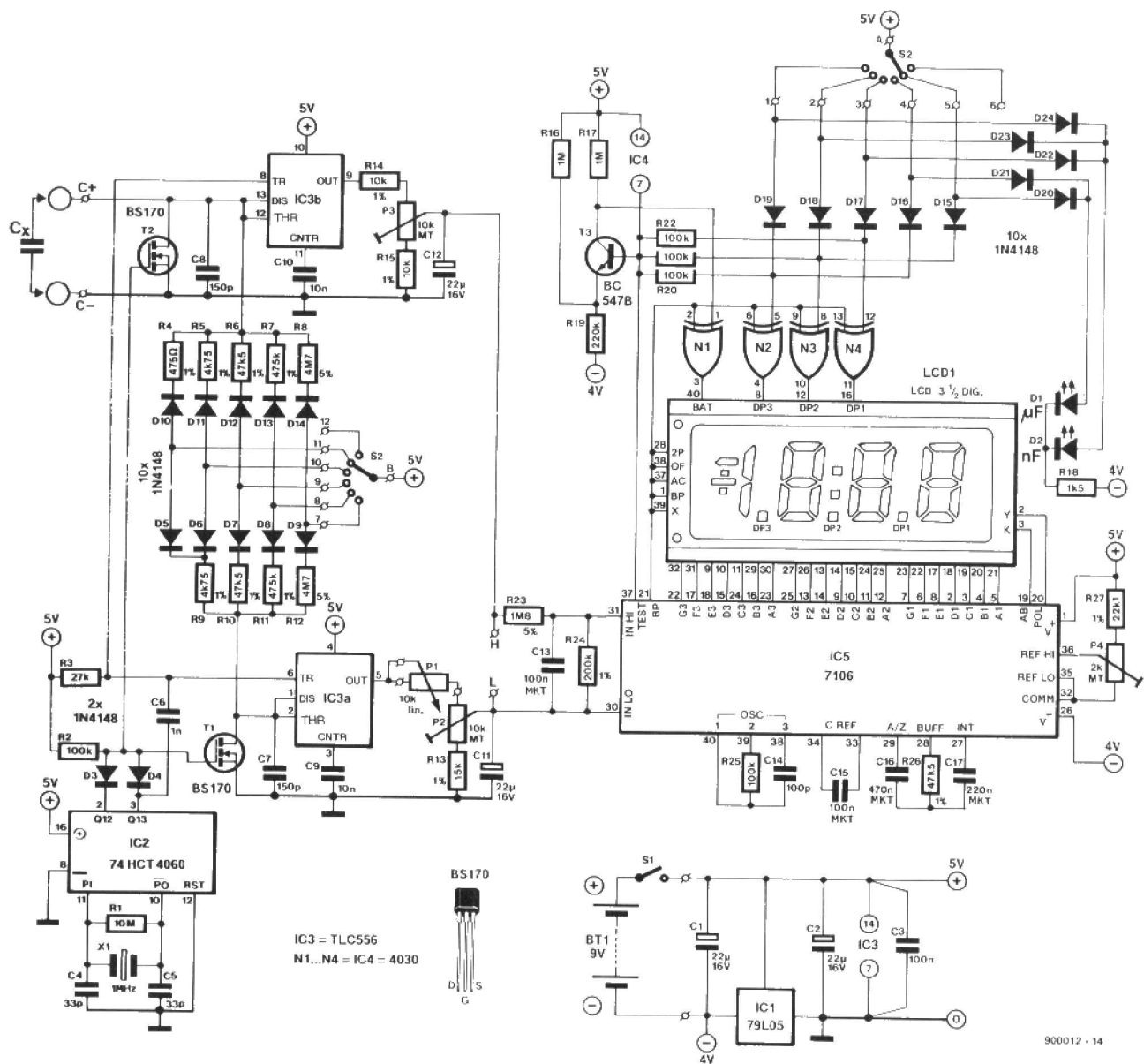


Fig. 2. Circuit diagram of the capacitance meter.

either a preset with an adjustment spindle or a potentiometer with a 4 mm spindle. It allows test lead capacitance to be compensated.

The accuracy of the instrument is determined mainly by the quality and tolerance of resistors R9–R12.

Connect a 1% or 2% polystyrene (styroflex) or silver-mica capacitor with a known value in the lowest measurement range (e.g., 1 nF). Set S2 to the 2 nF range, set P1 to the centre of its travel and P2 and P3 to maximum resistance to ground. Connect the reference capacitor, and adjust P4 until the correct value is displayed. Disconnect the reference capacitor and adjust the zero-indication of the meter with P2. Repeat the adjustments of P2 (capacitor connected) and P4 (capacitor disconnected) until the indicated value and the zero indication are both correct.

#### DMM as display

The value of the test capacitor must be adjusted with P3 instead of P4 if a DMM set to the 2 V range is connected to points L and H. The 'meter-zero' control, P1, is replaced by a 5.11 kΩ 1% resistor in this case because the adjustments for meter zero and capacitor value interact. Set P3 to maximum resistance to ground, and ad-

just P2 until the DMM reads 0 V. Connect the reference capacitor and adjust P3 until the correct value is displayed. Repeat the adjustments of P2 and P3 as detailed above for P2 and P4.


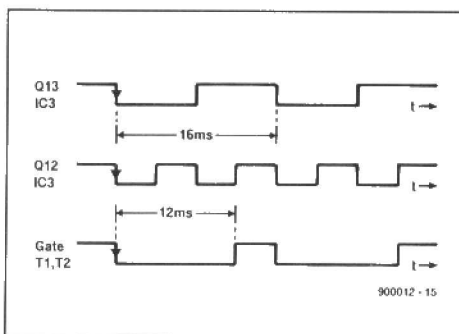


Fig. 3. The measurement cycle is stopped after 12 ms to discharge too large capacitors.

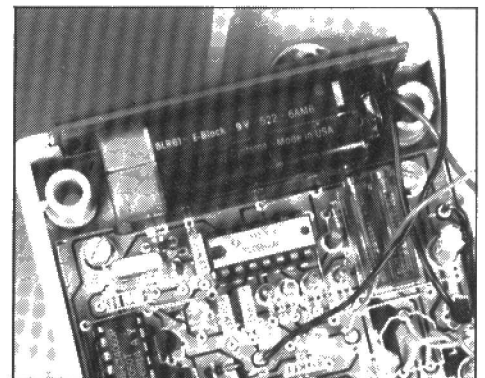

Close-up of the battery compartment.

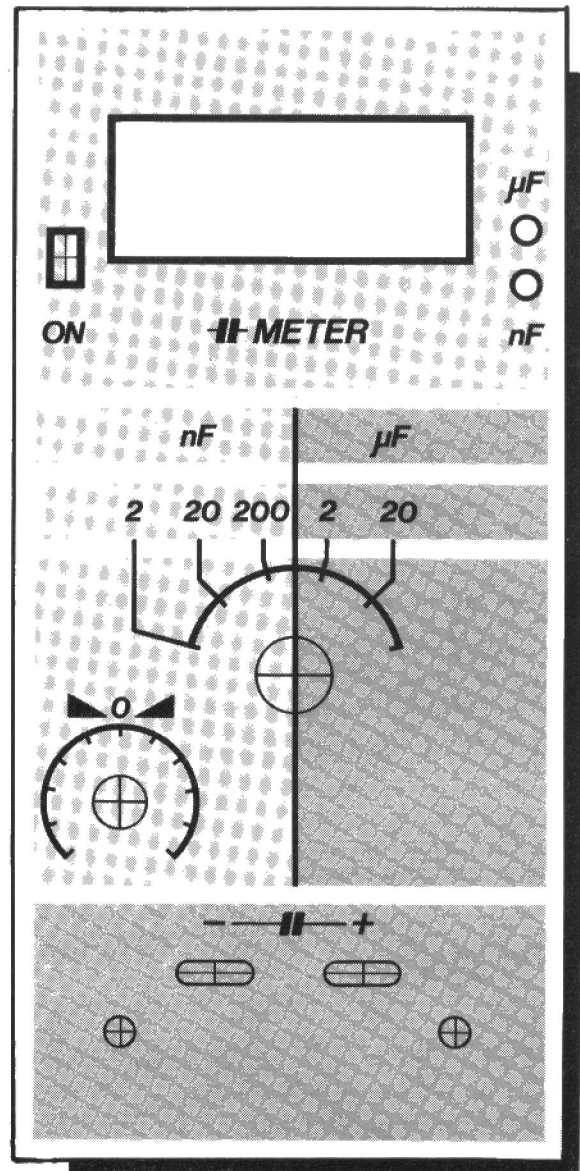
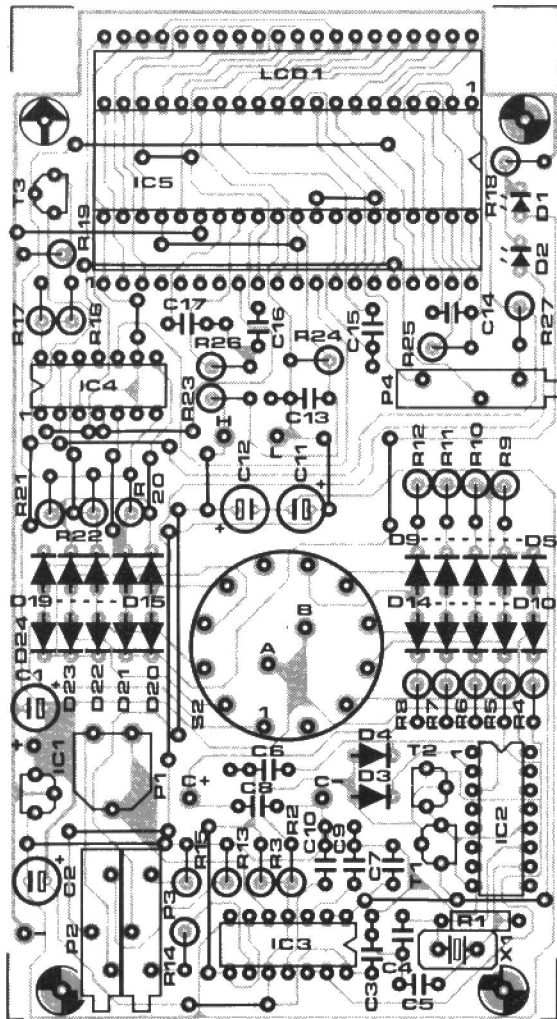


Fig. 4. Component mounting plan of the printed-circuit board for the capacitance meter (left) and suggested front-panel lay-out (right).

#### Parts list

##### Resistors:

R1 = 10M  
 R2;R20;R21;R22;R25=100k  
 R3 = 27k  
 R4 = 475Ω 1%  
 R5;R9 = 4k75 1%  
 R6;R10;R26 = 47k5 1%  
 R7;R11 = 475k  
 R8;R12 = 4M7 5% (see text)  
 R13 = 15k 1%  
 R14;R15 = 10k 1%  
 R16;R17 = 1M0  
 R18 = 1k5  
 R19 = 220k  
 R23 = 1M8 5%  
 R24 = 200k 1%  
 R27 = 22k1 1%  
 P1 = 10k linear potentiometer with 4 mm

spindle or 10k preset for horizontal mounting with spindle.

P2;P3 = 10k multiturn preset

P4 = 2k multiturn preset

##### Capacitors:

C1;C2;C11;C12 = 22μ; 16 V, radial  
 C3 = 100n  
 C4;C5 = 33p  
 C6 = 1n0  
 C7;C8 = 150p polystyrene (styroflex)  
 C9;C10 = 10n  
 C13;C15 = 100n MKT  
 C14 = 100p  
 C16 = 470n MKT  
 C17 = 220n MKT

##### Semiconductors:

D1;D2 = LED; 3 mm; red  
 D3 – D24 = 1N4148  
 T1;T2 = BS170

T3 = BC547B

IC1 = 79L05

IC2 = 74HCT4060

IC3 = TLC556 (LinCMOS)

IC4 = CD4030

IC5 = ICL7106


##### Miscellaneous:

S1 = miniature slide SPST slide switch.  
 S2 = 2-pole 6-way PCB-mount rotary switch.  
 X1 = 1 MHz quartz crystal.  
 LCD1 = general-purpose 3½-digit LC display.  
 9-V PP3 battery with clip and leads.  
 Hand-held ABS enclosure, e.g., Monacor PLG750BN (160×80×75 mm).  
 Loudspeaker terminal block.  
 PCB Type 900012 (see Readers Services page).



# CAR THEFT DETERRENT

by David Butler

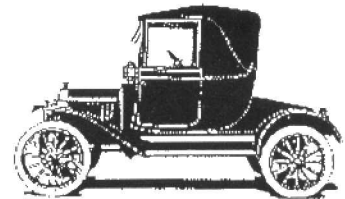

Cars seem to attract thieves, probably because of the relative ease of entering them. Anyone who has locked their keys inside will testify that a bent coathook can usually secure an early reunion. The deterrent proposed is aimed at discouraging casual joyriders who want not want to risk setting off an alarm – even if, as here, one did not exist. In fact, the deterrent is simply an alarm type indication that, if accompanied by suitable warning stickers, should provide basic protection. It must be stressed, of course, that this deterrent does not act as an alarm and it would be wise to invest in a security system, such as an immobilizer or a Krookloc.

The idea of a dummy alarm is not new, but the present design adds more credibility by the use of a single dual function LED. When the ignition is on, the LED radiates a steady green light to show that the 'system' is 'disarmed'. When the ignition is switched off, the LED emits a flashing red light to simulate 'alarm enable'.

The success of this idea rests with displaying the LED prominently (say, next to the ignition switch) and not telling anybody that it is just a flashing light! The project is inexpensive, simple to construct and install, and performs a worthwhile function.

## Circuit description

The circuit is designed around a dual function LED. This device looks like a normal 5 mm diameter clear LED, but has three terminals. The casing actually houses a green LED and a red LED driven by a flasher unit. The cathodes of the LEDs are commoned to the centre pin. When a voltage in the range 4.75–7.0 V is applied to the 'R' terminal, the red LED will flash at a rate of about 1.5 Hz. The green LED is connected to the other terminal (indicated by a

### Features:

**Deters casual joyriders from stealing your vehicle.**

**Inexpensive, simple design.**

**Compact dimensions.**

**Easy to install (3 wires).**

flat on the casing) and requires a series current limiting resistor to operate from any supply.

The relay used is of extremely small dimensions, and has a single-pole change-over contact set. The coil is energized by the +12 V ignition circuit in the car, with back e.m.f. protection provided by D2.

The LED terminals are connected to the relay contact set so that normally the red flashing LED is actuated (ignition off state). The regulator circuit formed by R1, D1 and C1 provides a fixed voltage for both LEDs. This was chosen to avoid problems

### COMPONENTS LIST

#### Resistors:

R1 = 390R; 0.25 W;  $\pm 5\%$  or better; carbon  
R2 = 220R; 0.25 W;  $\pm 5\%$  or better; carbon

#### Capacitor:

C1 = 100n; ceramic

#### Semiconductors:

D1 = 5V1; 400 mW; zener diode  
D2 = 1N4001  
LED1 = continuous green/flashing red LED  
(Maplin Electronics order code QY99H)

#### Miscellaneous:

RLA = micro miniature single pole change-over contacts; 12 V 320R coil  
(Maplin Electronics order code BK47B)  
PL1 = 4-way right-angle PCB type plug  
SK1 = 4-way housing plus contacts  
5 mm LED clip  
PCB or veroboard  
In-line fuseholder with 150 mA 20 mm fuse (if required)

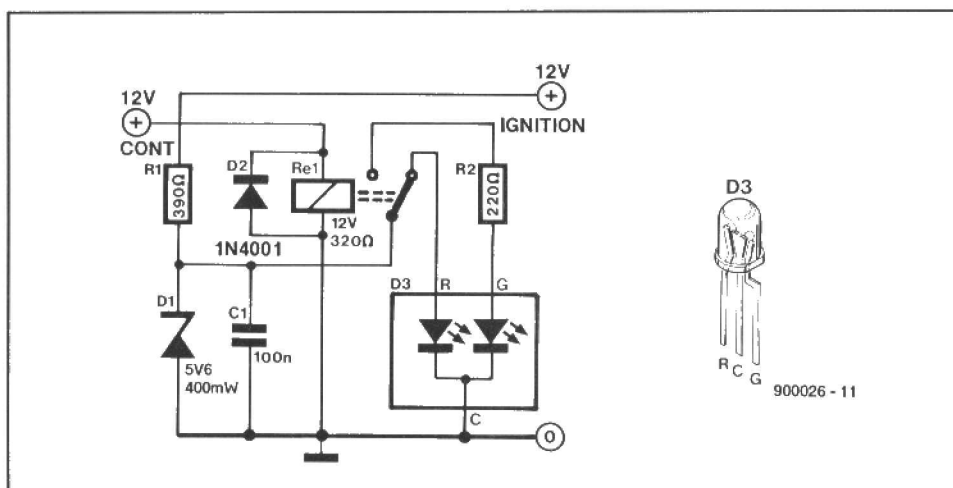


Fig. 1. Circuit diagram (ignition switched off).

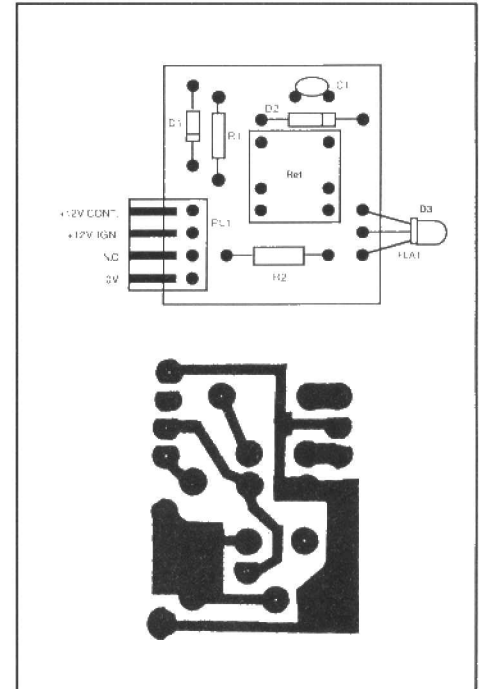


Fig. 2. Printed-circuit board of the deterrent. The component side is shown true to scale.

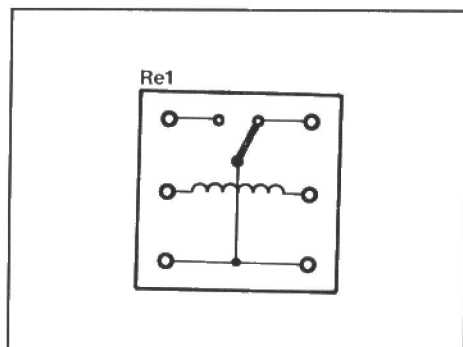


Fig. 3. Pinout of the relay (seen from the base.)

with the car's voltage supply.

The circuit consumes about 50 mA when the ignition is on and around 15 mA with the ignition switched off.

## Construction notes

The prototype was constructed on a scrap of vero board and then transferred on to a PCB (see Fig. 2). Although the method of construction is not important, care should be exercised in connecting the polarized components: D1, D2 and the LED.

## Installation notes

The prototype unit was installed in the author's Metro, which conveniently has a spare blanking plate next to the rear screen heater switch. This is quite close to the ignition switch and would be instantly noticed by any curious potential thief.

No doubt, other vehicles will have similar places to mount the LED, which requires a 6.35 mm dia. hole.

Once the LED is mounted, three wires run from the PCB may be connected to it with the aid of Scotchlock type break-in terminals. Usually, the set of wires leading to the radio can be used: +12 V continuous means that +12 V is available even when the ignition is switched off; +12 V ign means that the +12 V line is switched via the ignition.

For extra electrical protection an in-line fuse holder with a 150 mA fuse may be used: this rating depends on that of the car fuse fitted to the circuit being used.

Apart from these brief notes, no other fitting instructions can be given as each vehicle will vary.

Generally, the unit should be fitted away from sources of direct heat, with the LED displayed in a prominent position where it does not distract the driver.


# CALSOD NOW EVEN MORE VERSATILE

**The computing and optimization of loudspeaker enclosures is nowadays normally effected by computer. One of the programs that enables the complex calculations to be carried out on an IBM PC desktop computer is CALSOD, the first version of which was reviewed in this magazine last year. We have recently received an improved version of this program that offers even more possibilities to the professional designer to approach realistic sound reproduction.**

Designing loudspeaker enclosures requires such extensive measurements and calculations nowadays that it has become virtually impossible without the use of a computer and a suitable program. Last year we reviewed\* CALSOD, a unique combination of a simulation and an optimization program. We then thought that there was very little left to be desired. None the less, the designers have succeeded in adding some more facilities to their latest version 2.00, which bring the results even more closely to realistic sound reproduction.

The new version offers the possibility of working with a coprocessor. This is an especially welcome addition for XT's, since computations on these of three- or four-way systems are relatively slow (but still a lot faster than with comparable programs). However, this facility is merely to do with speed of processing.

To us, the most interesting addition is the RAB sub-module. This makes it possible to calculate the frequency characteristic of the entire system at a given angle (both horizontal and vertical) with respect to the listening axis, for instance,  $\pm 30^\circ$ . Even in the optimization of the filters this off-axis response may be taken into account. It is thus possible, for example, to design a filter whose characteristic remains within certain limits for an off-axis response of  $\pm 10^\circ$

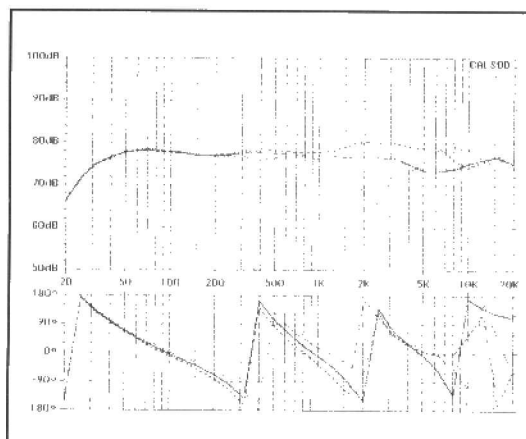

with respect to the listening axis (see illustration above).

The loudspeaker placement has also been extended. The original version enables the loudspeaker location to be calculated in a three-dimensional space: the new version makes it possible to take into account that loudspeakers are placed at an angle (for instance, in case of a backward sloping enclosure front). Also, the effective diameter of the drive units may be taken into account, so that the program may make provision for the radiation pattern of each individual drive unit.

Apart from optimization of the filter components to obtain a given characteris-

tic, it is now also possible to optimize the impedance of an individual loudspeaker or of the entire system. To that end, compensation networks are added that are calculated by the computer in a manner that keeps the impedance in a predetermined frequency range within a given percentage of a certain value. This is a very useful facility for compensating the behaviour of individual loudspeakers and for straightening out the impedance characteristic of a complete system, to ensure that the power amplifier is connected to a truly resistive load.

There is also a 'student' version (1.20) of the program available at a sharply reduced price (\$A99.00). This version offers all the facilities we have discussed. Its data files are compatible with Version 2.00 (\$A349.00) so that transfer to the professional version at a later date is facilitated.

CALSOD is available from the designers, **Audiosoft, 128 Oriel Road, West Heidelberg 3081, MELBOURNE, Australia**. It may also be obtained from **Old Colony Sound Lab, P O Box 243, PETERBOROUGH NH 03458, USA**, or, in Europe, from **Audio Specialists, Weichselstrasse 22, 1000 BERLIN, Federal Germany**.


\*Elektor Electronics, January 1989, p. 62


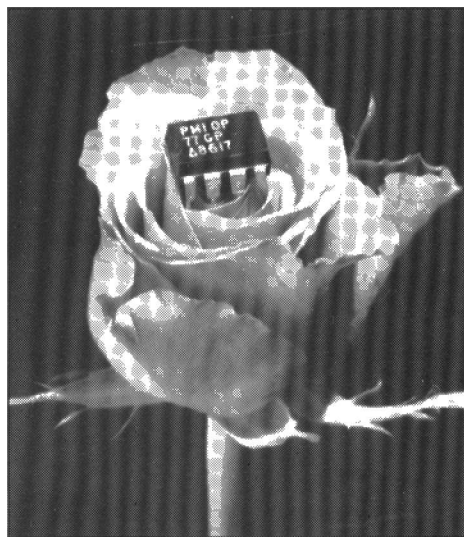
# INTRODUCING OP-SERIES OPAMPS

J. Ruffell

Dozens of new, improved operational amplifiers are introduced every month by leading IC manufacturers around the world. A number of high-performance opamps from the 'young' OP-series are described in relation with construction projects featured in this magazine over the past year or so. The reasons for preferring these new devices over, say, a Type 741 are manifold and call for an introduction to opamp selection criteria.



Designing a wide variety of clever electronic circuits on the basis of ideal operational amplifiers is fairly easy. In not a few cases, however, the efforts remain paper designs after the disappointing results obtained with practical constructions. The problem is clear: the ideal opamp does not exist. The ideal model does have its uses, however, because it allows the operation of complex circuits based on opamps to be analysed and understood.

In practice, the ideal opamp is only useful for the design of low-performance circuits, and for function analyses. In all other cases, the most important non-ideal characteristics must be taken into account. The relative importance of all the design parameters involved depends on the type of circuit in which the opamp is to be used. In an alternating-voltage amplifier, for instance, off-set drift is less important than the slew rate. Conversely, the performance of a DC amplifier is limited by off-set drift rather than the slew rate.

Distinguishing between the important and the not so important opamp characteristics on the basis of the function of the circuit not only raises the quality of the final product, but also avoids needlessly complex calculations. Clearly, a well-

**ELECTRICAL CHARACTERISTICS** at  $V_S = \pm 15V$ ,  $55^\circ C \leq T_A \leq 125^\circ C$ , unless otherwise noted.

PARAMETER	SYMBOL	CONDITIONS	OP-07A			OP-07			UNITS
			MIN	TYP	MAX	MIN	TYP	MAX	
Input Offset Voltage	$V_{OS}$	(Note 1)	—	25	80	—	60	200	$\mu V$
Average Input Offset Voltage Drift Without External Trim	$TCV_{OS}$	(Note 2)	—	0.2	0.6	—	0.3	1.3	$\mu V/^\circ C$
With External Trim	$TCV_{OSa}$	$R_P = 20k\Omega$ (Note 3)	—	0.2	0.6	—	0.3	1.3	$\mu V/^\circ C$
Input Offset Current	$I_{OS}$		—	0.8	4	—	1.2	5.6	nA
Average Input Offset Current Drift	$TCI_{OS}$	(Note 2)	—	5	25	—	8	50	$pA/^\circ C$
Input Bias Current	$I_B$		—	+1	+4	—	+2	+6	nA
Average Input Bias Current Drift	$TCI_B$	(Note 2)	—	8	25	—	13	50	$pA/^\circ C$
Input Voltage Range	$V_{IR}$		+13	+13.5	—	+13	+13.5	—	V
Common-Mode Rejection Ratio	CMRR	$V_{CM} = \pm 13V$	106	123	—	106	123	—	dB
Power Supply Rejection Ratio	PSRR	$V_S = 1.5V$ to $\pm 15V$	—	5	20	—	5	20	$\mu V/V$
Large-Signal Voltage Gain	$A_{VO}$	$R_L \geq 2k\Omega$ , $V_O = \pm 10V$	200	400	—	150	400	—	V/mV
Output Voltage Swing	$V_O$	$R_L \geq 2k\Omega$	+12	+12.6	—	+12	+12.6	—	V

**NOTES:**

1. OP-07A grade  $V_{OS}$  is measured approximately one minute after application of power. For all other grades  $V_{OS}$  is measured approximately 0.5 seconds after application of power.
2. Sample tested.
3. Guaranteed by design.

Parameter	Conditions	LM741A/LM741E			LM741			LM741C			Units
		Min	Typ	Max	Min	Typ	Max	Min	Typ	Max	
Input Offset Voltage	$T_A = 25^\circ C$ $R_S \leq 10k\Omega$ $R_S \leq 50\Omega$		0.8	3.0		1.0	5.0		2.0	6.0	mV mV
	$T_{AMIN} \leq T_A \leq T_{AMAX}$ $R_S \leq 50\Omega$ $R_S \leq 10k\Omega$			4.0			6.0			7.5	mV mV
Average Input Offset Voltage Drift				15							$\mu V/^\circ C$
Input Offset Voltage Adjustment Range	$T_A = 25^\circ C$ , $V_S = \pm 20V$	$\pm 10$				$\pm 15$			$\pm 15$		mV
Input Offset Current	$T_A = 25^\circ C$		3.0	30		20	200		20	200	nA
	$T_{AMIN} \leq T_A \leq T_{AMAX}$			70		85	500			300	nA
Average Input Offset Current Drift				0.5							$nA/^\circ C$
Input Bias Current	$T_A = 25^\circ C$		30	80		80	500		80	500	nA
	$T_{AMIN} \leq T_A \leq T_{AMAX}$			0.210			1.5			0.8	$\mu A$
Input Resistance	$T_A = 25^\circ C$ , $V_S = \pm 20V$	1.0	6.0		0.3	2.0		0.3	2.0		M $\Omega$
	$T_{AMIN} \leq T_A \leq T_{AMAX}$ , $V_S = \pm 20V$	0.5									M $\Omega$
Input Voltage Range	$T_A = 25^\circ C$							$\pm 12$	$\pm 13$		V
	$T_{AMIN} \leq T_A \leq T_{AMAX}$				$\pm 12$	$\pm 13$					V
Large Signal Voltage Gain	$T_A = 25^\circ C$ , $R_L \geq 2k\Omega$ $V_S = \pm 20V$ , $V_O = \pm 15V$ $V_S = \pm 15V$ , $V_O = \pm 10V$	50			50	200		20	200		V/mV V/mV
	$T_{AMIN} \leq T_A \leq T_{AMAX}$ , $R_L \geq 2k\Omega$										V/mV V/mV
	$V_S = \pm 20V$ , $V_O = \pm 15V$ $V_S = \pm 15V$ , $V_O = \pm 10V$	32			25			15			V/mV V/mV
	$V_S = \pm 15V$ , $V_O = \pm 10V$ $V_S = \pm 15V$ , $V_O = \pm 2V$	10									V/mV V/mV

890151 - 11

Fig. 1. Main specifications of the OP07 and OP07A compared to those of the 741A/E/C.

founded choice can only be made on the basis of knowledge and experience.

Infinite amplification and input impedance and zero output impedance are probably familiar terms in relation to opamps. The real thing, however, starts with off-set voltages, input bias currents, noise, slew rate, and many other factors.

## Opamp technology

Several integration technologies are used in the production of opamps. In their quest for the ideal opamp, manufacturers are faced with a real dilemma: improvement of one opamp characteristic results in degradation of another. Inevitably, a particular integration technology is linked with near-optimum performance in one or a few respects only. A clear example of this vicious circle is that an increase of the slew rate is inevitably coupled to increased current consumption. Although not all opamp characteristics can be optimized at the same time, today's production techniques do allow improvements in the performance to be achieved if the aim is clearly defined. This results in a particular opamp performing better than another in the same application. The use of the most favourable production technology for a particular characteristic has resulted in many opamp families with many members. Currently, the four major technologies are bipolar, BiFET, BiMOS and LinCMOS (Ref 1).

## Off-set and drift

Bipolar opamps such as the ubiquitous 741 consist of npn and pnp transistors. Bipolar amplifiers have the best specifications as regards stability of the input off-set voltage. This characteristic is often referred to as input voltage drift, or the temperature co-efficient,  $dU_{os}/dT$ , of the input off-set voltage.

Field-effect transistors are less easy to match than bipolar transistors, and as a result BiMOS and BiFET opamps generally suffer from the resultant drift effects. Modern bipolar opamps such as the Type OP07 are specified for a maximum off-set voltage drift of  $1.3 \mu V/K$ , although values better than  $0.2 \mu V/K$  are no exception.

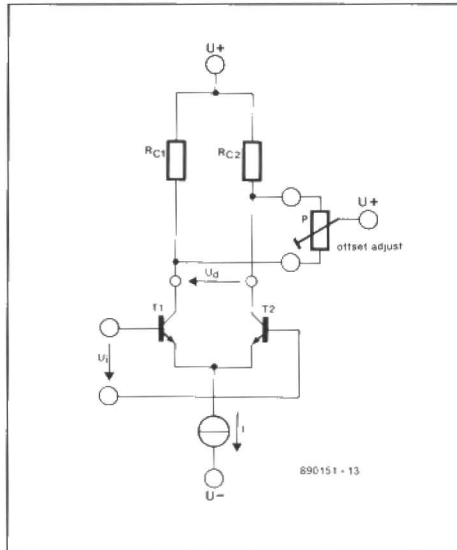


Fig. 3. Opamp input with external offset compensation preset.

This means that the drift specification of the OP07 is roughly 15 times better than that of the 741.

Extracts from the datasheets of the OP07 and the 741 are given in Fig. 1. Clearly, the OP07 has a smaller drift, and the absolute value of the off-set voltage is also lower. Apparently, the drift specification may be improved by keeping the absolute off-set voltage,  $U_{os}$ , small.

## Zener-zap trimming

This technique is used to reduce  $U_{os}$  of the OP07 to a value smaller than  $200 \mu V$  without the use of external components. The function and operation of zener-zap trimming is best explained by studying the cause of the off-set voltage.

The basic structure of a standard bipolar opamp input circuit is shown in Fig. 2. The output voltage,  $U_d$ , is the potential difference between the collectors of  $T_1$  and  $T_2$ :

$$U_d = \Delta [I_{c(T1)}R_{C1} - I_{c(T2)}R_{C2}]$$

If the collector resistors  $R_C$  are equal in both branches,  $U_d = 0$  if  $I_{c(T1)}$  equals  $I_{c(T2)}$ . Also, assuming that  $T_1$  and  $T_2$  are perfectly matched, i.e., identical, equal collector currents result in equal threshold voltages  $U_{be(T1)}$  and  $U_{be(T2)}$ . From this it follows that the output voltage,  $U_d$ , can only become zero if the input voltage,  $U_i$ , equal to

$$U_{be(T1)} - U_{be(T2)}$$

is also zero. In practice,  $T_1$  and  $T_2$  are never identical, so that the threshold voltages at  $I_{c(T1)} = I_{c(T2)}$  are always (slightly) different. Hence,  $U_i$  must be made equal to the off-set voltage to achieve  $U_d = 0$  V.

In most opamp circuits, the output voltage is made zero by applying the required bias voltage to the input terminals. Some opamps, however, have separate terminals that provide access to internal components. This allows an external trimmer potentiometer to compensate the off-set

voltage without the need of a zero-adjust circuit at the sensitive inputs of the opamp. The principle is illustrated in the circuit diagram in Fig. 3.

The designers of the OP07 have gone a little further, however, as shown in Fig. 4: the collector resistor consists of a number of series-connected individual resistors, of which two have a zener diode in parallel. In the production process, the off-set voltage is reduced to the minimum value immediately after the chip is ready. Accurately controlled current pulses are applied to blow ('zap') one or more zener diodes, which then turn into shorting wires.

This automatic 'zener-zap' process allows off-set voltages to be reduced to  $50 \mu V$  (typical). In some cases, provision is made to compensate even that level with the aid of an external trimmer preset, which is usually included in a resistive bridge circuit. This arrangement is used because the temperature co-efficients of the components in the bridge have a much smaller effect than those in the circuit in Fig. 3.

All these goodies may lead you to start replacing all 741s by OP07s just like that. Remember, however, that the resultant improvement in the circuit performance, if at all required, does not come cheap: the OP07 is about 10 times as expensive as the 741.

## Input bias current

At room temperature, bipolar transistors have a much higher input bias current than JFETs (junction FETs), although this current is virtually temperature-independent. The input bias current of BiFET opamps roughly doubles for every ten de-

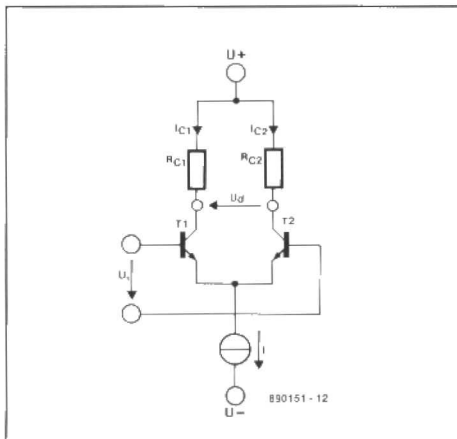


Fig. 2. Standard bipolar opamp input.

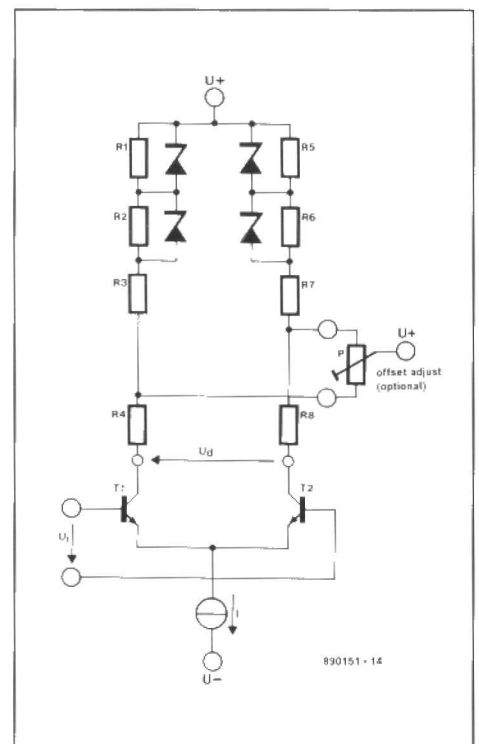



Fig. 4. Basic structure of OP07 input with zener-zap collector resistors.



degrees of temperature rise. In general, the input bias current (at normal operating temperatures) of a commonly used BiFET opamp such as the TL074 is often higher than that of a good bipolar type. This should not be taken to mean that BiFET opamps do not have advantages over bipolar types, since they offer much higher slew rate values in many cases. The BiFET Type OP16, for instance, has a slew rate of 25 V/ $\mu$ s, which makes the device about 75 times faster than the OP07 and the 741.

BiMOS opamps such as the Type CA3140 have MOSFET inputs and a bipolar output circuit. Their input bias current is strongly temperature-dependent owing to the presence of integrated input protection diodes.

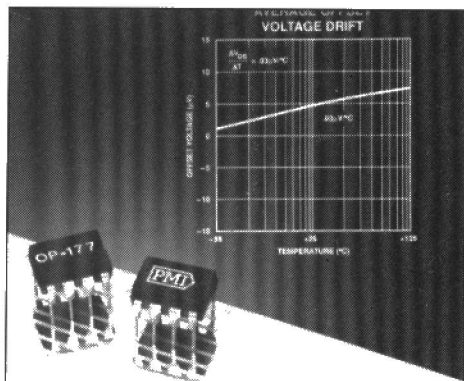The use of current mirrors in the OP07 has resulted in a drastic reduction of the input bias current with respect to the 741: designers should allow for about 50 nA for the OP07 compared with 500 nA for the 741.



## Opamp selection

Summarizing the above, the choice of an opamp is governed by the type of circuit it is used in. Broadly speaking, there are five application areas for opamps:

- general purpose
- low-power
- micro-power
- high-speed
- high accuracy

Each of these applications requires a particular type of opamp for optimum performance. Each opamp family, in turn, has members that are tailored to give optimum performance in one respect only.

The overview in Table 1 may prove useful as a first guide to opamp selection. The right-hand column gives the best-known types in a particular series.

### Reference:

1. LinCMOS circuits. *Elektor Electronics* July/August 1989, p. 20 ff.

### Application area

general-purpose

low-power

micro-power

high speed

high accuracy

### Primary characteristics

low-cost

low supply current ( $I < 1$  mA)

very low supply current ( $I < 100$   $\mu$ A)

high gain-bandwidth

low input off-set; high DC gain;  
high CMRR

### Opamp type

LM741; OP02

(=741 upgrade)

TLC271; OP21

TLC271; OP20

LF356; CA3140;

OP15; OP16

OP07; OP77;

OP27 (low-noise)

### ELECTRICAL CHARACTERISTICS at $V_S = \pm 15$ V, $T_A = +25^\circ$ C, unless otherwise noted.

PARAMETER	SYMBOL	CONDITIONS	OP-177A			OP-177B			UNITS
			MIN	TYP	MAX	MIN	TYP	MAX	
Input Offset Voltage	$V_{OS}$		-	4	10	-	0	25	$\mu$ V
Long-Term Input Offset Voltage Stability	$\Delta V_{OS}/T$ Me	(Note 1)	-	0.2	-	-	0.2	-	$\mu$ V/Me
Input Offset Current	$I_{OS}$		-	0.3	1.0	-	0.3	1.5	nA
Input Bias Current	$I_B$		-0.2	-	1.5	0.2	-	2.0	nA
Input Noise Voltage	$e_n$	$f = 1$ Hz to 100 Hz (Note 2)	-	118	150	-	118	150	nV <sub>RMS</sub>
Input Noise Current	$i_n$	$f = 1$ Hz to 100 Hz (Note 2)	-	3	8	-	3	8	pA <sub>RMS</sub>
Input Resistance Differential-Mode	$R_{IN}$	(Note 3)	26	45	-	26	45	-	M $\Omega$
Input Resistance Common-Mode	$R_{INCM}$		-	200	-	-	200	-	G $\Omega$
Input Voltage Range	IVR	(Note 4)	113	114	-	113	114	-	V
Common-Mode Rejection Ratio	CMRR	$V_{CM} = \pm 13$ V	130	140	-	130	140	-	dB
Power Supply Rejection Ratio	PSRR	$V_S = \pm 3$ V to $\pm 18$ V	120	125	-	115	125	-	dB
Large-Signal Voltage Gain	$A_{VO}$	$R_L \geq 2$ k $\Omega$ , $V_O = \pm 10$ V (Note 5)	5000	12000	-	5000	12000	-	V/mV
Output Voltage Swing	$V_O$	$R_L \geq 10$ k $\Omega$	-13.5	-114.0	-	-13.5	-114.0	-	V
		$R_L \geq 2$ k $\Omega$	-12.5	-113.0	-	-12.5	-113.0	-	
		$R_L \geq 1$ k $\Omega$	-12.0	-112.5	-	-12.0	-112.5	-	
Slew Rate	SR	$R_L \geq 2$ k $\Omega$ (Note 2)	0.1	0.3	-	0.1	0.3	-	V/ $\mu$ s
Closed-Loop Bandwidth	BW	$A_{VC} = +1$ (Note 2)	0.4	0.6	-	0.4	0.6	-	MHz
Open-Loop Output Resistance	$R_O$		-	60	-	-	60	-	$\Omega$
Power Consumption	$P_d$	$V_S = \pm 15$ V, No Load	-	50	60	-	50	60	mW
		$V_S = \pm 3$ V, No Load	-	3.5	4.5	-	3.5	4.5	
Supply Current	$I_{SY}$	$V_S = \pm 15$ V, No Load	-	1.6	2.0	-	1.6	2.0	mA
Offset Adjustment Range		$R_p = 20$ k $\Omega$	-	13	-	-	13	-	mV

#### NOTES:

1. Long-Term Input Offset Voltage Stability refers to the averaged trend line of  $V_{OS}$  vs. Time over extended periods after the first 30 days of operation. Excluding the initial hour of operation, changes in  $V_{OS}$  during the first 30 operating days are typically less than 2  $\mu$ V.

2. Sample tested

3. Guaranteed by design

4. Guaranteed by CMRR test condition

5. To insure high open-loop gain throughout the  $\pm 10$  V output range,  $A_{VO}$  is tested at  $-10$  V  $\leq V_O \leq 0$  V,  $0$  V  $\leq V_O \leq 10$  V, and  $-10$  V  $\leq V_O \leq -10$  V.


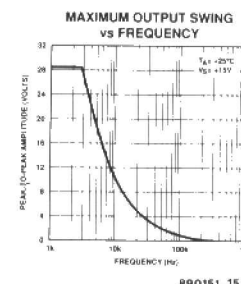
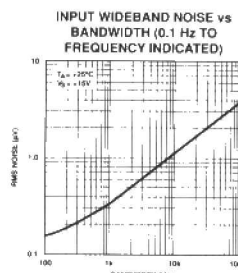
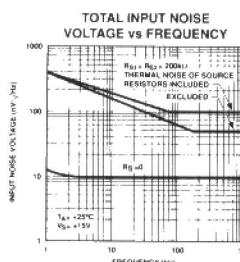
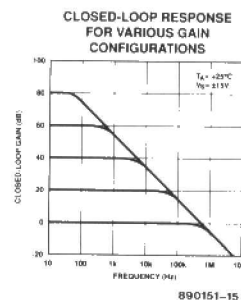
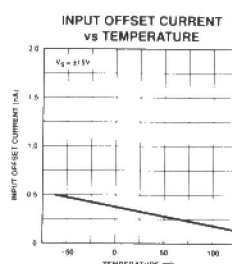
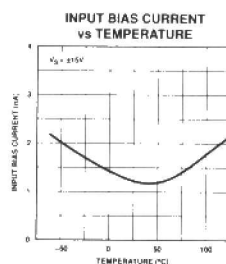


Fig. 5. Introducing the OP177 ultra-precision opamp (illustrations courtesy Precision Monolithics Inc.)

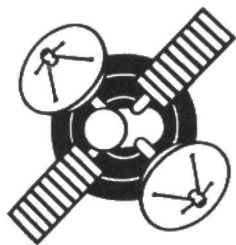

# SAVE DECODER

## Part 1: Operation and technical background

P.N.P. Wintergreen

**The scrambling system employed for the BBC-TV Europe and the now defunct Premiere channel on the Intelsat-VF11 TV satellite is generally classified as a low-level video encoding scheme. Based on controlled interference in the video spectrum it is, however, not so simple to defeat with traditional filter designs that have already caused much hair-pulling and teeth-gnashing among technically inclined dish owners. The decoder discussed here leaves traditional filters for what they are, yet offers a perfectly decoded picture at a cost of £25 or so.**

The Intelsat-VF11 TV satellite is positioned in geostationary orbit at 27.5° west, and can be received in large parts of western Europe if a dish of 1.2 m or larger is used. The BBC-TV Europe programme is transmitted at 10.987 GHz with vertical polarization. The channel is encoded according to the SAVE (*sound and vision encryption*) system, with occasional changes in the interference frequency used.

### Tackling SAVE

The SAVE scrambling system looks relatively simple at first glance, because the encoding is effected entirely in the frequency domain. This is in contrast to many other analogue encoding systems, which use signal inversion in combination with amplitude-shifting and frame and/or line polarity control (Ref. 1).

In the SAVE system, the video signal from the TV studio has its amplitude reduced by 50% before it is inverted. The original amplitude is then restored by the addition of a pure sine-wave with a frequency of about 94 kHz. This encoding scheme has prompted many technically inclined dish owners to design and build a wide variety of filters, only to find that the interfering signal is much harder to get rid of than expected. This is mainly because any residual interfering signal, however small, gives an irritating effect on the TV screen. As found out the hard way, the 94 kHz notch is simply not capable of ensuring a perfectly stable picture.

Without a suitable decoder, a SAVE-encoded video signal produces a totally unintelligible picture. In principle, the signal becomes at least visible by invert-

ing it and doubling the amplitude. Although these measures result in a picture that can be recognized on many TV sets, the quality is very poor owing to the interfering carrier that is still present at its full


level. The suppression, in particular, of the interference poses considerable problems if conventional filter techniques are used.

The phase and amplitude recovery of the 94 kHz interference signal is affected by the video signal, and designers must take into account that this can have an infinite number of instantaneous amplitude-frequency configurations because the spectrum is a function of the current picture content, which changes in real-time.

A narrow 94 kHz filter, however, will give reasonable results in many cases. A crystal filter as used in communications receivers is

ideal for this function. Unfortunately, crystal filters are notoriously expensive and hard to obtain, especially for a non-standard frequency like 94 kHz. These problems may be resolved, however, by a compensation circuit with a PLL (*phase-locked loop*), and a VXO (*variable crystal oscillator*) that functions as a VCO (*voltage controlled oscillator*). An advantage of this arrangement is that it can be designed to operate at a multiple of 94 kHz.

The block diagram of Fig. 1 shows the basic structure of a VXO-PLL (Ref. 2). Although not used for the present design, the principle merits a short discussion. The crystal is cut to order for one particular interference frequency around 94 kHz. In practice, however, the interference frequency is changed on an irregular basis, so that a number of crystals are required when BBC-TV Europe is to be decoded. Clearly, this is a relatively expensive solution since the station operators can change the interference frequency within a certain range, requiring new crystals to be cut. The present decoder is much more

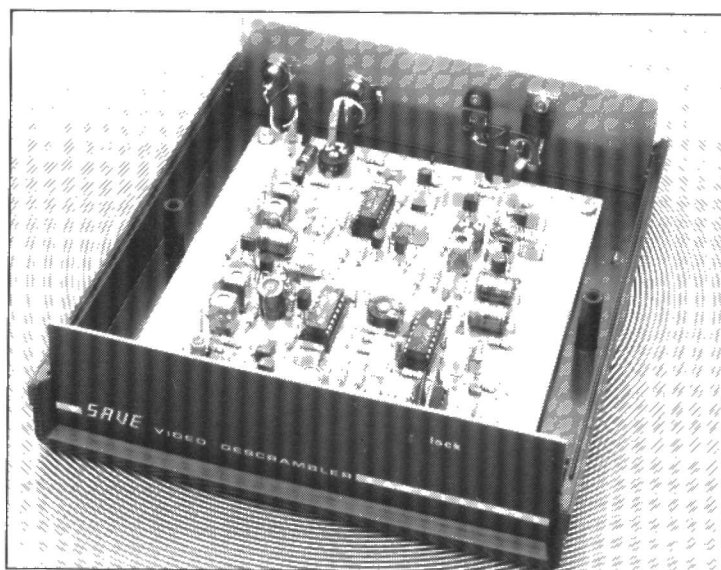

### SAVE DECODER

- low-cost design; no cut-to-order quartz crystal(s)
- complete suppression of SAVE interference
- L-C oscillator with amplitude and phase control loops for optimum stability
- simple-to-connect to any indoor unit
- standard clamped video output: 1 V<sub>pp</sub>/75 Ω
- automatic switch-over between non-encoded and SAVE-encoded channels
- automatic search for interference frequency within 1.5 kHz band




flexible in respect of frequency control because it is based on an *L-C* oscillator that uses inexpensive components, and works at 94 kHz. A number of special techniques, combined with 'all-analogue' signal processing have resulted in a stop-band filter (*notch*) whose performance in respect of selectivity comes close to that of a crystal filter.

The low-cost decoder presented here features automatic processing of any SAVE-encoded video signal that contains an interfering carrier between about 93 kHz and 94.5 kHz, so that BBC-TV Europe ( $f_i=93,275$  Hz) is reliably recognized and decoded, irrespective of the current interference frequency.

## Spectral analysis

The frequency spectra of Fig. 2 illustrate the basic operation of *pre-* and *de-emphasis* techniques used in the present decoder. The spectrum of Fig. 2a shows the typical amplitude distribution, within the frequency range from 0 to 500 kHz, of a video signal. It should be noted that the drawing is purposely simplified: the spectrum applies to a completely black picture, while the effect of the raster synchronization pulses is not shown. The simplified spectrum with line sync components and the interference signal is, however, still useful for a basic analysis.

The frequency range between 90 and 95 kHz is shown enlarged in the lower spectrum of Fig. 2a. Clearly, the interference carriers are quite close to the sixth harmonic of the line frequency. The frequency differences are small — only 475 Hz in the case of BBC-TV Europe, and

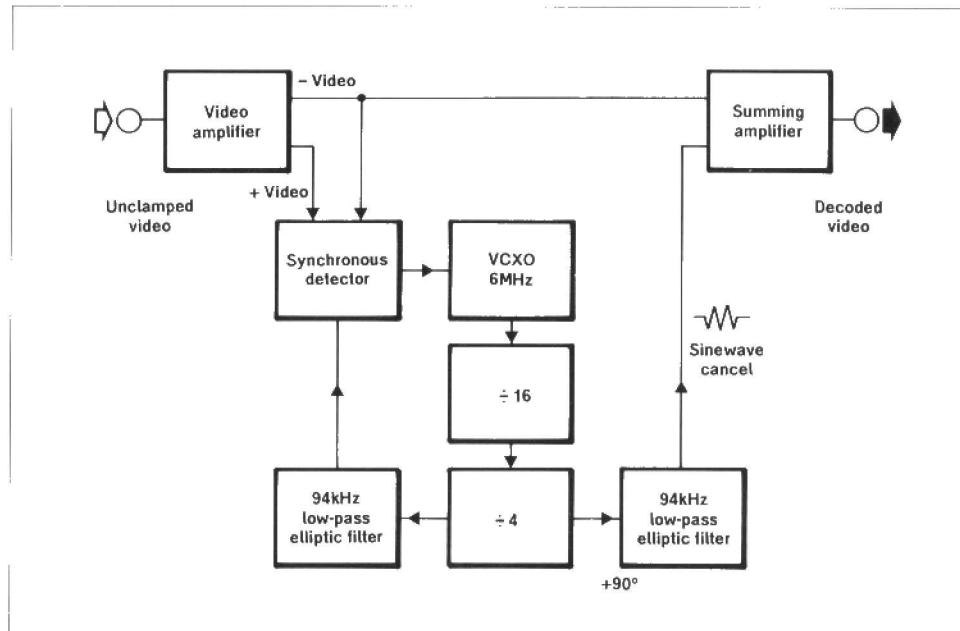


**Fig. 1.** The first approach to a SAVE decoder is nearly always a VCXO design. The inherent disadvantages are, however, relatively high cost and the 'one channel, one crystal' rule (source: Ref. 2).

575 Hz in the case of Premiere — and make selective suppression of the interference frequency fairly difficult because the phase and amplitude of the sixth harmonic of the line sync must be left completely unaffected. If this condition is not met, the picture is visibly distorted. Hence, a simple notch is unsuitable for building a reliable SAVE-decoder.

For those less familiar with video techniques, it may come as a surprise that the interference signal must be amplified before it can be suppressed. Pre- and de-emphasis are used to achieve this. These

techniques are applied in FM communications systems to improve the signal-to-noise ratio. At the transmitter side, a certain part of the frequency spectrum of the modulation signal is given a greater amplitude, which is reduced again in the receiver by a matched filter to restore the original signal level. Ideally, the frequency response between the input of the transmitter and the output of the receiver is flat because the pre- and de-emphasis filters are closely matched by means of complementary curves.

A two-section *L-C* filter in the present

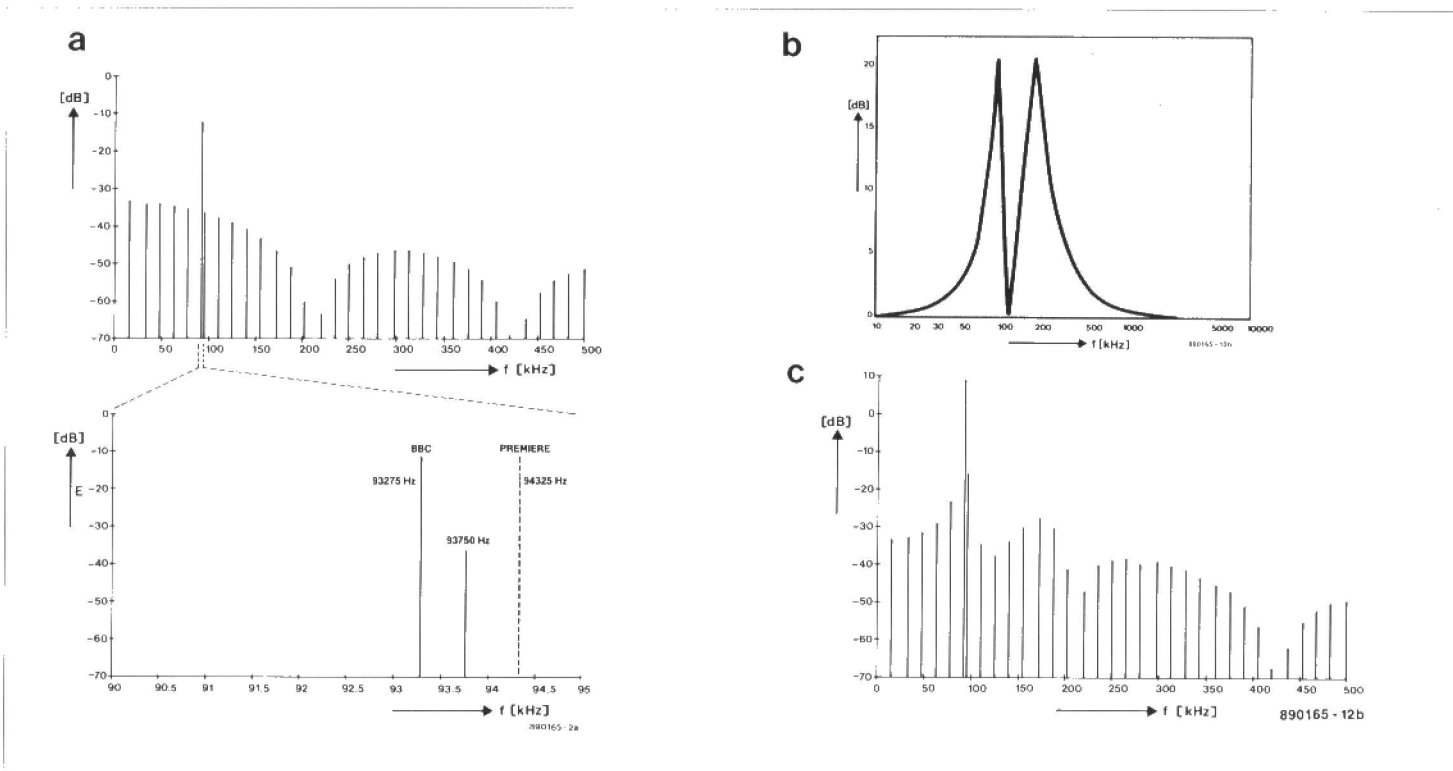

**Fig. 2.** Frequency spectrum of a SAVE-encoded video signal with no picture content (2a); theoretical pass-band of the pre-emphasis filter (2b); and the result of the pre-emphasis operation on the original spectrum (2c). It should be noted that the spectra shown are theoretical and purposely simplified.

SAVE decoder raises frequency components around 94 kHz and 188 kHz about 20 dB with respect to the rest of the video spectrum. The theoretical pass-band curve of this filter is shown in Fig. 2b, and its effect on the spectrum of Fig. 2a is apparent from Fig. 2c. The interference signal has the highest amplitude in the latter spectrum.

The control principle adopted for the SAVE decoder requires the second pass-band at 188 kHz. The analogue control circuit that is to supply the regenerated 94 kHz signal does not have filters to ensure a well-defined phase response, and multiplication of the 94 kHz signal inevitably produces a 188 kHz component. Owing to cross-talk, a part of this component ends up in the video signal, where it produces interference. This is prevented, however, with the aid of a de-emphasis filter, of which one section is tuned to 188 kHz.

Since the interference frequency is always an odd multiple of the interlace frequency (25 Hz), residual levels of the 94 kHz signal that remain after decoding are virtually unnoticed owing to the optical averaging function of the human eye.

After removal of the 94 kHz component, the signal amplitude must be restored to the level before pre-emphasis. This is achieved with a de-emphasis filter whose pass-band curve is accurately dimensioned to form the inverse of the pre-emphasis curve.

### Block diagram

The basic operation of the SAVE decoder is best described along the lines of the block diagram shown in Fig. 3.

The heart of the circuit is formed by an *L-C* oscillator, which is controlled by loop circuits for amplitude and phase. In principle, the regenerated 94 kHz sine-wave is added to the scrambled video signal. The amplitude of the regenerated sine-wave is identical to that of the interference component, but the phase is opposite. This is achieved with the aid of a control circuit that is capable of continuously monitoring, and, if necessary, correcting, the phase and the amplitude of the regenerated 94 kHz signal. The oscillator used is a voltage-controlled Colpitts type based on an *L-C* tuned circuit with a relatively high *Q*-factor. In combination with a double loop filter that forms part of a PLL, it ensures good phase stability of the regenerated sine-wave when the circuit is locked.

The block diagram shows that the unclamped video signal supplied by the satellite-TV receiver is amplified before it is passed through the pre-emphasis filter discussed above. The output signal of the two-stage  $L$ - $C$  filter is compared to that of the 94 kHz oscillator. The phase comparator is an analogue multiplier available in IC Type XR2208 from Exar. The result of the multiplication operation is a difference frequency that is fed to the first loop filter. This filter is realized with the

ELEKTOR ELECTRONICS FEBRUARY 1990

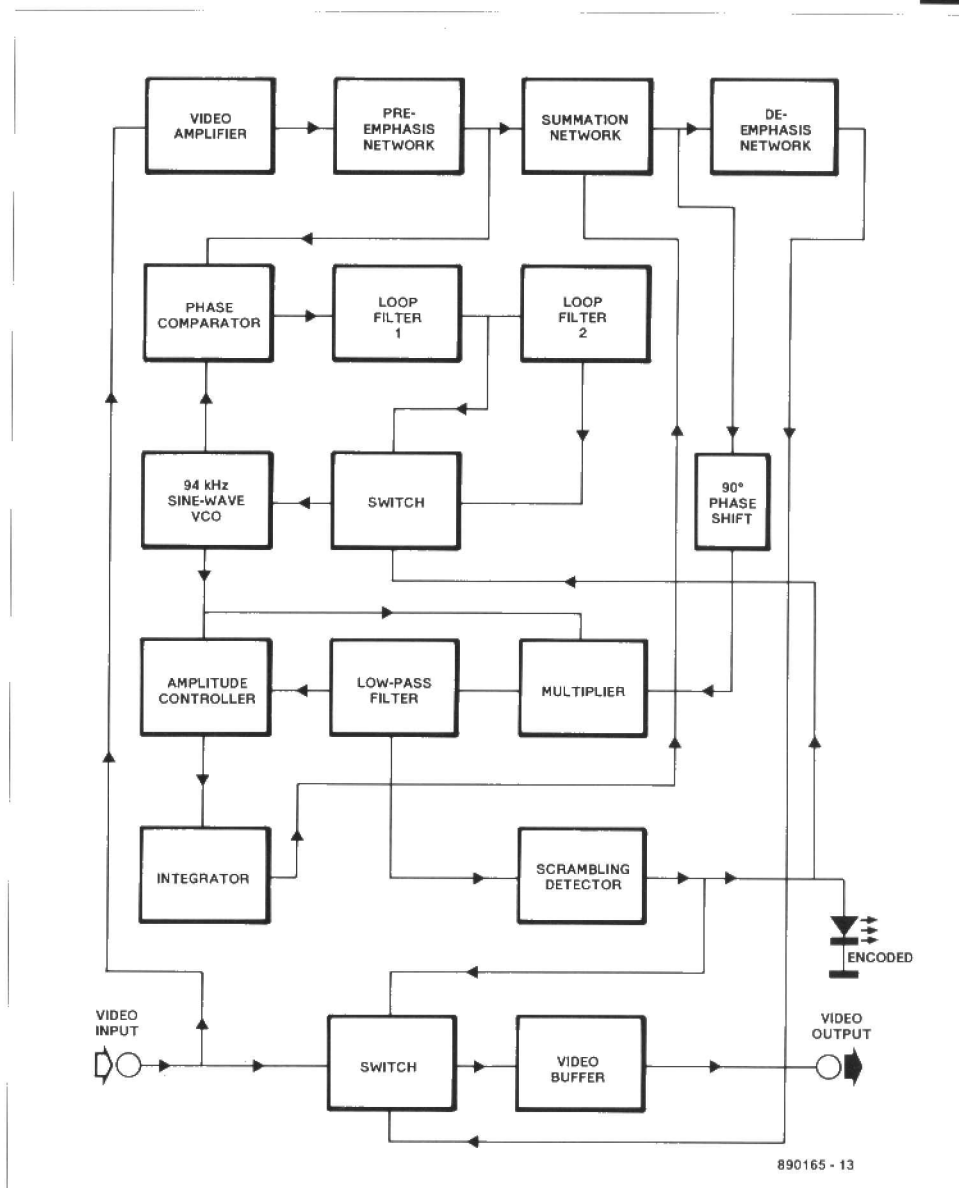


Fig. 3. The block diagram of the SAVE decoder is fairly complex. The operation of the circuit is based on a 94 kHz *L-C* VCO surrounded by control loops for amplitude and phase.

opamp available in the XR2208. When the circuit is not locked, the first loop filter is given a bandwidth of a few hundred Hz to enable the PLL to lock on to sufficiently strong signals in a frequency band of about 1.5 kHz around 94 kHz. The PLL does not lock on to signals below a certain threshold level, so that, for instance, the sixth harmonic of the line frequency can not switch the circuit to the decoding mode. Without special measures, however, the sixth harmonic of the line frequency is likely to cause problems once the PLL has locked on to, say, the SAVE-encoded BBC-TV Europe signal. In that condition, the phase comparator supplies 475 Hz, the frequency difference between the sixth harmonic and the interference signal. Without a correctly dimensioned loop filter, this difference frequency gives rise to phase modulation of the VCO, which, in turn, leads to incomplete compensation of the interference. The result is an annoying interference on the TV screen.

The solution to this problem has been found in automatic bandwidth reduction of the loop filter. After the PLL has locked,

the loop filter is given a pass-band of about 15 Hz rather than a few hundred Hz. This arrangement requires high VCO stability, however, since frequency deviations can only be corrected relatively slowly. Fortunately, the  $L$ - $C$  oscillator used meets this requirement, so that a phase-locked reference signal is obtained. What remains is control of the amplitude, and a shift of phase by  $90^\circ$ . Both functions are realized by an operational transconductance amplifier (OTA), a Type LM13700 from National Semiconductor. A useful background on OTAs can be found in Ref. 3.

The VCO reference signal is passed through an amplitude control circuit and an integrator before it is added to the input signal after pre-emphasis. The result of the addition is phase-shifted by  $90^\circ$  and fed to a multiplier that determines the frequency difference between its input signals. Evidently, the difference is 0 Hz only when the VCO frequency equals the interference frequency. As shown in the 'Theoretical background' inset, complete compensation is achieved when the amplitude of the 94 kHz VCO signal equals



the amplitude of the interference signal. The control loop performs automatic corrections to the amplitude of the VCO signal until a stable condition is reached. Once aligned, the decoder is, therefore, insensitive to small amplitude variations of the input signal, and other forms of instability.

The integrator that shifts the phase of the VCO signal by 90° gives a frequency-independent phase shift, and is located after the amplitude control circuit. An additional benefit of the integrator is its ability to suppress harmonics generated by light distortion. These harmonics are suppressed at 6 dB per octave.

The control voltage for the amplitude controller is used to light a LED that indicates the decoding of a SAVE signal. When the LED lights, the loop filter is automatically switched to reduced band-

width, and the output signal of the de-emphasis network is fed to the video buffer with associated clamping circuit. The decoded video signal has an amplitude of about 1 V<sub>pp</sub> at a load impedance of 75 Ω, and is suitable for direct connection to a monitor or remodulator.

## From theory to practice

The previously discussed functions are easily found back in the circuit diagram of Fig. 4. The unclamped video signal from the satellite-TV receiver must have an amplitude of at least 0.5 V<sub>pp</sub>. Components P1, C1, R3 and ES1 take the non-encoded video signal to amplifier T5. From there, it is passed through clamping circuit D1-D2-T6 before it is applied to output buffer T7. The output amplitude is set to 1 V<sub>pp</sub> into 75 Ω with the aid of preset P1.

The pre-emphasis L-C filter in the collector line of T1 supplies a video signal with a 94 kHz component of about 3 V<sub>pp</sub> when the receiver is tuned to a SAVE-encoded TV channel. The transistor works as an inverting amplifier. Capacitor C7 feeds the signal with the 94 kHz component to the phase comparator in IC3, where it is multiplied with the VCO signal applied via C18.

### Phase control

The 94 kHz Colpitts VCO built around FET T8 is tuned by means of a direct voltage applied to dual variable capacitance diode D7. The circuit around D6 and T9 is an amplitude stabilizer. When the amplitude of the oscillator signal exceeds a certain level, T9 conducts via D6, and draws current through R44. This causes the drain current of the oscillator FET to drop to a level at which the feedback gain in the

## Theoretical background

### 1. Pre- and de-emphasis

Current source T1 uses pre-emphasis impedance Z formed by L1-L2-C4-C5-R6 to generate a signal voltage at TP1:

$$U_{B(T1)} = U_i$$

$$U_{E(T1)} = U_i$$

$$I_{Q(T1)} = -I_{E(T1)} = -U_i / R_5$$

$$U_{TP1} = I_{Q(T1)} (Z + R_7) = -U_i (Z + R_7) / R_5$$

Since T3 offers high current amplification, Z is hardly loaded.

The regenerated 94 kHz sine-wave is added in anti-phase to the video signal. Emitter follower T4 forms a virtually ideal voltage source for the de-emphasis impedance, Z:

$$U_{B(T4)} = U_{E(T4)} = -U_i (Z + R_7) / R_5 + u_p \sin(\omega t + \varphi)$$

where

$$\omega = 2\pi 94000 \text{ [rad/s]}$$

The decoded video signal across R15 may be written as

$$U_{R15} = U_o$$

$$U_o = R_{15} / (R_{15} + Z) U_{E(T4)}$$

$$U_o = \frac{R_{15}}{(R_{15} + Z)} \left[ -U_i \frac{(Z + R_7)}{R_5} + u_p \sin(\omega t + \varphi) \right]$$

The input voltage,  $U_i$ , may be written as

$$U_i = U_{video} + u_p \sin(\omega t + \varphi).$$

Owing to noise in the input signal, the residual 94 kHz component,  $U_{res}$ , has to be taken into account:

$$U_o = R_{15} / (R_{15} + Z) (-U_{video} (Z + R_7) / R_5 + U_{res})$$

$$U_o = -U_{video} \frac{R_{15} (Z + R_7)}{R_5 (Z + R_{15})} + \frac{R_{15}}{Z + R_{15}} U_{res}$$

With  $R_7 = R_{15}$ :

$$U_o = -R_{15} / R_5 U_{video} + R_{15} / (Z + R_{15}) U_{res}$$

$$U_o = -1.23 U_{video} + R_{15} / (Z + R_{15}) U_{res}$$

When pre-emphasis network L4-C9 (Z) resonates at 94 kHz, it forms a very high impedance. R13 alone then determines the impedance of Z. With  $R_{13} = 2700\Omega$ :

$$U_o = -1.23 U_{video} + 0.09 U_{res}$$

Correctly aligned, the pre- and de-emphasis networks yield more than 20 dB suppression of the 94 kHz component, without distorting the video signal.

### 2. Amplitude control circuit

The frequency of the amplitude control voltage,  $U_{reg}$ , is 0 Hz if the regenerated frequency equals the frequency of the interference voltage,  $U_i$ :

$$U_{reg} = \int_0^\infty \sin(\omega t) [ (U_i - U_{reg}) \sin(\omega t) ] dt$$

$$U_{reg} = \int_0^\infty 0.5 (U_i - U_{reg}) [1 - \cos(2\omega t)] dt$$

The integrator gives virtually complete suppression of the 188 kHz component, so that:

$$U_{reg} = \int_0^\infty 0.5 (U_i - U_{reg}) dt$$

This equation can be solved if  $U_i = U_{reg}$ , which corresponds to complete compensation.

### 3. 90° phase shifter

Pin 5 of OTA1 supplies a sinusoidal current,  $I_o$ , which is integrated by C29:

$$I_o = I_p \cos(\omega t)$$

$$U_{C29} = 1 / C \int_0^\infty I_o dt$$

$$U_{C29} = 1 / C \int_0^\infty I_p \cos(\omega t) dt$$

$$U_{C29} = \frac{I_p}{\omega C} \sin(\omega t)$$

where

$$\omega = 2\pi 94000 \text{ [rad/s]}$$

The phase is shifted 90° independently of frequency.

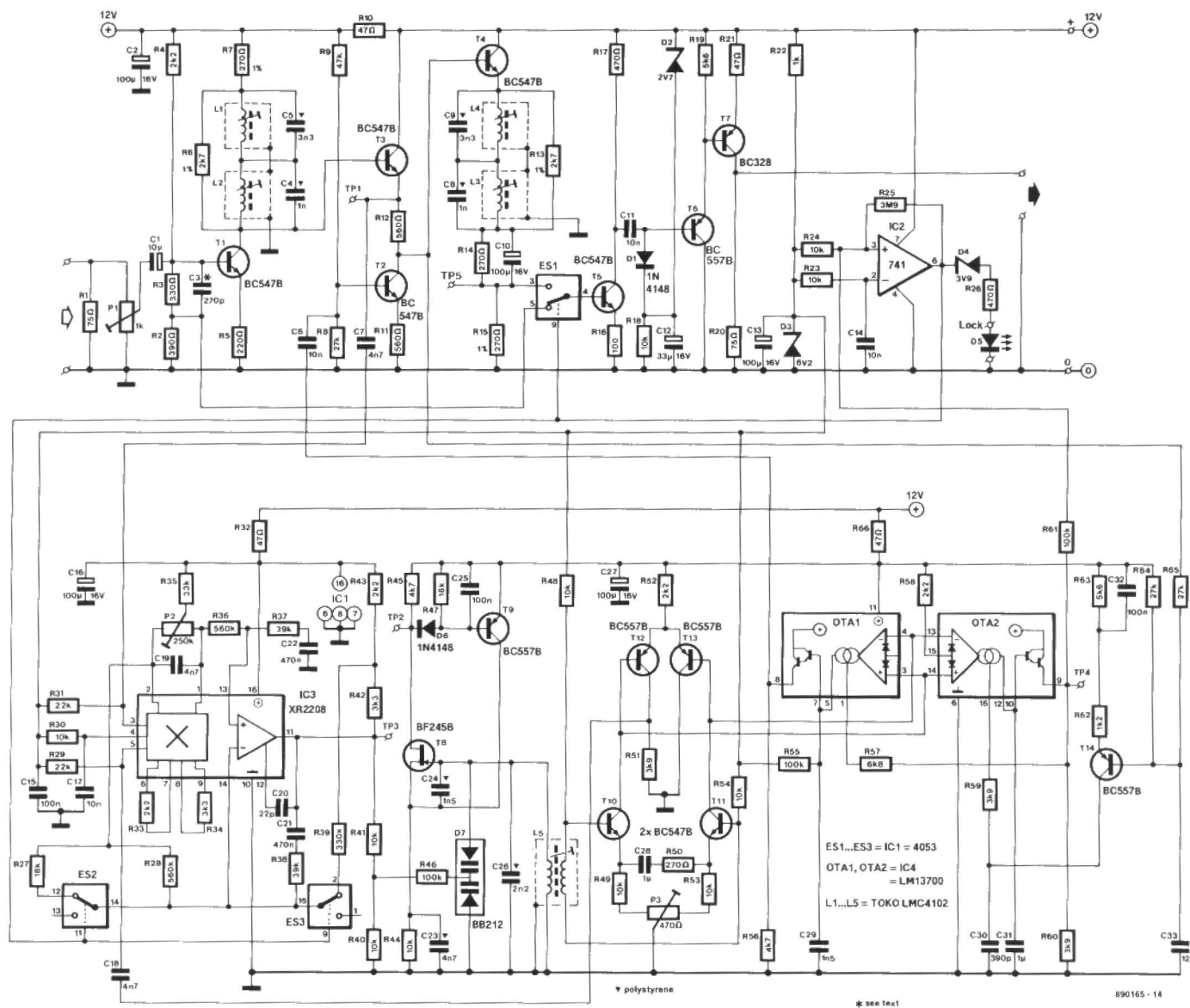


Fig. 4. Circuit diagram of the SAVE decoder.

oscillator is unity. The result is a clean and stable oscillator signal that is coupled out inductively via L5. Transistors T10 and T11 amplify the oscillator signal and convert it into a symmetrical current that is fed to the pair of diodes at each of the parallel-connected OTA inputs (IC4).

The OTA inputs are also connected to T12 and T13 to form a *gain-cell*. In principle, a gain-cell provides linear conversion of an input signal into an output signal. The gain of the cell is determined by a current supplied by an external source. In the present case, this control current emanates from R52, while the basic gain of the cell is defined by the ratio R52:R58.

The 94 kHz signal is taken asymmetrically from the collector of T12 and fed to the phase comparator via C18. The difference frequency is available as a balanced signal between pins 1 and 2 of the XR2208. The balanced difference signal is passed to the opamp in the XR2208, by means of networks R28-R38-C21 and R36-R37-C22.

Depending on whether the PLL is

locked or not, the bandwidth of the loop filter is changed by ES2 connecting R27 in parallel with R28, and ES3 selecting a different R-C network at the output of the opamp in the XR2208. The control voltage is passed to the varicap via R41 and R46. This closes the phase-locked loop.

#### Amplitude control

The amplitude of the regenerated 94 kHz sine-wave is determined with the aid of a current sent into pin 1 of OTA1. This current is supplied by OTA2, which works as a multiplier. The result is that pin 5 of OTA1 supplies a sinusoidal current to integrator C29. The mathematical deduction in the 'Theoretical background' inset demonstrates that the phase is shifted 90° independently of frequency. The voltage developed across C29 is fed back into the IC via pin 7, and reappears buffered at pin 8. The regenerated, amplitude-controlled and 90° phase-shifted 94 kHz signal is fed to T2 via C6, and from there to summation point T2-R12. This forms the nucleus of the circuit: the interference disappears against its regenerated counter-

part, which has the same amplitude but the opposite phase.

The summation signal is taken through the de-emphasis network in the emitter line of T4. The first of the two L-C sections removes residual 94 kHz levels, and the second ensures sufficient suppression of the 188 kHz component. The decoded signal is fed to the clamping circuit via ES1.

The amplitude control circuit receives its error signal from the summation point, via R65. Components C33, R64, R65, C30 and R59 shift the phase of the error signal by 90° so that it can be used for driving multiplier OTA2. This supplies a current that is integrated by C31. The resulting voltage on this capacitor is buffered by the darlington transistor in the OTA, and serves to supply the control current to the previously mentioned gain cell (OTA1) via R37. This closes the amplitude-controlled loop.

*The construction and alignment of the decoder will be described in Part 2 of this article.*

# DESIGN IDEAS

The contents of this column are based solely on information supplied by the author and do not imply practical experience by *Elektor Electronics*.

## WAVEFORM MODULATION OF THE MAINS VOLTAGE

by A.M. Karailiev

In order to simplify the transmitter and to improve the noise immunity of the remote control receivers described in his earlier article\*, Mr Karailiev here offers another method of modulating and demodulating the mains voltage.

A thyristor, rated at not less than 25 A, is connected directly across the mains supply. It is controlled by a circuit as in Fig. 1 in a manner to make it conductive for a time  $\Delta t$   $\mu$ s at the end of every positive half cycle of the mains voltage.

The programming unit is an integrated circuit Plessey Type SL120, or SGS Type L120, or equivalent.

Assume that the thyristor will short-circuit the mains at the instant this reaches a value of +24 V – see diagram in Fig. 2. Then,

$$u = U_{\max} \sin \omega t = U_{\max} \sin(2\pi t/T)$$

or

$$24 = 310 \times \sin 2\pi \times 50 \Delta t.$$

Since, for a small angle,  $\sin \theta = \theta$ ,

$$24 = 310 \times 2\pi \times 50 \Delta t, \text{ and}$$

$$\Delta t = (24 \times 10^6) / 310 \times 2 \times 50 = 246 \mu\text{s}.$$

Thus, for a period of 246  $\mu$ s, the mains voltage is practically zero and this manifests itself, at minimal power dissipation, in a distortion signal on the mains voltage. It is interesting to note that since the signal is caused by a lack of voltage, it will not be attenuated by the power lines, so that it will be detectable over fairly large distances.

### Type of modulation

The effect of the momentary short circuit of the mains voltage will be a change of its sinusoidal waveform, so that we may

\* "Mains Signalling", *Elektor Electronics*, November 1988, p. 27.

Readers are advised that modulating the mains voltage in the United Kingdom is subject to the provisions of British Standard BS6839. Further information on the subject may be obtained from BIMSA (BEAMA Interactive and Mains Systems Association), Leicester House, 8 Leicester Street, LONDON WC2H 7BN, Telephone 01-437 0678.

speak of waveform modulation. However, as the depth of modulation is defined by the angle  $\theta$  during which the short circuit occurs, or by the time duration of the short circuit, other definitions of the type of modulation may be applied.

### Demodulation

The information on the mains voltage is extracted from it by means of a circuit as shown in Fig. 6. The instantaneous voltage,  $u$ , at the secondary of the input trans-

former, Tr, is

$$u = U_{\max} \sin(2\pi t/T)(T \pm t)$$

and this is represented graphically in Fig. 3.

If the full-wave rectified voltage ( $U_{\max} = 17$  V) is applied to the inverting input of an operational amplifier acting as a zero crossing detector, and a direct voltage of 0.25 V is applied to the non-inverting input, the output of the detector will consist of 93.66  $\mu$ s wide pulses at a pulse rate equal to twice the mains frequency.

When the positive voltage applied to the non-inverting input is higher than the voltage caused by the modulation, the pulse spacing (pulse repetition period) decreases. When, however, the voltage caused by the modulation is higher than that applied to the non-inverting input, the pulse spacing increases – see Fig. 4.

In the absence of modulation, the zero crossing detector should be adjusted to make the width of the output pulses as

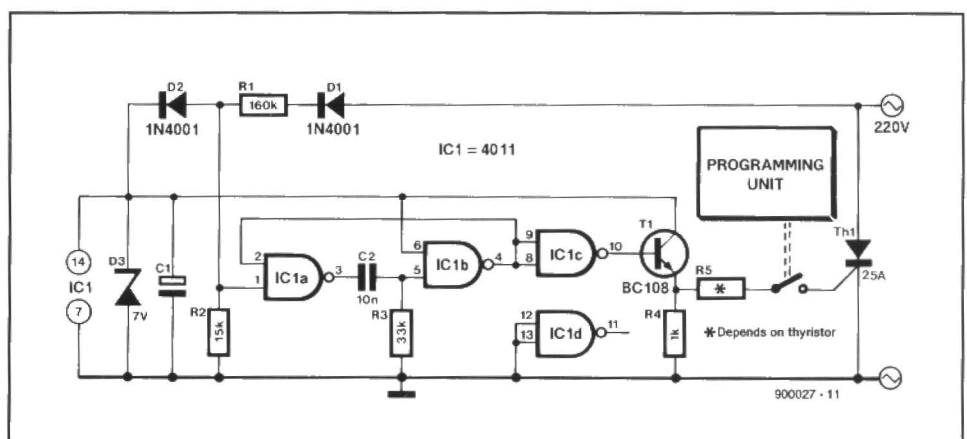


Fig. 1. Basic control circuit for the modulator; the value of R5 depends on the type of thyristor.



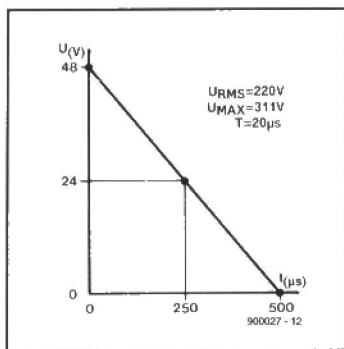


Fig. 2.

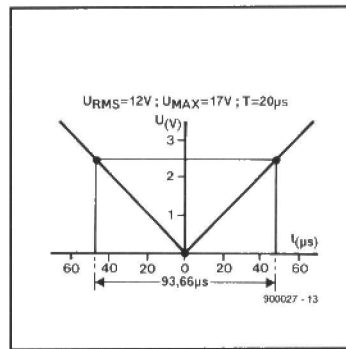


Fig. 3.

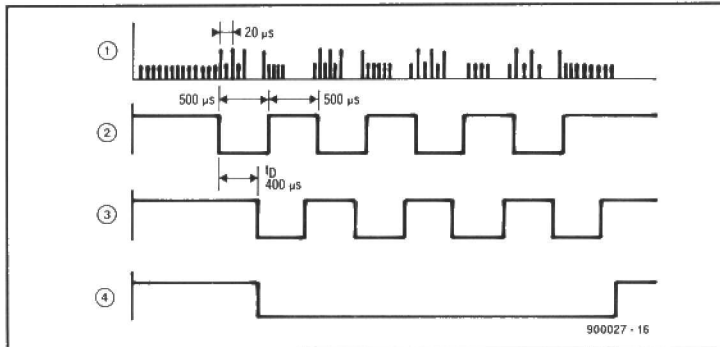


Fig. 5. Pulse diagrams at selected points in the circuit of Fig. 6. The numbers at the left correspond with the circled numbers in Fig. 6.

small as possible. For example, if the detector produces pulses 100  $\mu$ s wide in the absence of modulation, and a modulated signal with a depth of modulation of 250  $\mu$ s is applied, the width of the output pulses will increase to 300  $\mu$ s. If the detector is made more sophisticated, it may produce pulses only when there is modulation

present and no pulses at all in the absence of modulation.

## Receiver

In the circuit of the receiver shown in Fig. 6, T<sub>1</sub> serves as the zero crossing detector. It should preferably be a germa-

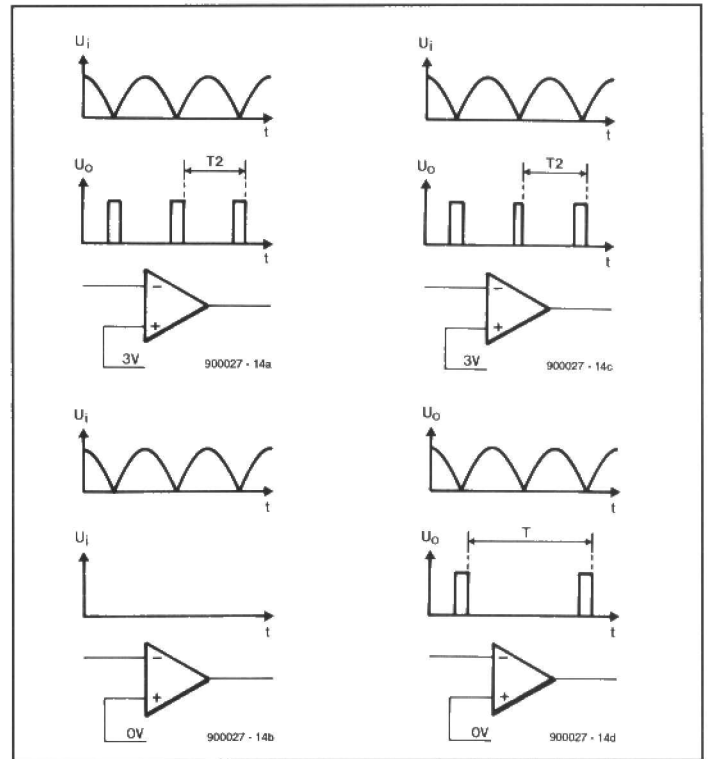


Fig. 4. In diagrams a and b there is no modulation; in diagrams c and d, modulation is present.

nium type to ensure minimum-width pulses in the absence of modulation.

Network R<sub>3</sub>-R<sub>4</sub>-C<sub>3</sub> forms a charge/discharge circuit that converts the pulse-width modulation into pulse-amplitude modulation. The pulse height can be adjusted by R<sub>3</sub>, so that monostable IC<sub>1</sub> may be triggered only by pulses above a certain height.

The monostable is retriggerable and produces a long output pulse at its pin 12 when there is modulation present. Here, the length of the pulses is predetermined at 500  $\mu$ s. Shorter pulses will be suppressed by a noise protection circuit consisting of R<sub>6</sub>-R<sub>7</sub>-C<sub>6</sub> and the two Schmitt triggers contained in IC<sub>3</sub>.

The output pulses of IC<sub>1</sub> are counted by IC<sub>4</sub>. When the pulse train ceases, retriggerable monostable IC<sub>2</sub> emits a pulse that is applied to the clock input of D-type bistable IC<sub>5</sub>. This causes the contents of one stage of the counter to be transferred to IC<sub>5</sub>, which acts as a latch. Since IC<sub>4</sub> is a four-stage counter, it is thus possible to control four different devices or machines.

Diagrams of the pulses at selected parts of the circuit are shown in Fig. 5.

The higher noise immunity of the receiver as compared with that in my earlier article is obtained because:

1. its input is open to the signal and closed to noise, since the thyristor short-circuits all noise;
2. of the noise protection circuit;
3. of the special form of the signal (absence of voltage).

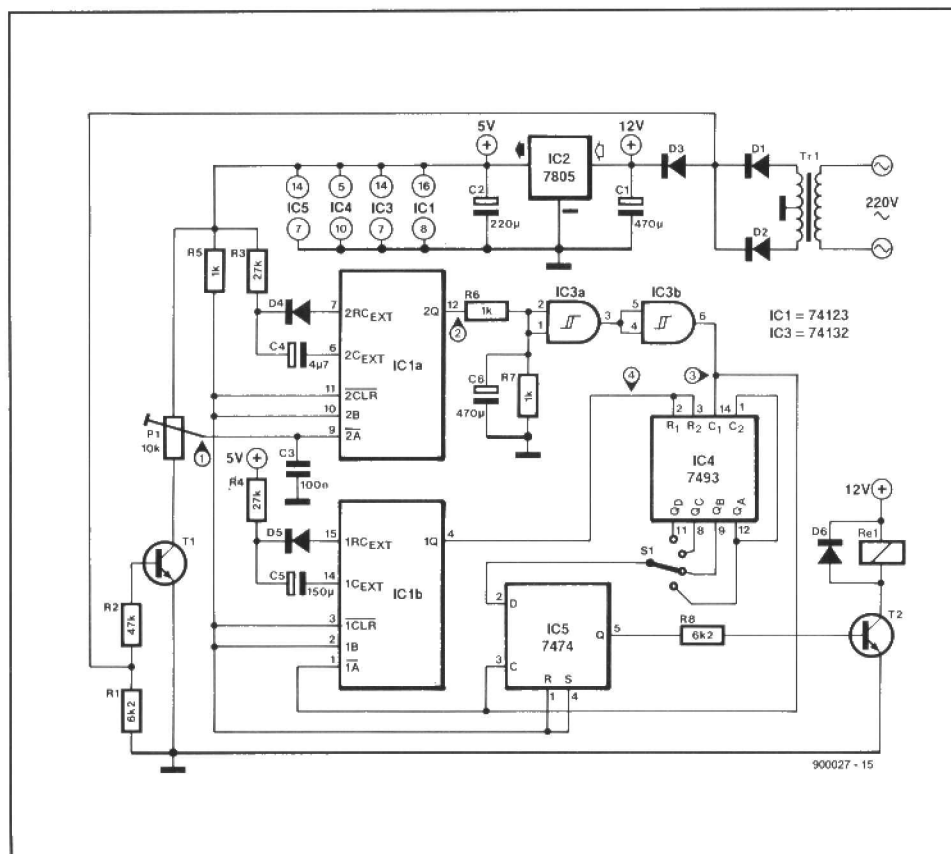


Fig. 6. Circuit diagram of the proposed receiver.

# FEEDBACK KILLER

T. Giffard

**This circuit helps to prevent feedback in public address (PA) systems. Feedback occurs at relatively high volume settings when a microphone is held too close to a loudspeaker. The effect is characterized by whistling or howling sounds that are annoying to the audience, the sound engineer and, of course, the speaker on the stage.**

Feedback is a constant source of worry to mixing desk operators in the backstage line, since the now shrill then howling sounds always seem to occur unexpectedly, and tend to irritate both the performers on the stage and the audience, who respond with boos, catcalls and plugging of ears. No good this equipment!

At a certain frequency, or frequencies, the phase shift in the closed loop formed by the microphone, the amplifier, the loudspeaker and the listening room is 0 degrees, 360 degrees or a multiple thereof. If, in this situation, the amplifier gain is greater than the room attenuation, the feedback signal rises to a level at which it tops all other sound. This is the well-known high-pitch whistle: the PA system oscillates.

Figure 1 illustrates what happens. The sound produced by the loudspeakers is reflected by the room or by objects or persons in the room, and is subsequently picked up by the microphone. The phase shift and attenuation depend on the acoustic parameters of the listening room (note that the audience forms a moving part of the room and must be taken into account as regards the loudspeaker positions).

Evidently, the best way to prevent feedback is to place the microphones in positions where they are unlikely to pick up reflections from the loudspeakers.


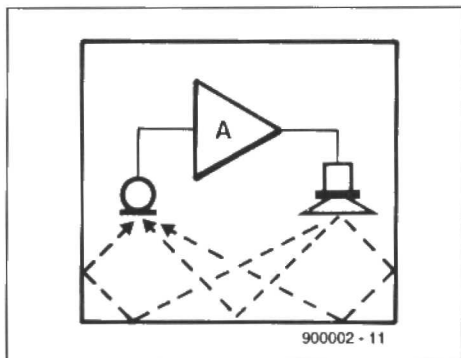


Fig. 1. Sound reflections.

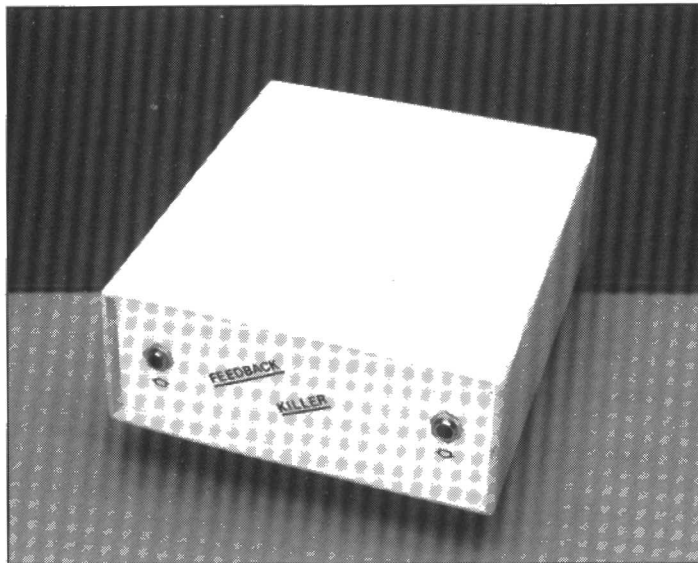

to mean that it makes feedback impossible: only the point at which the effect starts is shifted to a much higher level.

The risk of feedback occurring is reduced by creating a small frequency difference of 1 Hz to 30 Hz between the amplifier input- and output-signal. This operation causes the frequency of a (potential) feedback signal to be raised a little so that the condition for oscillation is no longer satisfied.

## Block diagram

A number of modulation techniques may be applied to obtain a fixed frequency shift between an amplifier input- and output-signal. In practice, virtually all these techniques make use of amplifiers, filters and mixers.

The block diagram of the feedback killer is shown in Fig. 2. The principle of operation is fairly simple. The input signal is passed through two all-pass filters whose output signals have a phase difference of 90°. These signals are multiplied with two clock signals that are also 90° out of phase. The resulting signals are added. As shown by equation (A) in Fig. 2, the multiplication and addition operations produce a new signal of a fre-

Sound technicians know a lot about microphone placement and often spend hours on small adjustments of the monitor loudspeakers. However, many artists are inclined to take the microphone from its stand the moment they are on stage. This requires great attention on part of the sound technician, since there remains a large risk of feedback occurring.

The circuit described here raises the sound level at which the feedback starts by a few decibels. This should not be taken

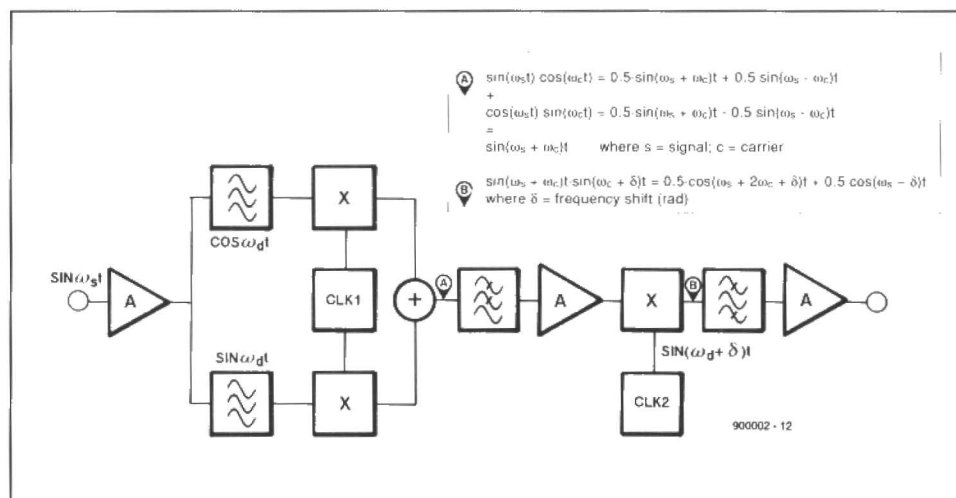


Fig. 2. Block diagram of the feedback killer, and its mathematical background.

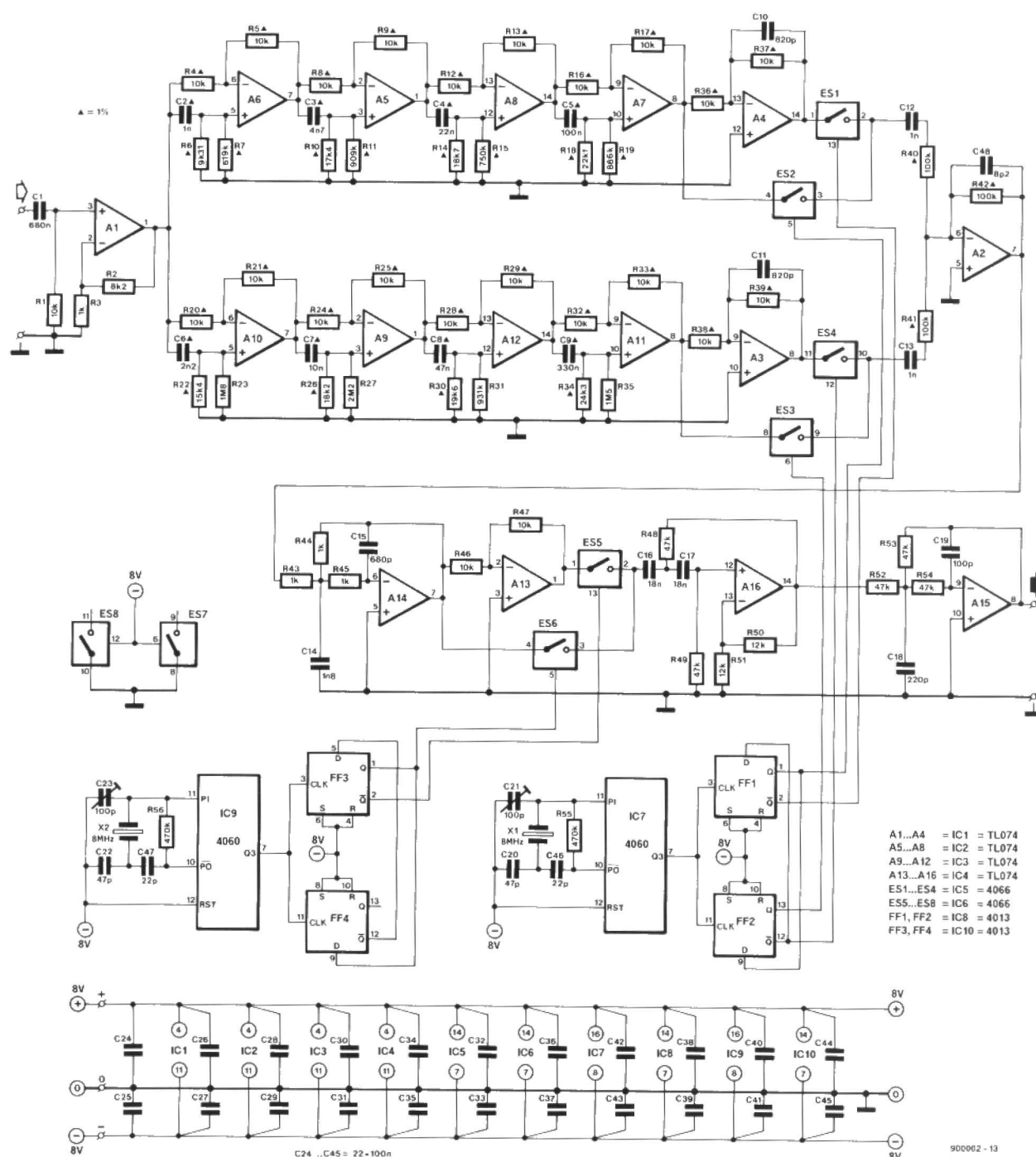


Fig. 3. Circuit diagram of the feedback killer.

quency equal to the sum of the frequency of the input signal and the frequency of the carrier with which it is mixed. The upshot is that the input signal is shifted over a small range in the frequency spectrum. Although the equation shows that the sum signal is a single frequency component only, it should be noted that this is only valid if the input signal is shifted exactly  $90^\circ$ . Unfortunately, this is only possible in theory. Any practical circuit produces spurious signals that cause amplitude-modulation (AM) of the mixer output signal. The all-pass filter used in the feedback killer ensures a phase shift of very nearly  $90^\circ$  over a frequency range of 50 Hz to 7 kHz:

The output signal of the mixer is taken through an active low-pass filter. This operation is required because the input signal is multiplied by  $90^\circ$ -shifted rectangular waves, rather than a sine-wave and a cosine-wave which would have given rise to a considerably more complex circuit. From Fourier analysis, a rectangular wave is composed of a fundamental frequency and an infinite number of odd-numbered sine-wave harmonics as

$$4/\pi(\cos(\omega t) - 1/3\cos(3\omega t) + 1/5\cos(5\omega t) \dots$$

The amplitude of the harmonics decreases with frequency. The use of two  $90^\circ$ -shifted rectangular waves results in a series of

sine-wave products and a series of cosine-wave products. The harmonics are removed in the previously mentioned low-pass filter, so that only the wanted mixer product remains.

There are two ways of shifting the input signal over a small range (1 Hz–30 Hz) in the frequency spectrum: 1) use a low-frequency modulation signal or 2) mix the signal a second time with a signal of which the frequency is almost the same as that of the first rectangular wave. Next, remove the undesirable sidebands with the aid of a filter.

The second principle is adopted in the feedback killer. Two carriers of a relatively high, but slightly different, frequency



are used.

The sum signal,  $A$ , obtained from the first mixer is filtered before it is mixed with a carrier,  $\sin(\omega_c + \delta)t$ , where  $\delta$  is the required shift in radians. The resulting signal,  $B$ , may be expressed as shown in Fig. 2. In the equation,  $-\cos(\omega_s + 2\omega_c + \delta)t$  is an unwanted sideband, and  $\cos(\omega_s + \delta)t$  the modulated input signal shifted by an amount  $\delta$  in the frequency spectrum. If the carrier frequency is relatively high (approx. 125 kHz), suppressing the unwanted sideband is relatively easy with the aid of a band filter, which doubles as a filter for the sidebands that are generated by the use of rectangular waves in the second clock generator.

## Circuit diagram

Figure 3 shows the circuit diagram of the feedback killer. The essential blocks in the circuit are an all-pass filter around IC<sub>2</sub>-IC<sub>3</sub>, an output filter around A<sub>15</sub> and A<sub>16</sub>, and two clock generators around IC<sub>7</sub>-IC<sub>10</sub>. The audio signal is buffered by A<sub>1</sub> before it is applied to the all-pass filter which introduces a phase shift of  $90 \pm 0.5^\circ$  for signals between 50 Hz and 7 kHz. The filter components have a tolerance of 1% to ensure that the deviation from  $90^\circ$  remains as small as possible (remember that the number of unwanted sidebands rises with the deviation from  $90^\circ$ ). The frequency range of the all-pass filter restricts the practical use of the circuit to speech. The feedback killer, must, therefore, not be used with singers or musicians, since the absolute frequency shift upsets harmonic relations and so causes the performers to play or sing out of tune.

The all-pass filter is followed by a buffer, A<sub>3</sub>-A<sub>4</sub>, which introduces a phase shift of  $180^\circ$  required for the first multiplication with the rectangular signal supplied by the first clock generator. The multiplication proper is effected by electronic switches ES<sub>1</sub>-ES<sub>4</sub> as illustrated in Fig. 4. The non-inverted and the inverted sine-wave is passed during the positive and negative half-cycle of the clock signal respectively.

Opamp A<sub>2</sub> adds the two mixed signals, and supplies, in principle, the components of which the rectangular wave consists. The frequencies of the components are, however, raised by the frequency of the input signal. Opamp A<sub>14</sub> suppresses all unwanted higher harmonics generated by the use of rectangular-wave clock (carrier) signals. As a result, the sum signal contains only the mixing product of the input signal and the fundamental frequency of the clock signal. The 'digital mixer' approach uses fewer components than an equivalent all-analogue (sine-wave/cosine-wave) circuit, and has the additional benefits of lower cost and the absence of adjustments.

The filtered signal is available in inverted form after opamp A<sub>13</sub>, and is mixed a second time with a clock signal. Like the first mixer, the second one uses electronic switches. The frequency dif-

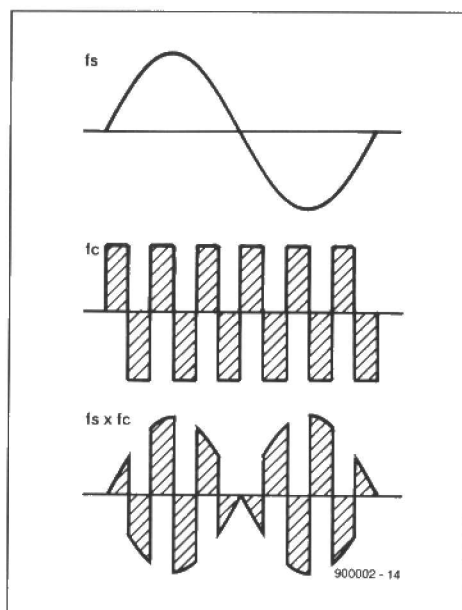


Fig. 4. Principle of frequency multiplication with the aid of electronic switches.

ference between the two clock signals determines the effective frequency shift of the input signal. The output signal of the second mixer is taken through a second-order high-pass filter, A<sub>16</sub>, and a second-order low-pass filter, A<sub>15</sub>, to remove all unwanted harmonics. The AF output is a virtual copy of the input signal: the only difference is that it covers a slightly different range in the frequency spectrum.

The clock generators around IC<sub>9</sub> and IC<sub>7</sub> are identical with a Type CD4060 oscillator/divider and an 8 MHz quartz crystal as the frequency determining element. The Q3-output of each CD4060 supplies the oscillator frequency divided by 16, i.e., 500 kHz. The two bistables (FF<sub>1</sub>-FF<sub>2</sub> and FF<sub>3</sub>-FF<sub>4</sub>) secure the required phase shift of  $90^\circ$  between the two clock signals. In this operation, the clock frequency is divided by four, so that the carriers have a frequency of 125 kHz. The trimmer capacitors in the crystal oscillators allow the frequency shift applied to the AF input signal to be adjusted to requirement.

## Components

The capacitors in the all-pass filter are preferably 1%-tolerance polystyrene ('styroflex') or silver-mica types, although the board allows MKT (plastic encapsulated multi-layer polytheterephthalate) types to be fitted also. These capacitors from Siemens generally have a tolerance of 5%. Note that when MKT capacitors are used, there is little point in using 1% resistors. The use of 5%-tolerance components in the all-pass filter increases the amplitude modulation of the output signal.

Two types of PTFE foil trimmer, 10x5 mm raster and 5x7.5 mm raster, may be used in positions C<sub>21</sub> and C<sub>23</sub>. Do not use ceramic types: they are not partly transparent as PTFE foil types and do not therefore allow the set capacitance to be deduced from the position of the rotor relative to the stator blades. Be sure to use quartz crystals and

CD4060's from one and the same manufacturer and, if possible, from a single batch (look at the production date indication, the type and batch number).

The circuit is a combination of analogue and digital electronics and has, therefore, relatively many decoupling capacitors to keep cross-talk and interference to a minimum. Fortunately, there is virtually no tolerance or quality requirement for the decoupling capacitors, so that inexpensive types may be used with impunity.

## Construction and adjustment


The circuit is preferably constructed on the single-sided PCB shown in Fig. 5. The construction is entirely straightforward and best started with fitting the wire links. Note that a fair number of resistors is mounted upright.

The adjustment of the circuit is simple. As already discussed, the frequency shift of the audio signal is determined by the frequency difference between the two crystal oscillators. This frequency difference is set with the respective trimmers, C<sub>21</sub> and C<sub>23</sub>.

The function of the circuit is relatively easy to check. Set both trimmers to about one-third of their travel. Connect a two-channel oscilloscope to the input and the output of the feedback killer. Apply a sine-wave to the input and synchronize the top channel of the scope. The circuit works if adjustment of one of the two trimmers causes the (output-) signal on the lower channel to start moving horizontally across the scope screen.

The frequency shift required for optimum suppression of feedback depends largely on the equipment used, the power ratings and anticipated sound levels, and, of course, the acoustic characteristics of the listening room. Finally, it will be clear that the effect of the circuit is less noticed at relatively small frequency shifts.

The circuit draws less than 50 mA from a regulated  $\pm 5$  V to  $\pm 8$  V power supply.

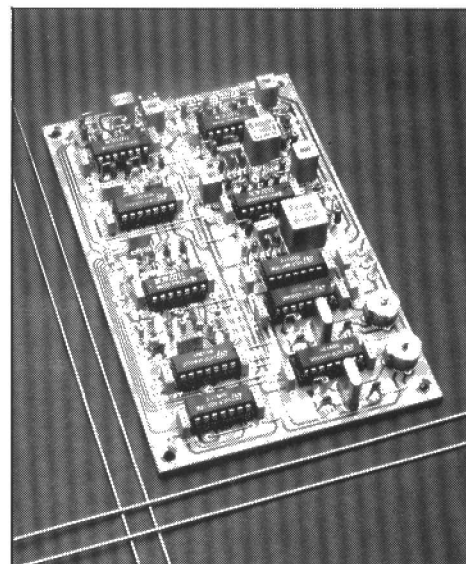

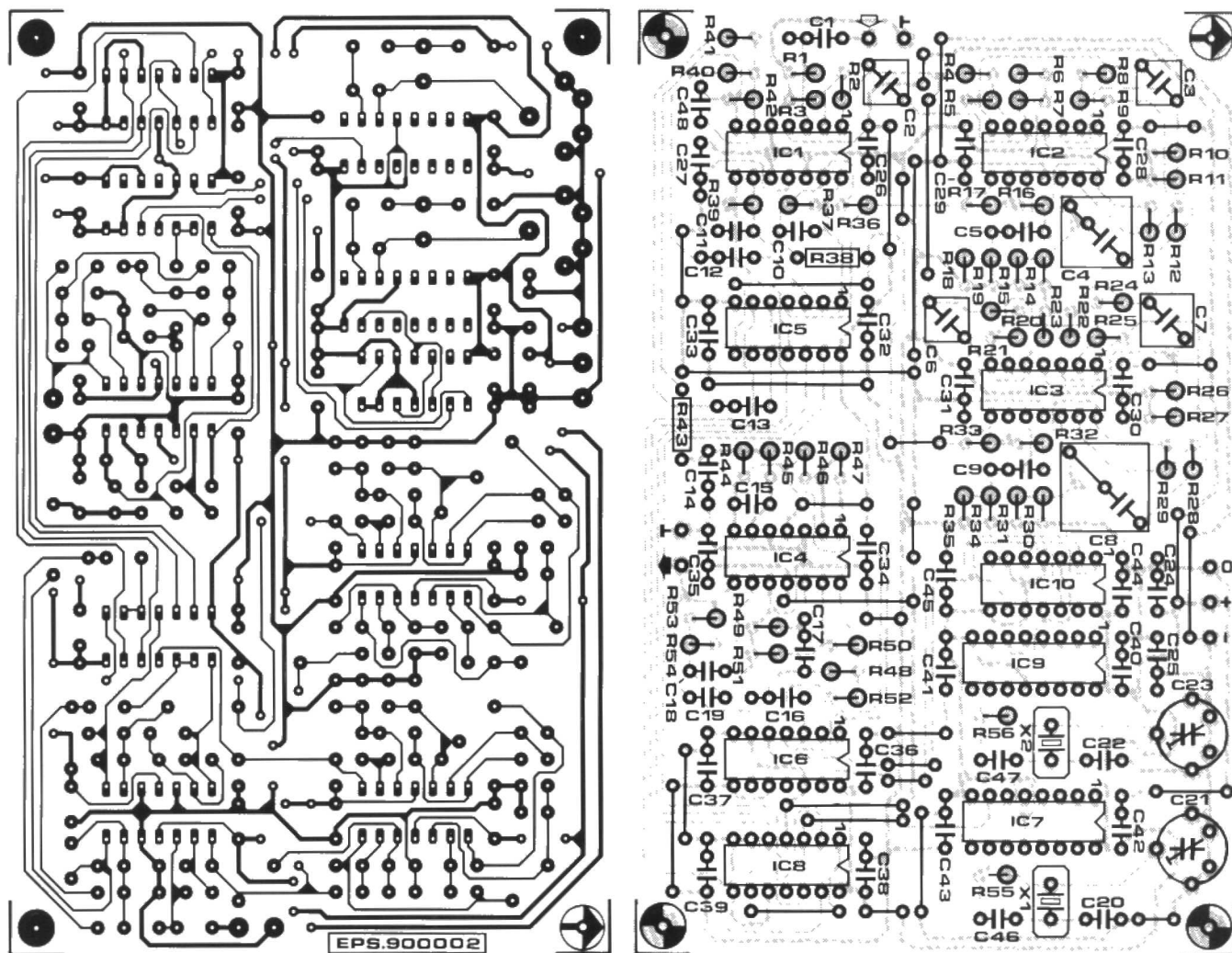


Fig. 5. Track layout and component mounting plan of the printed-circuit board for the feedback killer.

#### Parts list

##### Resistors:

R1 = 10k  
 R2 = 8k2  
 R3; R43; R44; R45 = 1k0  
 R4; R5; R6; R9; R12; R13; R16; R17; R20; R21; R24;  
 R25; R28; R29; R32; R33; R37; R38; R39;  
 R46; R47 = 10k 1%  
 R6 = 9k31 1%  
 R7 = 619k 1%  
 R10 = 17k4 1%  
 R11 = 909k 1%  
 R14 = 18k7 1%  
 R15 = 750k 1%  
 R18 = 22k1 1%  
 R19 = 866k 1%  
 R22 = 15k4 1%  
 R23 = 1M8  
 R26 = 18k2 1%  
 R27 = 2M2

R30 = 19k6 1%  
 R31 = 931k0 1%  
 R34 = 24k3 1%  
 R35 = 1M5  
 R40; R41; R42 = 100k 1%  
 R48; R49; R52; R53; R54 = 47k  
 R50; R51 = 12k  
 R55; R56 = 470k

##### Capacitors:

C1 = 680n  
 C2 = 1n0 1%  
 C3 = 4n7 1%  
 C4 = 22n 1%  
 C5 = 100n 1%  
 C6 = 2n2 1%  
 C7 = 10n 1%  
 C8 = 47n 1%  
 C9 = 330n 1%  
 C10; C11 = 820p  
 C12; C13 = 1n  
 C14 = 1n8

C15 = 680p  
 C16; C17 = 18n  
 C18 = 220p  
 C19 = 100p  
 C20; C22 = 47p  
 C21; C23 = 100p trimmer  
 C24 - C45 = 100n  
 C46; C47 = 22p  
 C48 = 8p2

##### Semiconductors:

IC1 - IC4 = TL074  
 IC5; IC6 = 4066  
 IC7; IC9 = 4060  
 IC8; IC10 = 4013

##### Miscellaneous:

X1; X2 = quartz crystal 8 MHz.  
 PCB Type 900002 (not available ready-made through the Readers Services).

# PC RADIO

**This FM radio, designed by ELV GmbH, consists of an insertion card for IBM PC-XTs, ATs and compatibles and is available as a kit or a ready-built and aligned unit. The radio has an on-board AF power amplifier for driving a loudspeaker or a headphone set, and is powered by the computer. A menu-driven program is supplied to control the radio settings.**

Take a look around many modern offices and you will notice PC users or terminal operators wearing headphones while sitting in front of their screens. In most cases, a portable radio or cassette recorder is placed on the desk or near the PC to lighten the work with a little music without annoying colleagues.


This PC radio with integrated power amplifier is constructed on an insertion card that can be plugged into any free bus extension slot on the motherboard of an IBM PC-XT, PC-AT or compatible computer running under MSDOS control.

## Control program and cursor keys

The control software for the radio is supplied on a 5¼-inch MSDOS formatted diskette with 360 KByte capacity. After the computer is switched on, this disk is inserted into one of the disk drives. Use the DOS to select the relevant disk drive and type PCRADIO to load and run the control program, which is automatically configured for the graphics adapter card used in the computer. The cursor keys are used to select the menu areas shown on the introductory photograph. The adjustments that can be made include bass, treble, volume, manual or automatic tuning and a signal-level-dependent muting. The volume area is selected as a default when the program is started. The left and right keys on the cursor keypad allow the volume to be reduced or increased respectively, while a coloured horizontal bar on the screen indicates the relative setting. A further volume indication is provided by a large two-digit number to the right of the bar. The volume setting can take values between 0 and 63.

The up and down cursor keys select the menu areas. Pressing ↓, for instance, moves the PC radio setting from the volume to the treble area, which uses a coloured bar and a two-digit indication like the volume setting. Pressing ↓ again selects the bass setting. Here, again, the ← and → keys may be used to change the setting.

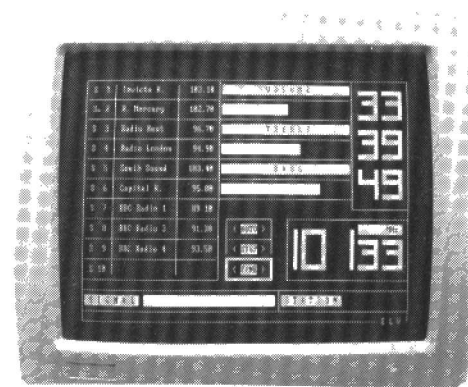The next area reached by pressing ↓ from the bass area is the tuning control. Press the → and ← keys to tune up and down respectively. The frequency step size in the VHF FM band is 10 kHz. The tuning rate is increased automatically to



The PCRADIO menu screen (control program version 1.2).

about 2 MHz per second if the ← or → keys are depressed longer than necessary for a single keystroke. The fast tuning feature allows the full VHF FM broadcast band to be covered in about 10 seconds.

Manual tuning is accomplished by typing the required frequency on the number keys. Automatic station scan is selected on pressing the ↑ or ↓ key. In this mode, the ← and → keys select between scanning up or down from the current frequency. The scanner stops when a station is received. If the band is empty (hardly likely these days) or if the stations are too weak, the radio automatically reduces its detection threshold and starts a new scan. The high sensitivity mode may also be entered by pressing the scan cursor keys twice within one second at the start of the station scan.

The relative field strength of the received station is indicated in the lower left-hand corner of the screen. The 'mute' function allows the level to be defined below which the AF amplifier of the radio is automatically muted. This function eliminates noise between stations as the scan mode is in operation. It is selected via the ↑ and ↓ keys, while the ← and → keys allow the mute level — displayed in a different colour — to be adjusted to individual requirement. Reception of very weak signals is made possible by moving the mute bar to the extreme left of the screen.

The menu area in the lower right corner of the screen is reserved for the station name, provided this is among the ones listed to the left of the screen. Any station can be pre-programmed. When it is listed, it may be selected rapidly by pressing the associated function key F1 through F10.

Stations are pre-programmed as follows. First, tune to the desired station, then hold the SHIFT key depressed before pressing the function key to define the station number in the list. Next, type the station name on the keyboard and press ENTER.

The PCRADIO control program is left on pressing ESC (escape). Next, the user is asked whether or not the previously made changes to the settings and the station list are to be saved or cancelled. After going through this menu, the user is returned to the DOS prompt. The radio remains on, however, using the current settings, although the control program is removed from the computer's memory. The computer is ready to load and run other software at this stage.

## For advanced PC users

The following information is aimed at advanced PC users, allowing them to use a number of special features of the PC radio.

The PC radio kit is supplied with a diskette that, apart from the previously described user software, contains a documentation file, READ.ME, and an installation program, INSTALL.EXE. Hard copy of the (ASCII-) READ.ME file is obtained in the usual way by typing CONTROL-P followed by TYPE READ.ME and a carriage return. Turn off the printer again by typing CONTROL-P.

The PCRADIO program may be made memory-resident by calling it up with a switch: PCRADIO /I <CR>. The program may be called up while another program is running by pressing the two SHIFT keys simultaneously. This key combination may be changed to requirement as detailed further on. The radio settings in use may be changed as described earlier, but they can not be saved to disk in the resident mode of the control program. The PCRADIO program is left by pressing the ESC key. It may be cleared from the resident program memory by typing PCRADIO /R from the DOS prompt.

The installation program allows a number of hardware and software parameters to be pre-defined. Its menu starts with the I/O address, which has been set to default 300H on the PCB as well as in the control program. Changes may be made as required. Next, the system checks if the PC radio card can be addressed in the selected I/O area.



The next menu step allows the user to define the key combination for calling up the memory-resident program. The default is the left and right SHIFT keys on the keyboard. Depending on whether other memory-resident programs use the same combination, this may be changed via a submenu.

## Block diagram

With reference to the block diagram in Fig. 1, a special feature of the VHF tuner block that receives the signal from the external aerial is that it contains an IF (intermediate frequency) stage as well as an audio preamplifier. This allows the output of the tuner to be connected direct to a tone control section, which has direct voltage inputs for the bass, treble and volume settings. The output signal provided by the tone control stage is applied to an on-board AF power amplifier capable of driving a 4  $\Omega$  loudspeaker.

The control voltages for the tuner and the preamplifier/tone control section are provided by digital-to-analogue converters (DACs) which translate the binary values obtained as digital combinations from the PC bus via a databuffer into corresponding voltage levels. A 12-bit DAC supplies the tuning voltage for the variable capacitance diodes (varicaps) in the FM tuner. The field strength voltage is sent to the computer via an A-D converter. The DACs for volume-, bass and treble control are 6-bit types which offer ample resolution for the purpose.

## Circuit description

The circuit diagram of the PC radio is given in Fig. 2. The operation of the four main circuit sections that make up the PC radio is discussed under separate headings.

### VHF FM tuner

The aerial signal is applied to the mixer inputs of the TDA7021, pins 12 and 13, via bandfilter L1-C27-C28-C29. The bandfilter suppresses signals outside the VHF FM broadcast band. In the configuration used, the Type TDA7021T single-chip FM receiver achieves a sensitivity of about 4  $\mu$ V. The local oscillator frequency is determined by external components L2-C30-C32 and varicap KD1. The LO is tuned by applying a direct voltage between 0 V and 10 V to R71. The IF amplifier on board the TDA7021T operates at 76 kHz, and uses only three external capacitors, C33, C34 and C35. The field strength (f-s) output of the chip, pin 9, supplies a current of about 20  $\mu$ A when a strong station is received, and about 150  $\mu$ A when no station is received. This current is passed through R74 on which it causes a proportional voltage. Capacitor C41 eliminates short variations of the field strength voltage.

The amplified IF signal is internally demodulated, and the resultant AF signal is applied to an on-board AF amplifier. The AF output voltage of the chip has an

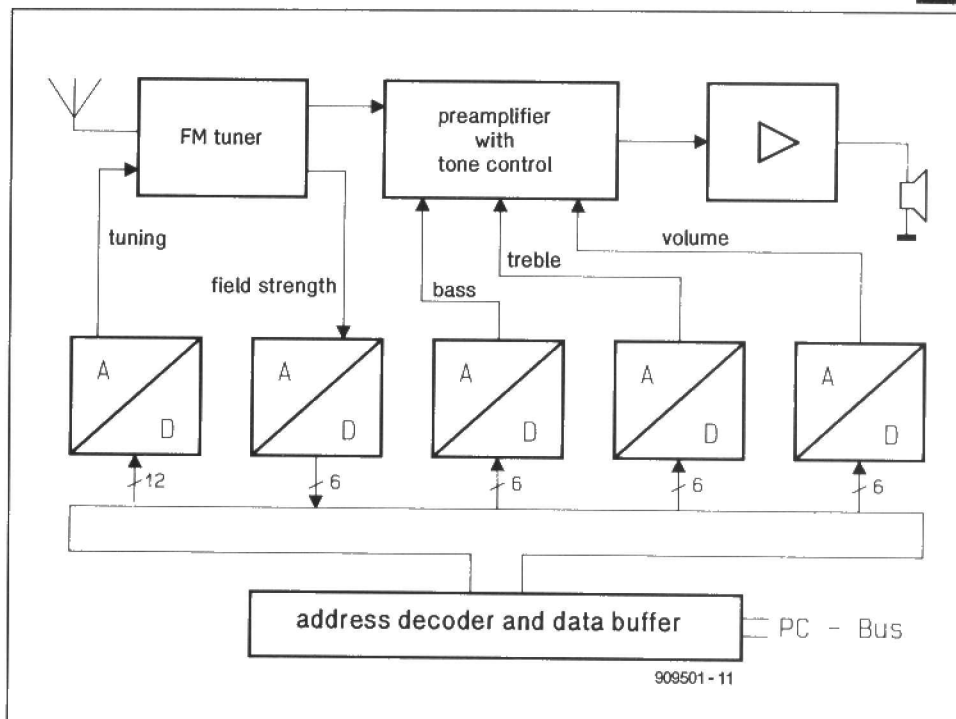


Fig. 1. Block diagram of the PC radio card.

amplitude of about 80 mV<sub>pp</sub> at pin 14.

### Tone control

The Type TDA1524A preamplifier/tone control chip receives its input signal via C42. The second input of the chip, pin 4, is decoupled by C43 because the stereo mode is not used in this application. Direct voltages applied to pins 1, 9 and 10 enable the tone and volume parameters to be set with the aid of the internal electronic potentiometers. Capacitors C44 and C45 and resistor R77 are used for the bass control, while treble control is effected with C46. Resistor R95 is optional, and selects between linear and contour operation of the preamplifier. If chip output pin 17 supplies a current between 1.5 mA and 10 mA, the preamplifier works linearly. If the current is smaller than about 0.5 mA, the loudness/contour correction is actuated.

The bass response of the TDA1524A also depends on external components. R77 may be omitted, and C45 or C44 may be replaced by a wire link to limit the low frequency range.

The chip receives its supply voltage via pin 3. The chip supply voltage is cleaned and buffered by C48 and C47 respectively.

### AF power amplifier

The AF output signal at pin 11 of the TDA1524A is coupled out with C49 and taken to input pin 1 of an integrated AF power amplifier, IC16, a Type TDA2030. This chip provides a voltage amplification of about 8 as well as the necessary current amplification in its power output stage.

Since the chip output is at about half the supply voltage, a coupling capacitor, C53, is required to connect the loudspeaker. Components R83 and C56 suppress any tendency of the AF amplifier to oscillate.

### Digital section

The description of the digital section of the PC radio card is best started at the address decoder. This consists of an 8-bit comparator, IC4, for the base address, and two 1-of-4 decoders in IC3 for the addresses within the selected block. Address lines A2 through A9 are applied to the comparator to achieve block decoding. The base address is set with jumpers Br1 through Br8. Omitting jumpers Br1 and Br2, for instance, selects base address 300H, the default setting of the card (consult Table 1 for the address assignment).

When the CPU in the PC addresses I/O location 300H (A8 and A9 are high), output P=Q of IC4 goes low. Assuming that the I/O access is a write operation (i.e., pin 4 of IC2 is low), pin 15 of IC3 goes low also. Depending on the bit combinations on address lines A0 and A1, one of four outputs Y0 through Y3 changes to low. If, for instance, address 302H is selected, pin 11 of IC36 goes low and provides a latch pulse for IC7. The 8-bit word on the databus is latched into D-type register IC7, which holds the bass setting.

The four 6-bit D-A converters are discrete types set up around four 8-bit latching registers, IC6 through IC9, and associated R-2R ladder networks. The voltage at the output of each ladder is programmable between 170 mV and 3.2 V in 64 steps.

Circuit IC9, an 8-bit latch, is used for driving the 12-bit D-A converter, IC10, as well as for field strength measurement.

The 12-bit DAC receives an 8-bit word from IC9, and 2-bit words from IC7 and IC8. The DAC reads these words from address BASE+1. The reference voltage for the DAC is provided by voltage divider R62-R63 at pin 19. Opamp IC11a supplies a voltage between 0 V and -1 V in 4,096 (10<sup>12</sup>) steps. This voltage is amplified and inverted by a further opamp, IC11b. Resistors

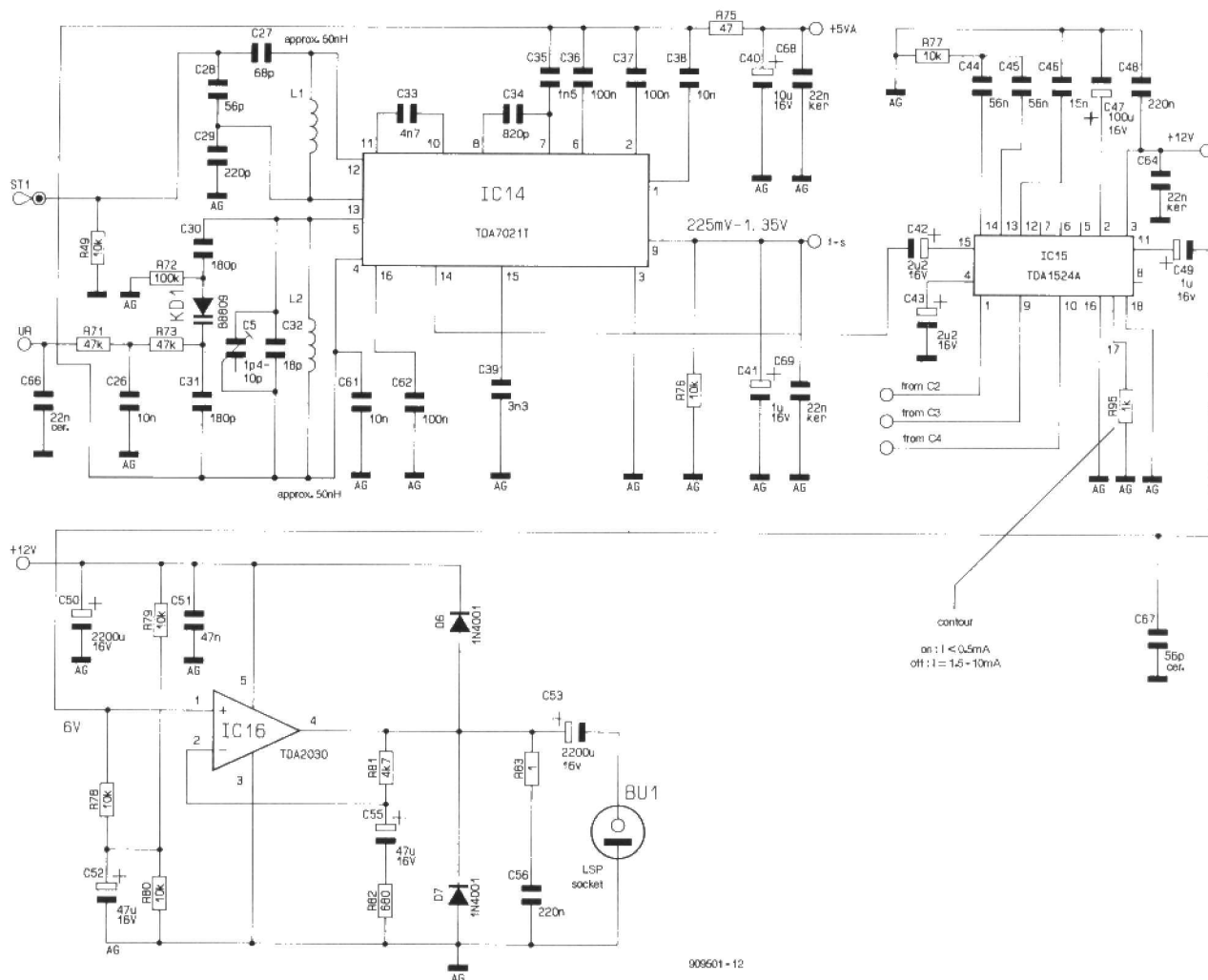


Fig. 2. Circuit diagram of the RF and AF sections of the PC radio.

R71 and R73 feed the tuning voltage to the varicap in the FM tuner. The gain of the second opamp is adjustable over a relatively wide range to allow the tuning range required to cover the FM band to be set with preset R92.

The field strength voltage provided by the TDA7021T is applied to pin 10 of opamp IC<sub>11c</sub>. A field strength indication of 0 on the screen corresponds to about 1.35 V, and one of 63 to about 245 mV. The opamp raises the field strength voltage to a level at which pin 12 of comparator IC<sub>11d</sub> is held at a voltage of between 0 V and 4 V. The DAC built around IC<sub>9</sub> and the R-2R network allow the comparator threshold at pin 13 of IC<sub>11d</sub> to be changed. The output state of the comparator can be requested at I/O address BASE+1 via buffer IC<sub>12a</sub>. Since the output voltage of the opamp can take values between -5 V and +12 V, R<sub>69</sub>, R<sub>70</sub>, D<sub>4</sub> and D<sub>5</sub> are required to limit the voltage to 0 V and 5 V.

The remaining three drivers in IC<sub>12</sub> are used to check the addressing of DACs IC<sub>6</sub>, IC<sub>7</sub> and IC<sub>8</sub>.

The circuit is reset at power-on by a 100-ms long low pulse at pins 1 and 2 of IC<sub>5a</sub>. This causes bistable IC<sub>5c</sub>-IC<sub>5d</sub> to be reset via gates IC<sub>2a</sub> and IC<sub>5b</sub>. Transistor T<sub>1</sub>

short-circuits the voltage at pin 1 of the TDA1524A to ground to reset the internal electronic volume potentiometer. After 100 ms, pin 4 of IC<sub>5</sub> reverts to logic high,

and it can be set, i.e., pin 6 can be made low, by a read operation to address BASE+2 via IC<sub>3a</sub>. Depending on the position of jumper JP<sub>1</sub>, the radio may also be switched

Off-set address	read operation	write operation
0 (base)	D5 – D0 = 6-bit DAC for volume control  D6 = not used D7 = control bit 1	D0 = comparator output for field-strength measurement D1 = control bit 1 D2 = control bit 2 D3 = control bit 3
+1	D5 – D0 = 6-bit DAC for bass control D7; D6 = D9; D8 for 12-bit tuning DAC D7 = control bit 2	latch data into 12-bit DAC
+2	D5 – D0 = 6-bit DAC for treble control D7; D6 = D11; D10 of 12-bit tuning DAC D7 = control bit 3	turn on AF
+3	D5 – D0 = 6-bit DAC for field-strength D7 – D0 = D7 – D0 for 12-bit tuning DAC	turn off AF

**Table 1. Input/output address assignment on the PC radio card.**

to mute when the PC is reset. Another possibility to control the mute function exists in a read operation to address BASE+3 (IC<sub>3a</sub> pin 7).

All supply voltages for the circuit are

taken from the PC expansion bus. Note, however, that the 5 V supply for the analogue circuits is provided by voltage regulator IC<sub>13</sub>.

## Construction

The complete circuit is built on a double-sided through-plated printed circuit board supplied with the kit. The size of the

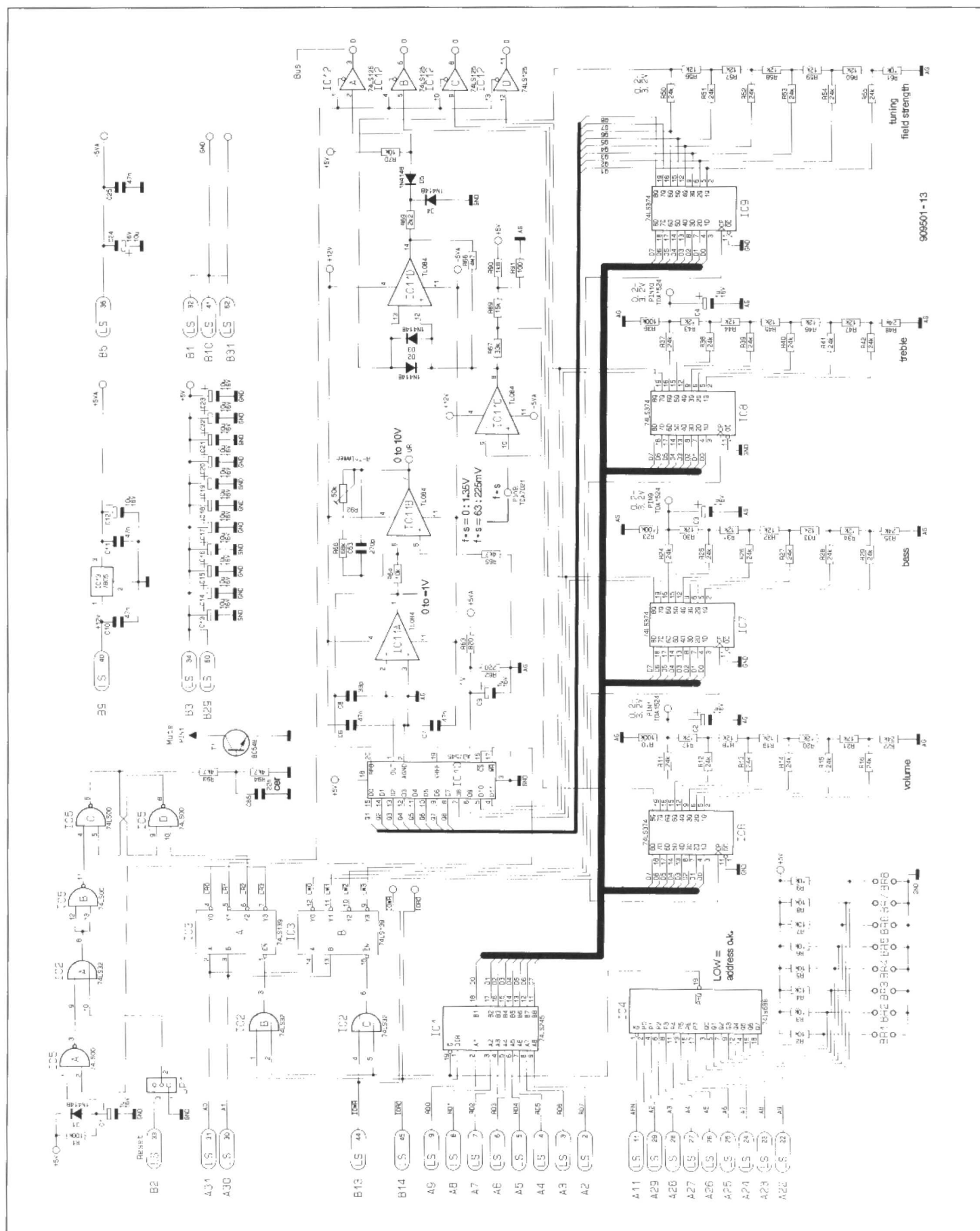


Fig. 3. Circuit diagram of the digital section and the PC-interface of the FM radio card.



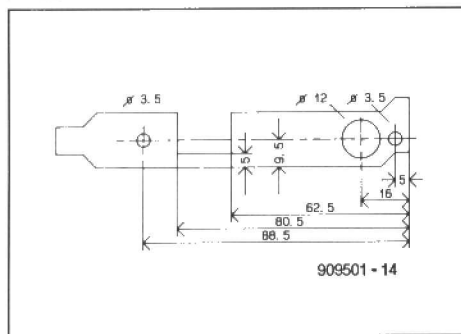


Fig. 4. Cutting and drilling details of the aluminium support bracket.

board is 230×108 mm.

Start with fitting the low-profile components as per the indications on the component overlay (Fig. 5) and the parts list. Proceed with the taller components. Since the board is through-plated, soldering at the component side is not required. Leave the wire terminals of C<sub>50</sub> and C<sub>53</sub> longer than usual to enable these capacitors to be bent towards the board as shown in the photograph. The TDA2030 and its heat-sink are also mounted horizontally and secured on to the board with an M3 bolt.

The TDA7021T FM receiver chip is an SMA (surface-mount assembly) type which requires great care and precision in handling as well as soldering. First place the IC on to the board. Next, position it accurately with the aid of a pair of tweezers so that the terminals align with the solder areas. Use a low-power solder iron with a fine tip and a power rating of not more than 16 W to solder one of the corner pins of TDA7021T to the associated track. Next, use a sharp device to align the other IC pins with the tracks below. Heat the pins briefly in rapid succession while applying very little solder.

Interconnect the points marked A and those marked B on the PCB with an insulated wire of 0.4 mm<sup>2</sup> cross-sectional area or larger.

The position of the tin-plate screen around the FM tuner section on the PCB is shown in the top view of the completed printed-circuit board in Fig. 5. Bend the screen in the form of a rectangle and join its ends by soldering. Place the screen so made vertically on to the component side of the PCB, and align it with the PCB edges. This is necessary for the PCB support bracket which is secured to the screen later. Solder the screen to the PCB, applying a generous amount of solder tin from the inside, but taking care not to damage components by overheating. Be sure to cover the entire length of the screen, i.e., do not solder it to the PCB in just a few locations. Next, bend and fit a similarly shaped, but lower, screen on to the component side of the PCB, opposite the screen just mounted. Drill a hole in the taller screen for the aerial input socket (9.4 mm dia.).

Use an M3×6 mm bolt, a washer and a nut to secure a small aluminium bracket to the lower side of the PCB. Next, prepare a standard PCB support bracket as shown

#### Parts list

##### Resistors:

R<sub>83</sub> = 1Ω  
 R<sub>75</sub> = 47Ω  
 R<sub>91</sub> = 100Ω  
 R<sub>62</sub> = 220Ω  
 R<sub>82</sub> = 680Ω  
 R<sub>63</sub> = 820Ω  
 R<sub>95</sub> = 1kΩ  
 R<sub>90</sub> = 1kΩ  
 R<sub>69</sub> = 2kΩ  
 R<sub>65</sub>; R<sub>81</sub>; R<sub>93</sub>; R<sub>94</sub> = 4kΩ  
 R<sub>2</sub> – R<sub>9</sub>; R<sub>49</sub>; R<sub>61</sub>; R<sub>64</sub>; R<sub>70</sub>; R<sub>76</sub> – R<sub>80</sub> = 10k  
 R<sub>17</sub> – R<sub>21</sub>; R<sub>30</sub> – R<sub>34</sub>; R<sub>53</sub> – R<sub>47</sub>; R<sub>56</sub> – R<sub>60</sub> = 12k  
 R<sub>98</sub> = 15k  
 R<sub>11</sub> – R<sub>16</sub>; R<sub>22</sub>; R<sub>24</sub> – R<sub>29</sub>; R<sub>35</sub>; R<sub>37</sub> – R<sub>42</sub>; R<sub>48</sub>; R<sub>50</sub> – R<sub>55</sub> = 24k  
 R<sub>67</sub> = 33k  
 R<sub>71</sub>; R<sub>73</sub> = 47k  
 R<sub>66</sub> = 68k  
 R<sub>1</sub>; R<sub>10</sub>; R<sub>23</sub>; R<sub>36</sub>; R<sub>72</sub> = 100k  
 R<sub>68</sub> = 4M7  
 R<sub>92</sub> = 50k preset V

##### Capacitors:

C<sub>32</sub> = 18p  
 C<sub>8</sub> = 33p  
 C<sub>28</sub>; C<sub>67</sub> = 56p  
 C<sub>27</sub> = 68p  
 C<sub>30</sub>; C<sub>31</sub> = 180p  
 C<sub>29</sub> = 220p  
 C<sub>63</sub> = 270p  
 C<sub>34</sub> = 820p  
 C<sub>35</sub> = 1n5  
 C<sub>39</sub> = 3n3  
 C<sub>33</sub> = 4n7  
 C<sub>26</sub>; C<sub>38</sub>; C<sub>61</sub> = 10n  
 C<sub>46</sub> = 15n  
 C<sub>64</sub>; C<sub>65</sub>; C<sub>66</sub>; C<sub>68</sub>; C<sub>69</sub> = 22n ceramic  
 C<sub>6</sub>; C<sub>7</sub>; C<sub>10</sub>; C<sub>11</sub>; C<sub>25</sub>; C<sub>51</sub> = 47n  
 C<sub>44</sub>; C<sub>45</sub> = 56n  
 C<sub>36</sub>; C<sub>37</sub>; C<sub>62</sub> = 100n

C<sub>48</sub>; C<sub>56</sub> = 220n

C<sub>1</sub> – C<sub>4</sub>; C<sub>9</sub>; C<sub>41</sub>; C<sub>49</sub> = 1μ0; 16 V

C<sub>42</sub>; C<sub>43</sub> = 2μ2; 16 V

C<sub>12</sub> – C<sub>24</sub>; C<sub>40</sub> = 10μ; 16 V

C<sub>52</sub>; C<sub>55</sub> = 47μ; 16 V

C<sub>47</sub> = 100μ; 16 V

C<sub>50</sub>; C<sub>53</sub> = 2200μ; 16 V

C<sub>5</sub> = 40p trimmer

##### Semiconductors:

IC<sub>10</sub> = AD7545

IC<sub>15</sub> = TDA1524

IC<sub>16</sub> = TDA2030

IC<sub>14</sub> = TDA7021T (SMD)

IC<sub>5</sub> = 74LS00

IC<sub>2</sub> = 74LS32

IC<sub>12</sub> = 74LS125

IC<sub>3</sub> = 74LS139

IC<sub>1</sub> = 74LS245

IC<sub>6</sub> – IC<sub>9</sub> = 74LS374

IC<sub>4</sub> = 74LS688

IC<sub>11</sub> = TL084

IC<sub>13</sub> = 7805

T<sub>1</sub> = BC548

KD<sub>1</sub> = BB809

D<sub>6</sub>; D<sub>7</sub> = 1N4001

D<sub>1</sub> – D<sub>5</sub> = 1N4148

##### Miscellaneous:

Bu<sub>1</sub> = loudspeaker socket.

Qty 1: SK13 heat-sink

Qty 1: coax socket.

Qty 1: 3-way pin header.

Qty 1: jumper.

Qty 1: aluminium bracket.

Qty 1: tin-plate for screening

Qty 3: screw M3×6.

Qty 1: screw M3×8.

Qty 4: nut M3.

Qty 1: metal cover.

Solder pins.

90 mm insulated wire, min. 0.4 mm<sup>2</sup>.

140 mm silver-plated wire.

3 m coaxial cable.

in Fig. 4. Secure this bracket and the aerial input socket to the screen on the PCB. Solder the socket to screen, and secure the support bracket to it with two M3×6 mm bolts and nuts. Connect a short piece of insulated wire between the signal pin of the socket and point ST1 on the PCB. Note the position of C<sub>5</sub> on the PCB and drill a hole in the metal cover to be mounted on to the screen at the component side of the

board. This hole serves to access C<sub>5</sub> with a trimming tool. Solder the covers to the two screens.

Install the PC radio card into the computer, and screw the support bracket to the back panel. Do not forget to check that this panel is connected to ground of the PC — this is essential for the FM tuner on the PC radio card. Finally, connect an FM aerial via 75 Ω coaxial cable.

## Adjustment

Start the PC radio program from floppy- or hard disk. Use the menu to set the frequency to that of a station in the lower range of the FM band, e.g., to 88.5 MHz. Align C<sub>5</sub> with an insulated trimming tool until this station is received (use a second radio as a reference). Next, set a receive frequency near the top of the band, e.g., 104 MHz, and adjust R<sub>92</sub> until a previously selected station is received. If the adjustment of C<sub>5</sub> is correct, the frequency shown on the menu screen corresponds to the transmit frequency of the station.

A complete kit of parts for the PC radio is available from the designers' exclusive worldwide distributors (regrettably not in the USA and Canada):

#### ELV France

B.P. 40

F-57480 Sierck-les-Bains

FRANCE

Telephone: +33 82837213

Fax: +33 82838180

Also see ELV France's advertisement elsewhere in this issue.

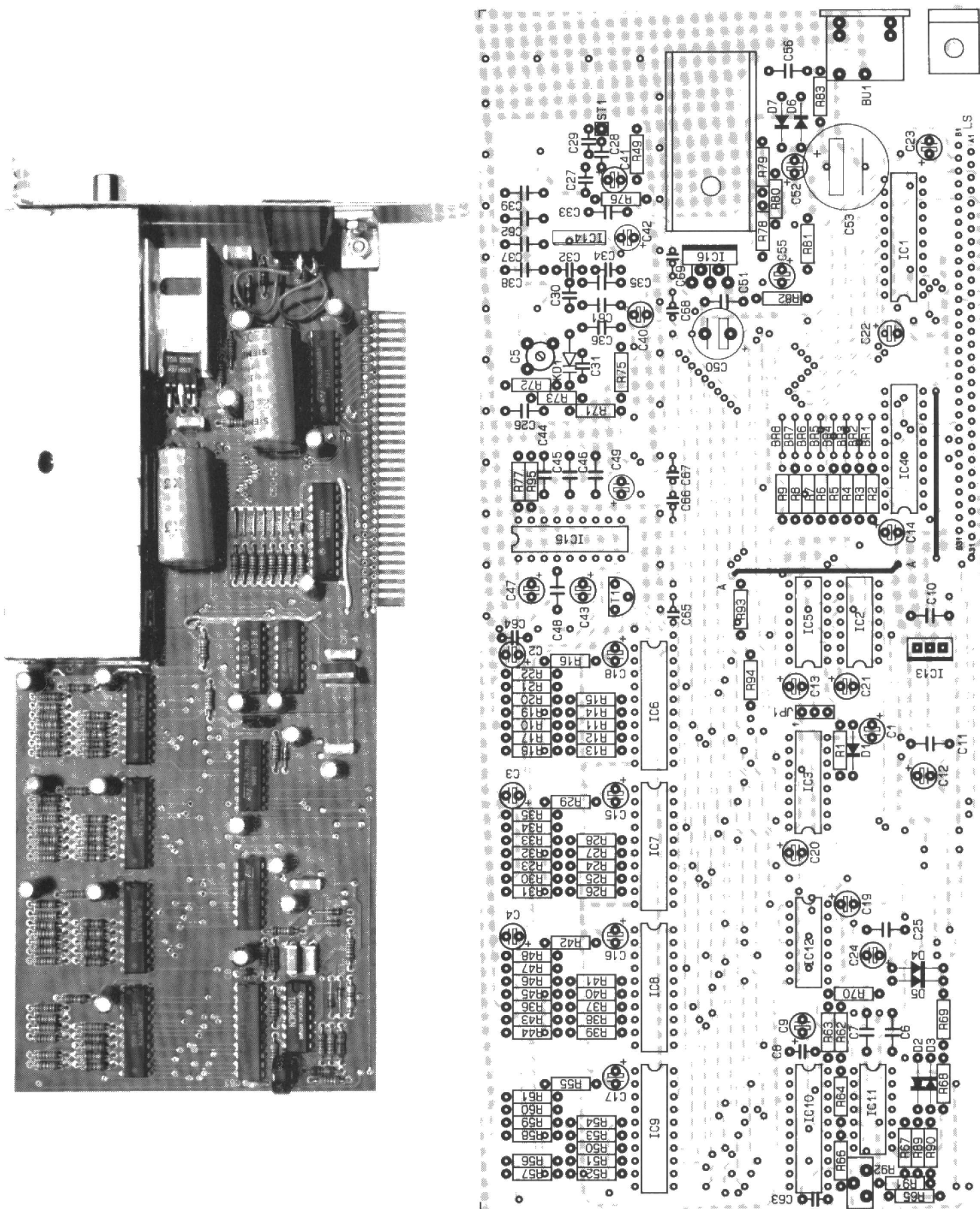


Fig. 5. Top view of the completed PC radio card with the screening installed (left) and the component mounting plan (right).

# AC-DC CURRENT SENSORS

Current may be measured without introducing losses in its path with the aid of the well-known series current transformers with clip-on probes or reed sensors in which a contact is closed by the presence of a magnetic field. These devices suffer from a serious drawback, however: they can not measure direct currents. The sensors described here depend on the Hall effect and are suitable for measuring both alternating and direct currents.

## The Hall effect

The Hall effect is observed in thin strips of metal and in some semiconductors. When a strip carrying current is placed in a magnetic field that is perpendicular to the strip's plane, a voltage appears between opposite edges of the strip that, although it is weak, will force a current through an external circuit.

The force due to the magnetic flux density,  $B$ , on a charge carrier of charge  $e$  and drift velocity,  $v$ , is equal to  $evB$ . This force displaces the carriers and sets up a non-uniform charge distribution that gives rise to an electric field,  $E$ . At equilibrium, the force on the charge carriers,  $eE$ , due to this field just balances that due to the flux density:

$$eE + evB = 0.$$

The drift velocity is related to the current density,  $j$ , by

$$j = nev$$

where  $n$  is the number of charge carriers per unit volume. Thus, the electric field is related to the vector product of the magnetic flux density and the current density by:

$$E = -R_H(jB)$$

where  $R_H$  is the Hall coefficient that is equal to  $1/ne$ . The electric field results in a potential difference,  $U_H$ , the Hall voltage, across the material.

In some materials, the direction of the field is reversed, which means that these materials have a positive Hall coefficient. This indicates that in these materials the current is carried by positively charged carriers, that is, by holes.

Electrons in an electric field move in straight lines as shown in Fig. 1a, whereas in an homogeneous electro-magnetic field they follow cycloidal paths (Fig. 1b). In degenerate semiconductor materials, they can not follow such paths owing to frequent collisions with atoms of the semiconductor material. Because of these collisions, the electrons lose velocity and this results in a waning of the magnetic field, since the strength of that field is directly proportional to the velocity of the charge carriers. The electrons are consequently attracted more strongly by the electric field as shown in Fig. 1c.

When a wafer of semiconductor material is connected as shown in Fig. 2 and placed in a magnetic field, an e.m.f., the Hall voltage,  $U_H$ , is generated across the longer sides of the wafer. Because of this, the wafer is called a **Hall generator**. The level of the e.m.f. is directly proportional to the strength of the magnetic field. If the direction of the field is reversed, the direction of the voltage also changes by  $180^\circ$ . Within certain limits, the e.m.f. is

$$U_H = R_H j B / d$$

where  $d$  is the thickness of the wafer. Note that the Hall voltage is inversely proportional to the thickness of the material.

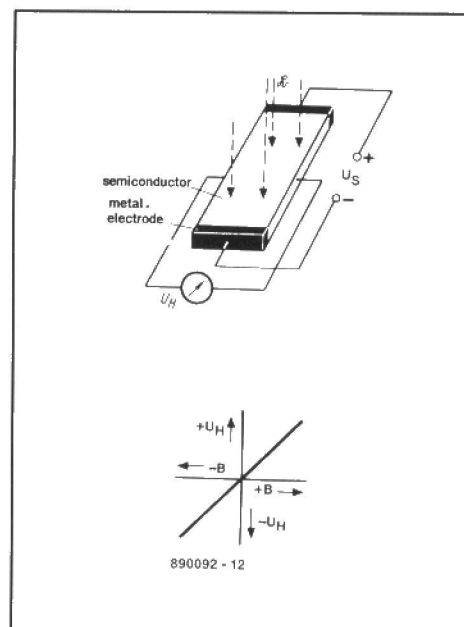


Fig. 2. The Hall voltage,  $U_H$ , is generated across the longitudinal sides of a Hall generator.

Hall generators have come more into vogue with the arrival of semiconductor materials such as indium antimonide (InSb) and indium arsenide (InAs), which have a high electron mobility, resulting in a large Hall coefficient, and a low specific resistance. Table 1 gives a comparison of the electron mobility (average drift velocity per unit electric field),  $v$ , in copper and a number of semiconductor materials.

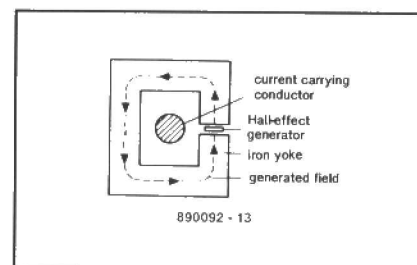


Fig. 3. With the Hall generator in the air gap of the iron yoke of a current sensor, the Hall voltage is directly proportional to the current flowing in a conductor that is at right angles to the cross-sectional plane of the yoke.

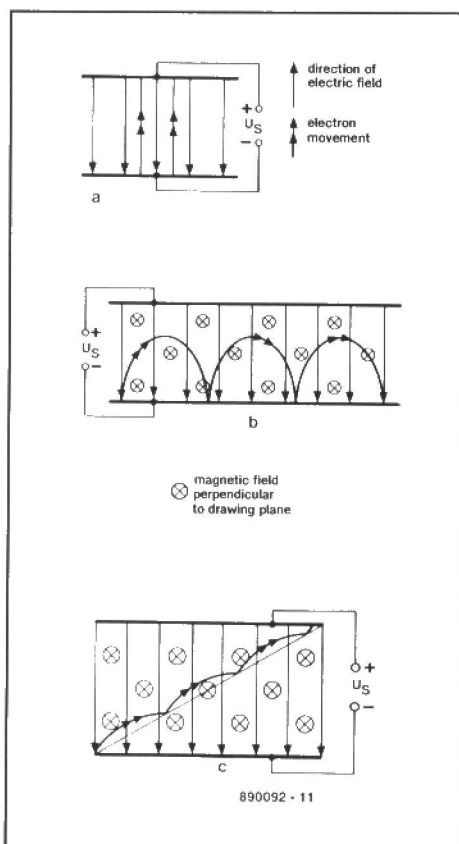


Fig. 1. Movement of electrons in: (a) an electric field; (b) a homogeneous electro-magnetic field in a vacuum; and (c) in a degenerate semiconductor material.



Material	Type	Drift velocity ( $\text{cm}^2 \text{V}^{-1} \text{s}^{-1}$ )
copper	metal	27–43
silicon	group 4 semiconductor	1350
germanium	group 5 semiconductor	3900
InAs	A <sup>III</sup> B <sup>V</sup> semiconductor	23 000
InSb	A <sup>III</sup> B <sup>V</sup> semiconductor	65 000

Table 1. Electron mobility in copper and a number of semiconductor materials.

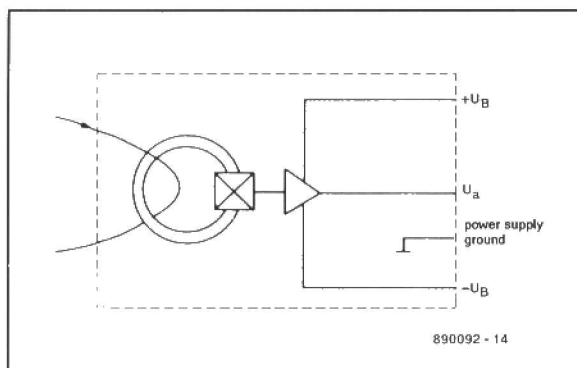


Fig. 4. Basic circuit of a direct-reading current sensor.

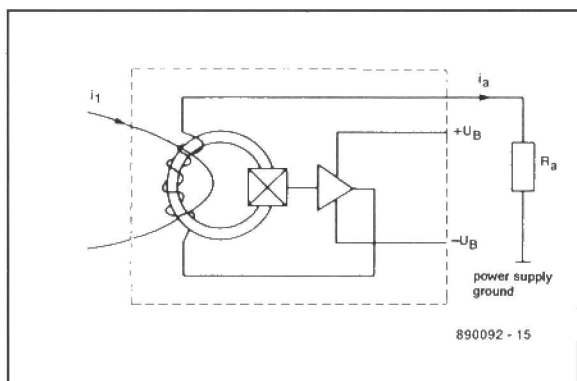


Fig. 5. In a compensating current sensor, the Hall element generates a current in a secondary winding.

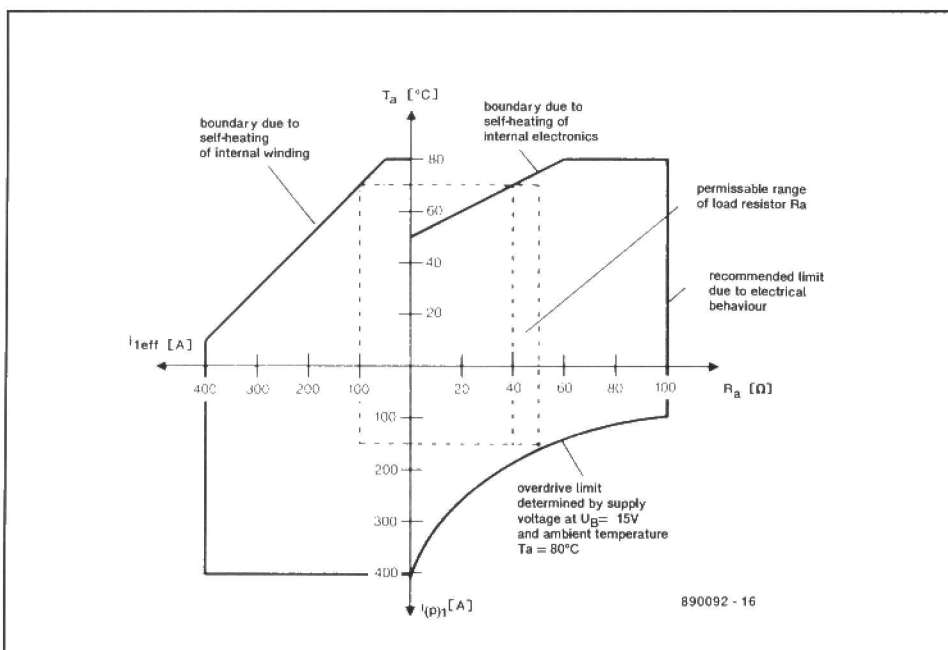


Fig. 6. The operating parameters may be determined from a four-quadrant diagram.

Parameter	Direct-reading	Compensating
Current rating	150–3000 A	100–250 A
Nominal output	10 V	100 mA
Nominal output impedance	10 k $\Omega$	50 $\Omega$
Supply current	15 mA	8 mA
Supply voltage	$\pm 15$ V	$\pm 15$ V
Ambient temperature	0–80 °C	–25 to +70 °C
Measuring accuracy	$\leq 2\%$	$\leq 0.5\%$
Linearity	$\leq 1\%$	$\leq 0.1\%$
Drift with temperature	$\leq 250$ ppm/°C	$\leq 50$ ppm/°C
Max frequency	10 kHz	75–300 kHz
Response time	$\pm 30$ $\mu$ s	$\pm 1$ $\mu$ s
<b>Output signal:</b>		
Offset	$\leq 20$ mV	$\leq 1$ mA
Drift	20–50 mV	0.05–0.1 mA
Hysteresis	$\leq 25$ mV	$\leq 0.2$ mA
Drift with temperature	$\leq 1$ mV/°C	$\leq 12$ $\mu$ A/°C
Drift with supply voltage	$\leq 0.1$ –10 mV/V	$\leq 0.01$ –0.03 mA/V

Table 2. Comparison of parameters of direct-reading and compensating sensors.

Note that in spite of the high value of  $v$  in indium antimonide this material is not used much because of the fairly large change in  $v$  with temperature: over the temperature range 20–120 °C, for example, the value of  $v$  changes by a factor 5.

## Practical sensors

In practice, the wafer thickness is of the order of 1–5  $\mu$ m, which not only gives a larger Hall voltage, but also enables the wafer to be

used in very small air gaps necessitated by weak magnetic fields. This may be seen in the schematic representation of a sensor in Fig. 3, in which the Hall voltage is directly proportional to the current flowing through a conductor that is perpendicular to the cross-sectional plane of the yoke of the sensor.

There are two types of Hall-effect current sensor: direct-reading and compensating—see Fig. 4 and Fig. 5.

The main advantage of the direct-reading type lies in the minimal losses it causes, which is, of course, particularly important when large currents are measured. The amplified output voltage,  $u_a$ , is directly proportional to current  $i_1$ .

The compensating type is particularly useful at higher frequencies—see Table 2. The current to be measured is coupled magnetically to a secondary winding on the yoke. The Hall element serves as a detector for the magnetic '0' which is induced with the aid of an auxiliary (compensating) current fed into the secondary winding. This compensating current is a very precise measure of the primary current. This type of sensor is eminently suitable for measuring square-wave currents.

Equivalent parameters of the compensating sensor may be determined from a four-quadrant diagram as in Fig. 6. If, for example, the r.m.s. value of the current to be measured is 100 A, its peak value is 150 A, and the maximum ambient temperature is 70 °C. Drawing lines at right angles to the three corresponding axes gives a load resistance of 40–50  $\Omega$ .

# VIDEO MIXER

## PART 2: MODULATION BOARD

A. Rigby & G. Dam

**Last month's introductory article described the general setup of the video mixer, and discussed the operation and construction of the video switching board. This month we turn our attention to the modulation board which supplies two sets of modulation waveforms that together put many attractive picture mixing, wipe, fade-in and fade-out effects at your disposal.**

As already discussed in Part 1 of this article, the video mixer consists of three blocks: a video switching board, a modulation board and a keyboard. These blocks form the basic configuration of the mixer as shown in Fig. 1 in last month's instalment. The modulation board and the keyboard receive a number of synchronization signals and the supply voltage from the video switching board. The keyboard circuit supplies all the necessary control signals to the video switching board and the modulation board.

### Effects waveforms

All picture mixing effects provided by the video mixer, and all combinations thereof selected by the user, are based on three elementary waveforms: the triangle, the ramp (linearly rising sawtooth) and the parabola. All three are available in the horizontal (line-synchronous) as well as the vertical (raster-synchronous) picture plane.

All picture mixing and combination effects rely on the switching between two video sources. A left-to-right wipe (curtain) effect, for instance, requires a circuit that switches between two video sources at accurately defined instants in the picture line. The HSW signal is used for this purpose. Similarly, the VSW signal is used if the wipe effect is required vertically (top-to-bottom). Both HSW and VSW are rectangular signals whose duty factor is controlled to obtain the wipe effect. The required duty factor variation is secured with the aid of a comparator that compares a ramp voltage to a reference voltage set with the wipe control (a slide potentiometer on the front panel of the video mixer). The other picture mixing and effects are obtained by combining different patterns, horizontally as well as vertically.

### Block diagram

The waveform generators for the mixing effects are shown to the left in the block diagram. The modulation board and the keyboard receive a number of synchronization signals and the supply voltage from the video switching board. The keyboard circuit supplies all the necessary control signals to the video switching board and the modulation board.

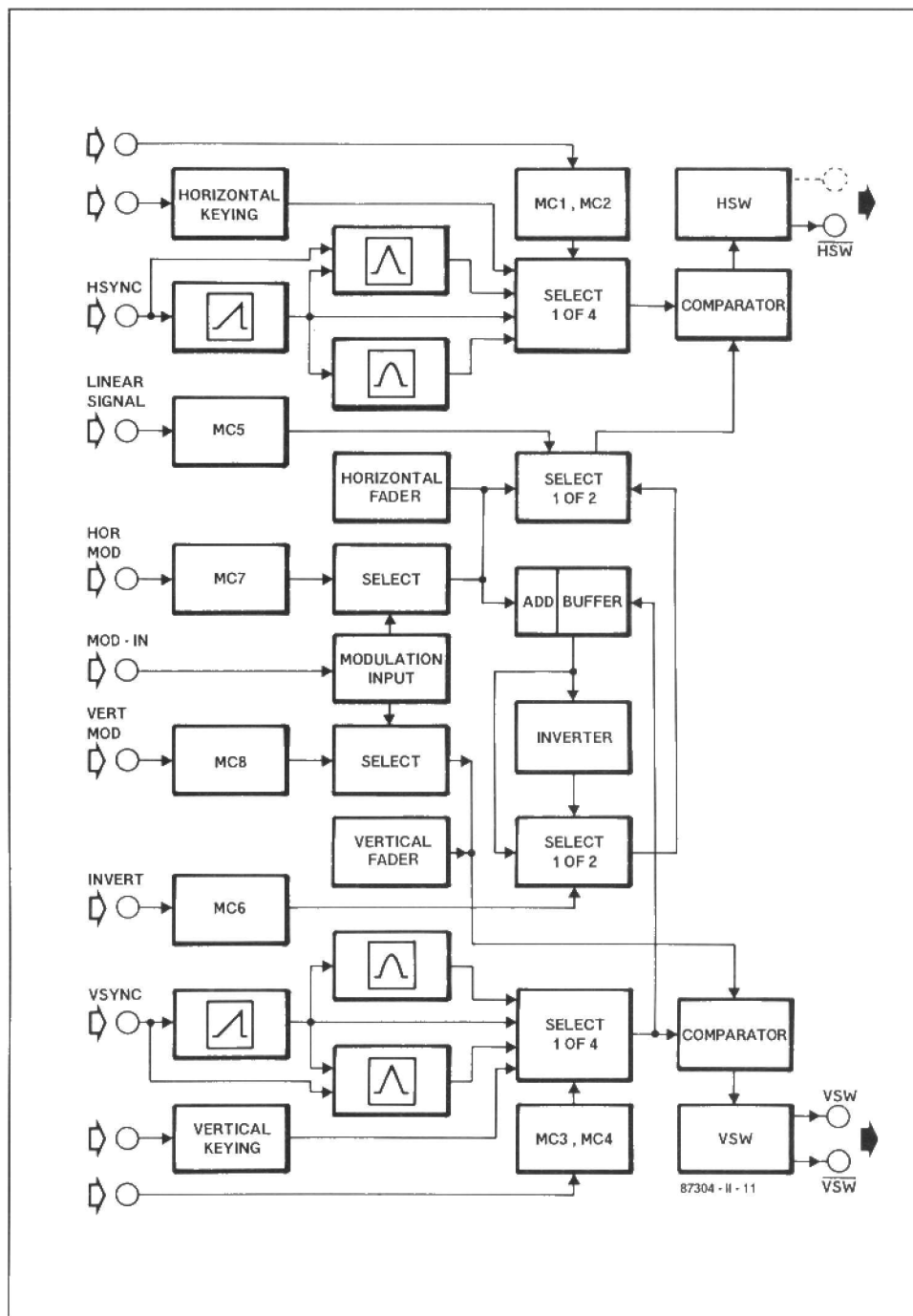


Fig. 6. Block diagram of the modulation board.

diagram in Fig. 6. Since the same waveforms are in principle required horizontally and vertically (only the frequency is different), almost identical generators are used. In both cases, the waveforms are synchronized with the video signal. The parabola- and triangle waveforms are derived from the ramp voltage. All three waveforms are applied to comparators via electronic switches. Depending on their function, the comparators supply either a horizontal (HSW) or a vertical (VSW) switching signal.

A separate modulation input allows additional control over the selected effect. The modulation signal applied to this input may be synchronous or non-synchronous in relation to the picture. Depending on the available video material and the applied waveform, remarkable and sometimes quite unpredictable effects may be obtained in addition to the ones normally provided by the video mixer.

The horizontal and vertical keying inputs, finally, enable 'home-made' patterns to be added to the picture.


A buffer and an inverter feed the selected vertical waveform to the horizontal comparator, which compares it to the waveforms generated in synchronism with the horizontal line pulses. The inverter may be switched on and off by a control on the keyboard. Depending on the levels applied to the comparator, an HSW signal is supplied that switches between two video sources at a particular instant in the picture line. This combination of vertical and horizontal waveforms allows fairly complex mixing effects to be realized.

The vertical waveforms are available in non-inverted as well as inverted form. The selection is made by the user with the aid of a keyboard control, and allows two video signals to be transposed on the screen. Taking the previously mentioned vertical wipe effect as an example, the invert control allows the 'top' and the 'bottom' pictures to change places in the mixed image.
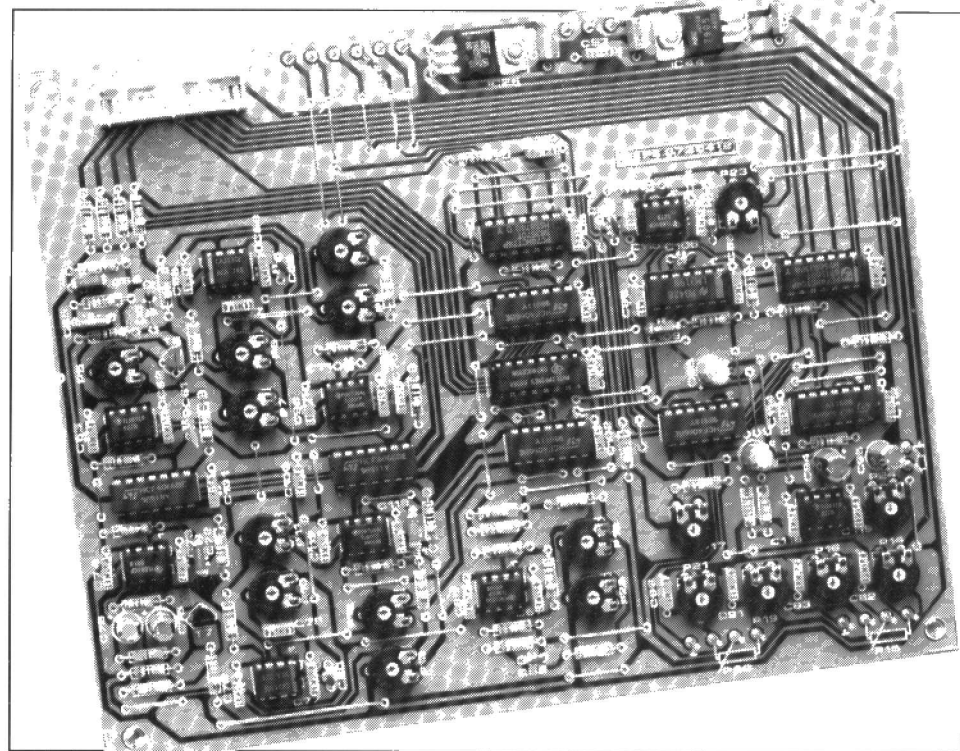
## Circuit description

The circuit diagram of the modulation board is given in Fig. 7. The three-stage horizontal waveform generator is shown in the top left hand corner. The almost identical vertical waveform generator is found in the lower left-hand corner. The following description of the operation of these circuits refers to the horizontal waveform generator, IC26-IC27-IC28-IC29a, T6 and IC40.

The HSYNC signal is applied to the waveform generator to ensure that this is synchronized with each picture line. During the HSYNC pulse, capacitor C61 is discharged via N47, so that integrator IC26 can start from zero at the end of the pulse. The result of the integration is a line-synchronous ramp voltage at the output of IC26. To produce a triangle voltage, the ramp is first converted into a rectangular wave by comparator IC27, which com-



pares the instantaneous amplitude of the ramp to the reference voltage at the wiper of preset P6. The rectangular signal so obtained is applied to integrator IC28a, which charges or discharges C70 as the output of IC27 goes high or low. The result of this second integration is a triangle voltage at the output of the opamp.

The horizontal synchronization pulse, HSYNC, causes the integrator capacitor, C70, to be completely discharged via N51 at the start of each picture line. Preset P6 determines the switching level of the comparator and with it the symmetry of the triangle voltage, while preset P7 sets the amplitude.

Transistor T6 converts the triangle voltage applied to its base via preset P5 into a parabolic voltage, which is subsequently amplified by IC28b. The amplitude and the off-set voltage of the parabolic waveform are adjusted with presets P8 and P9 respectively.

The vertical waveforms are obtained in a manner similar to the horizontal ones. However, the frequency is 50 Hz instead of 15,625 Hz, and VSYNC is used to ensure vertical synchronization to the mixed picture.

Demultiplexers IC29a and IC29b together determine the waveform selection for the mixing effects. This selection is accomplished in conjunction with electronic switches N52-N55 and N56-N59. Depending on the logic levels on control lines MC1-MC2 (IC29a) and MC3-MC4 (IC29b), either the ramp-, triangle-, parabola- or KEY- signal is used. The selected signal is applied to opamp IC34a for comparing to the voltage at the inverting input which takes either a steady voltage or one of the vertical waveforms.

The signal at the non-inverting input of IC34a is selected by electronic switches N61 or N63. To ensure that the effects selection remains in synchronism with the raster,

these switches are controlled in complementary fashion by bistable IC33b. The other bistable in the 74HCT74 package, IC33a, functions as a monostable multivibrator. It is clocked with VSYNC and supplies short pulses at its Q output. These pulses clock IC33b and time the instant it latches the logic level of control line MC5 connected to its D (data) input. The latched level is subsequently transferred to the Q and Q outputs.

The direct voltage supplied by the horizontal FADING control, P15, may be applied to the input of IC34a by switching on N63. The toggling of the HSW signal supplied by inverter N38 determines the border between the mixed pictures — in other words, the location (or instant) in the picture line at which the switching between the two video sources takes place. Presets P14 and P16 serve to give potentiometer P15 its maximum usable range, i.e., the width of the picture. Capacitor C84 allows an alternating voltage to be superimposed on to the direct voltage at the wiper of P15. This alternating voltage is taken from the external effects input and first buffered by IC37. If the external input is not used, the negative terminal of C84 is taken to ground by switch N66. This is done to prevent noise being picked up, which would cause interference in the mixed picture.

The modulation signal supplied by IC37 is also applied to comparator IC34b, which adds it to the direct voltage supplied by vertical FADING control P20. The selected vertical waveform is applied to the positive input of the comparator. The output signal is VSW or VSW which indicates the vertical (raster-synchronous) switching instant.

Series-connected opamps IC35a-IC35b-IC36 form a precision inverter or buffer for the vertical effects waveform selected by the user via N56 - N59. Presets P17, P18 and P22 are adjusted to cancel off-set voltages




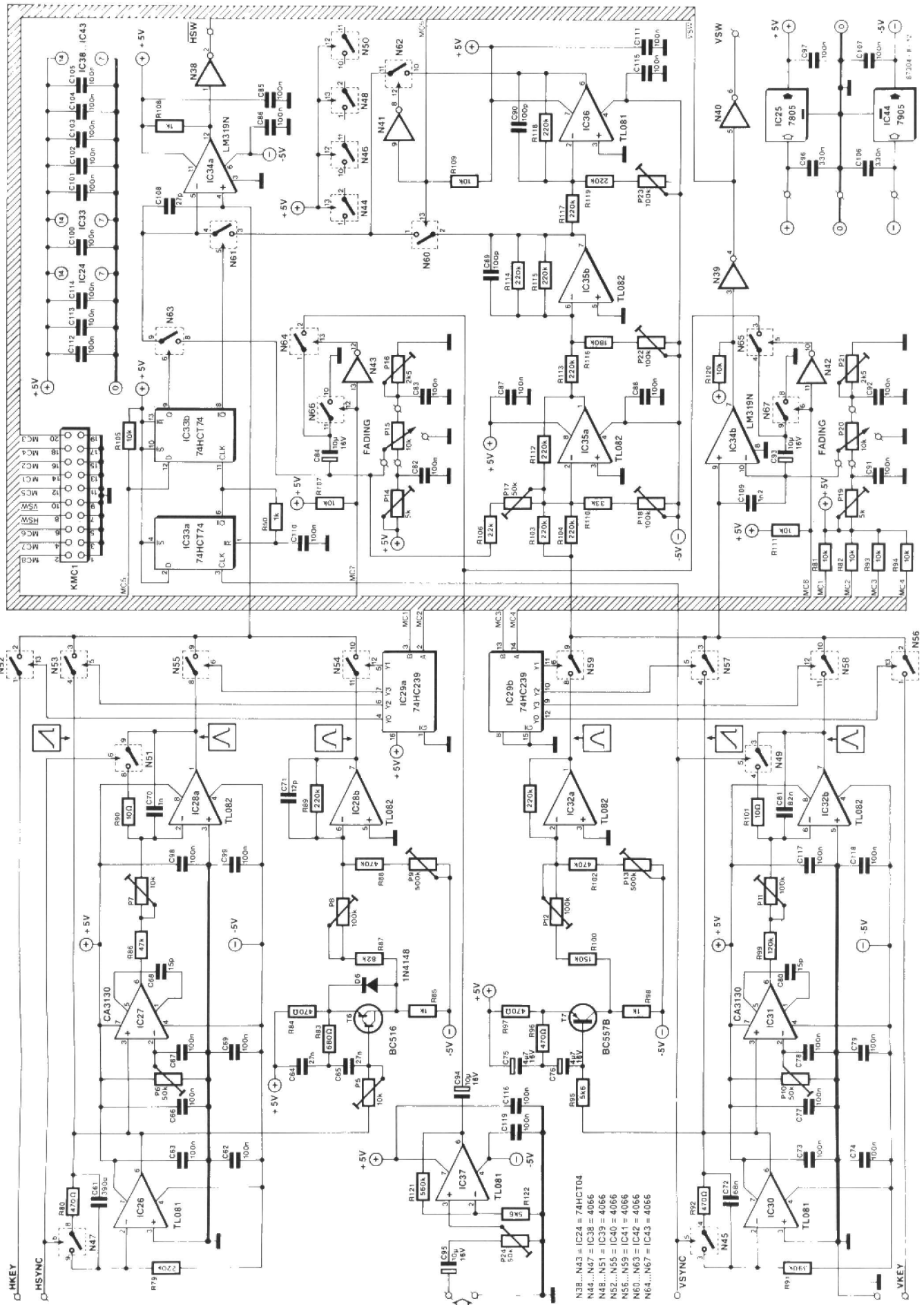


Fig. 7. Circuit diagram of the second unit in the video mixer, the modulation board.

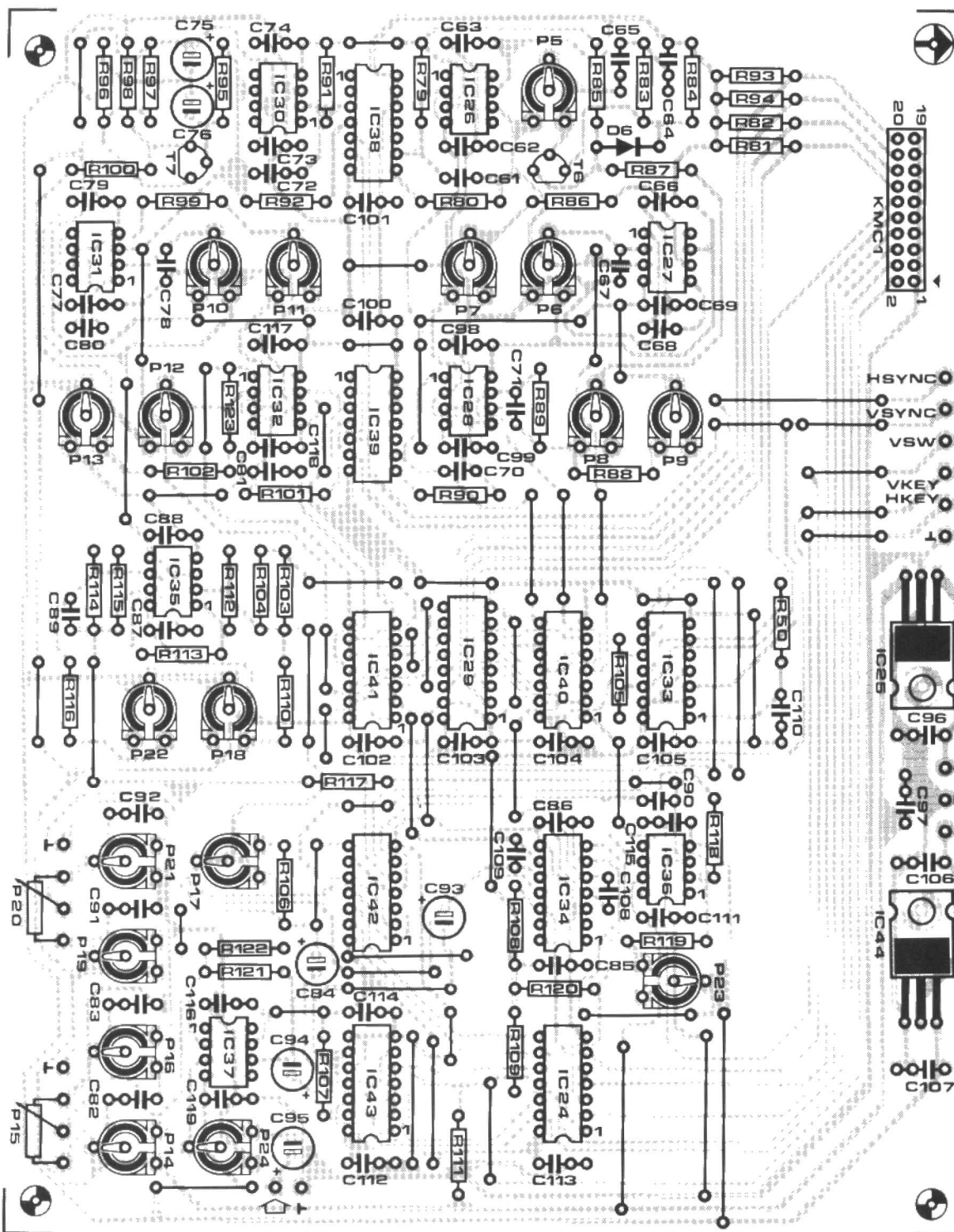

**Fig. 8.** Component mounting plan of the PCB for the modulation board.

in the three stages. The fairly extensive compensation is required to ensure that the output of IC36 supplies the exact inverse of the signal applied to the external effects input. Control line MC6 is used to select between the inverted and non-inverted version of the vertical effects voltage.

## Construction

The single-sided printed-circuit board for the circuit is shown in Fig. 8. Construction

should not present problems to the experienced electronics constructor at whom this project is aimed.

Start the construction of the board with fitting all the wire links. Next, mount the solder pins, connectors and IC sockets, if used. Check your work so far and proceed with the passive parts and the single diode. Be sure to observe the polarity of the electrolytic capacitors and the diode. Next, mount the voltage regulators and bolt them straight on to the board — heat-sinks are not required. Lastly, plug the ICs

in their sockets or, if sockets are not used, solder them direct on to the board. The slide potentiometers are mounted on to the keyboard PCB to be discussed in Part 3 of this article. Set all presets on the modulation board to the centre of their travel.

*To be continued next month*

Part 1 of this article appeared in the January 1990 issue of *Elektor Electronics*.

**Parts list****Resistors:**

R79 = 220k  
 R80; R84; R92; R96; R97 = 470Ω  
 R81; R82; R93; R94; R105; R107; R109;  
 R111 = 10k  
 R83 = 680Ω  
 R50; R85; R98; R108; R120 = 1kΩ  
 R86 = 47k  
 R87 = 82k  
 R88 = 470k  
 R89; R103; R104; R112 – R115; R117 – R119;  
 R123 = 220k  
 R90; R101 = 10Ω  
 R91 = 390k  
 R95; R122 = 5kΩ  
 R99 = 120k  
 R100 = 150k  
 R102 = 470k  
 R106 = 22k  
 R110 = 33k  
 R116 = 180k  
 R121 = 560k  
 P5; P7 = 10k preset H  
 P6; P10; P17 = 50k preset H  
 P8; P12; P11; P18; P22; P23 = 100k preset H

P9; P13 = 500k preset H  
 P14; P19 = 5k preset H  
 P15; P20 = 10k linear slide potentiometer  
 (not on PCB)  
 P16; P21 = 2k5 preset H  
 P24 = 50k preset H

**Capacitors:**

C61 = 390p  
 C82; C83; C66; C67; C69; C73; C74; C77; C78;  
 C79; C82; C83; C85 – C88; C91; C92;  
 C97 – C105; C107; C111 – C119 = 100n  
 C84; C65 = 27n  
 C68; C80 = 15p  
 C70 = 1n0  
 C71 = 12p  
 C72 = 68n  
 C75; C76 = 4μ7; 16 V radial  
 C81 = 82n  
 C84; C93; C94; C95 = 10μ; 16 V radial  
 C89; C90 = 100p  
 C96; C106 = 330n  
 C108 = 27p  
 C109 = 1n2

**Semiconductors:**

D6 = 1N4148  
 IC24 = 74HCT04

IC25 = 7805  
 IC26; IC30; IC36; IC37 = TL081  
 IC27; IC31 = CA3130  
 IC28; IC32; IC35 = TL082  
 IC29 = 74HC239  
 IC33 = 74HCT74  
 IC34 = LM319N  
 IC38 – IC43 = 4066  
 IC44 = 7905  
 T6 = BC516  
 T7 = BC557B

**Miscellaneous:**

KMC1 = 20-way PCB header.  
 PCB Type 87304-2 (see Readers Services page).

**IEE MEETINGS**

- 5 Feb — Evaluating student performance: key issues and strategies.
- 6 Feb — Integrating control system design with the analysis of flexible structures.
- 7 Feb — The role of venture capital in the UK electronics industry.
- 8 Feb — Broadcast TV recording.
- 8 Feb — Technical visit and discussion meeting at Colchester Technology Park.
- 12 Feb — The radio data system.
- 13 Feb — Safety critical software in vehicle and traffic control.
- 13 Feb — Data storage technology.
- 14 Feb — Stereo sound for television: implementation.
- 15 Feb — Interactive computing: a revolutionary medium for teaching and design.
- 20 Feb — Definition of traceability.
- 21 Feb — The interaction of radiowaves with the sea surface.
- 28 Feb — Safety regulations and codes for power and lighting in public areas.
- 28 Feb — Nucleonic instrumentation.

Information on these, and many other, events may be obtained from the **IEE, Savoy Place, LONDON WC2R 0BL, Telephone 01-240 1871.**

The **UKCMG** conference entitled “New dimensions in application development”

**EVENTS**

organized by the **UKCMG** in association with **Blenheim Online** will be held on 7–8 February at the Metropole Hotel, Brighton

The conference is designed to assist in making sense of the critical developments in the IT industry today. Application developers need to understand the issues inherent in the move towards high productivity development environments, the desire for open systems and application portability and the continuing trend towards more flexible and adaptable database management systems. Further details from **Blenheim Online, Blenheim House, Ash Hill Drive, PINNER HA5 2AE, Telephone 01-868 4466.**

**Frost & Sullivan** have organized a number of seminars for this month on **Information Technology; Telecommunications & Data Communications; and Electronic Engineering.** Details from **Frost & Sullivan, Sullivan House, 4 Grosvenor Gardens, LONDON SW1W 0DH, Telephone 01-730 3438.**

**CALL FOR PAPERS**

Papers are invited for the **Second International Conference on Rural Communications**, which will be held at the Institu-

tion of Electrical Engineers, London, on 29–31 October this year, and for the **Fourth Conference on Television Measurements**, which will be held in Montreux, Switzerland, on 20–22 June 1991. Details from **IEE, Savoy Place, LONDON WC2R 0BL, Telephone 01-240 1871.**

A number of courses are conducted by **Learning Tree International** between now and May in London, Stockholm, Paris, Los Angeles, Washington, Toronto and Ottawa. There are courses for “**Managers in technical environments**”, on “**Networks, Datacom and Telecom**”, and on “**Software Development and Systems**”. For further information phone 0800 282 353 or 01-748 6667 in London (fax 01-748 5005) or 08-18 99 00 in Stockholm (fax 08-18 99 07).

**Saudicom 90**, Riyadh's third electronics, communications and computer show takes place from 28 January to 1 February. All the giants of the industry such as **A T & T, Siemens, Ericson, British Telecom, Telettra, Plessey, France Telecom, Aerospatial, Alcatel, Telecom Australia International**, and others, will be there. Further information from **Overseas Exhibition Services Ltd, 11 Manchester Square, LONDON W1M 5AB, Telephone 01-486 1951.**





soldered, but if the board is fitted in an enclosure, preference should be given to the use of 2.5 mm plugs and sockets.

## Connecting up and actuating the inputs

Monitor units are interconnected via K1 and K2. The arrow shown near these connectors in Fig. 70 must always point to the mother board. If this is not observed, the system will not work, although nothing more disastrous will happen.

All connector pins must be connected to the same numbered pin on the connectors in other units, preferably by the use of ready-made non-twisted, 5-core DIN cable. The total length of cable between the units is of no importance to the correct operation of the system.

In principle, a monitor unit is actuated when the brown wire or rail of the system is connected to earth. For this purpose, two earthing points are provided on the PCB. It is also possible to actuate it by connecting an input to the red wire of the system, but not if the system is in the STOP mode.

## Electronic train detection

Signalling to and from locomotives and coaches is often performed with the aid of reed relays. Both from a technical and an aesthetic point of view, this is not a good way of doing it: electronic means are invisible and seldom fail (which can not be said of reed relays).

If Märklin rails are used, M-sections are available in which one rail is isolated from the 'metal gravel' base. This isolated section is simply connected to one of the inputs of a monitor unit.

Where K-rails (which are isolated from each other) are used, a section of one rail may be isolated from that rail by two saw cuts as shown in Fig. 72. The length of this

section should be at least as long as the largest wheel base of locomotives and coaches used: this results in one long signal instead of a series of shorter ones. Cut the rail at an angle rather than straight across: in that way trains will have a smoother ride over the section.

Where a standard rail system is used, the detection methods shown in Fig. 74 or Fig. 75 should be used.

The isolated section of rail in Fig. 74 is powered via two anti-parallel-connected diodes. It does not matter whether the diodes are connected to the brown or the red terminal. Rails sections from which no signal is required may be connected direct to the booster unit.

A disadvantage of the method in Fig. 74 is that only powered rolling stock can be detected. If a train loses one or more coaches, these will be 'invisible' to the system. Therefore, the circuit in Fig. 75 may be preferred. The output of the comparator in that circuit is actuated when a relatively high resistance exists between the two rails. By providing coaches with a 10 k $\Omega$  resistor as shown in Fig. 76, they can also be detected by monitor units.

## Status requests

The status of monitor units can be requested only via the RS232 interface. After power-up or a reset, one or more groups of two bytes from two successive monitor units (that is, groups of 16 inputs) are sent in response to each status request instruction. This is done in this way to ensure full compatibility with the Märklin Digital System. However, as explained in Part 10, if desired, the monitor units may be made to react individually.

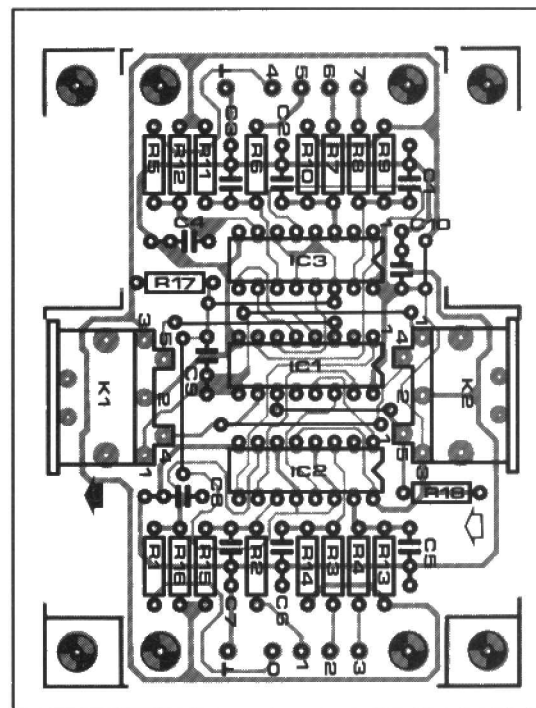


Fig. 71. Printed circuit board for the monitor unit.

### COMPONENTS LIST

#### Resistors:

R1-R8 = 10 k  
R9-R17 = 100 k  
R18 = 47 k

#### Capacitors:

C1-C8 = 10 n  
C10 = 100 n

#### Semiconductors:

IC1 = 4014  
IC2, IC3 = 4044

#### Miscellaneous:

K1; K2 = 5-way DIN connector for PCB mounting  
Enclosure: OKW Type A9407111  
10 pairs of 2.5 mm plugs and sockets (see text)  
PCB Type 87291-8

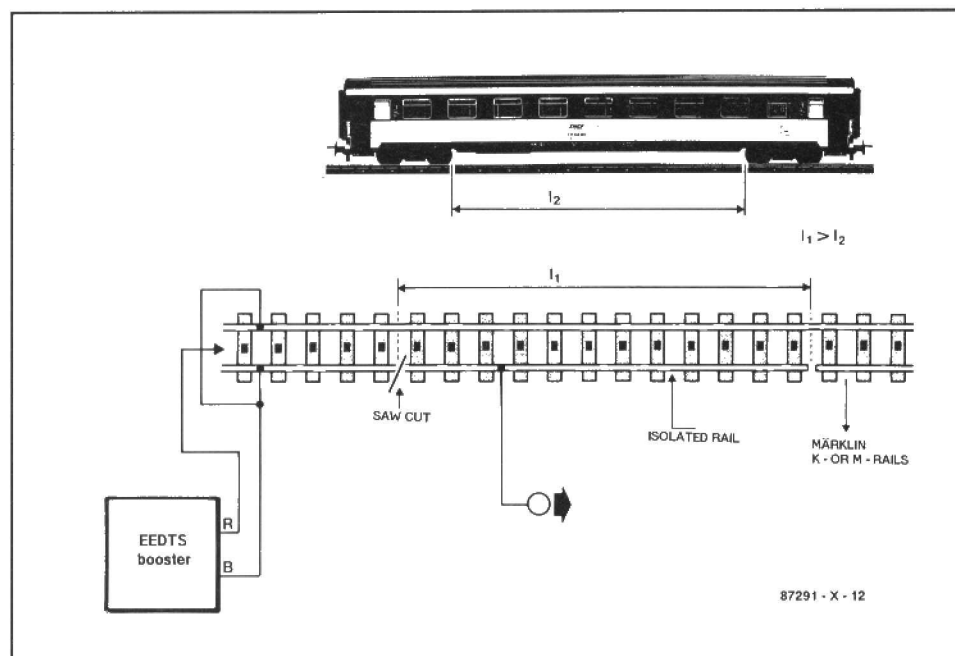


Fig. 72. How to connect an isolated section of the track to a monitor unit (black arrow points to input on monitor unit). In the illustration, use is made of Märklin rails.

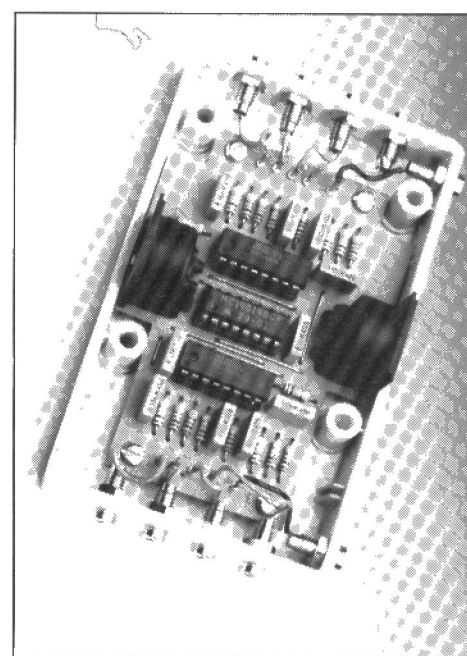


Fig. 73. The finished board fitted in the specified enclosure; note the cut-away corners.

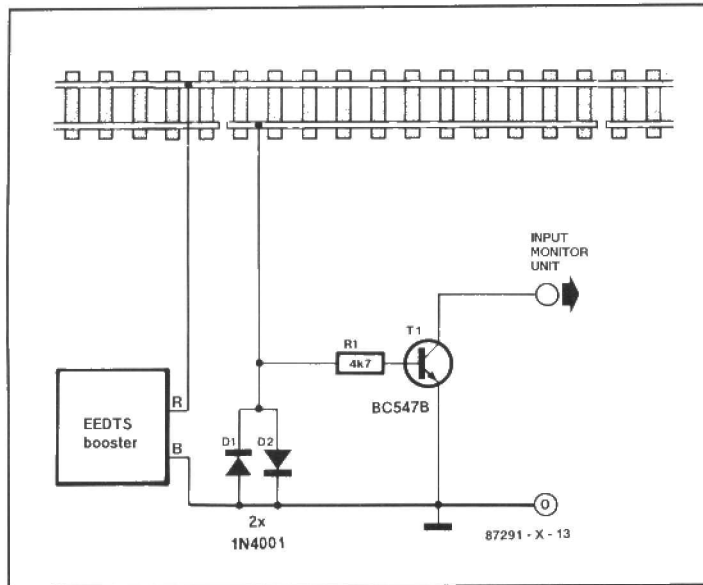


Fig. 74. This circuit for electronic train detection can locate only powered rolling stock (locomotives and coaches with lighting).

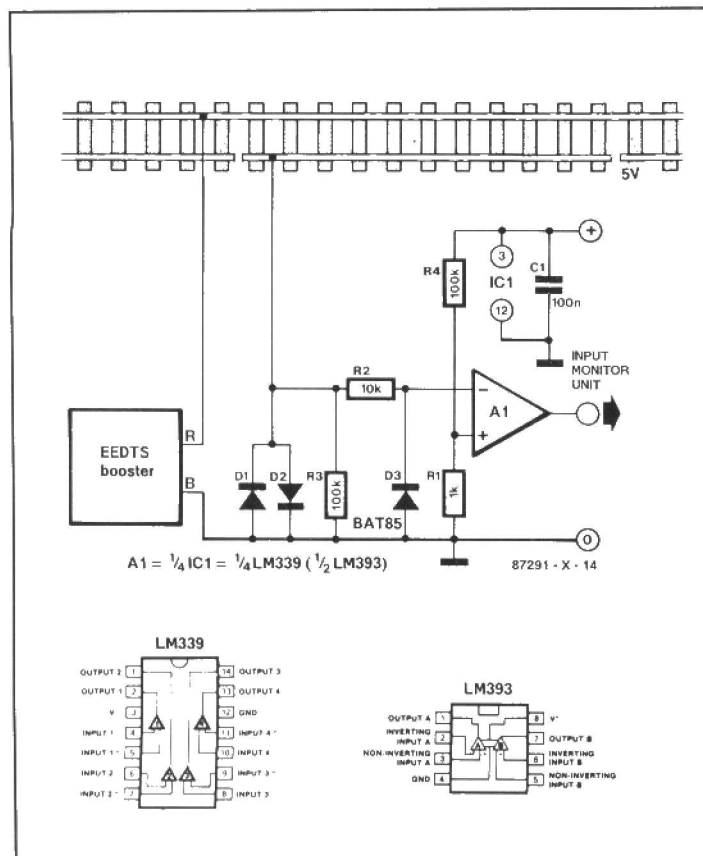


Fig. 75. Circuit of a sensitive detector system that is actuated by a relatively high resistance between the two rails.

## System miscellany

### Locomotive decoders (Part 2).

It appears that loc decoders can be affected by switching instructions intended for points and signals. This can be prevented by increasing the value of R1 from 12 kΩ to 33 kΩ or even 39 kΩ.

### Switching decoders (Part 4).

An error has occurred in the circuit diagram and components list. Circuits IC5 and IC6 should be Type ULN2003 and not ULN2001 as stated. The decoder will work

with the ULN2001 but not entirely to specification.

### Using more than one booster (Part 6).

If the size of the track makes it necessary for several booster units to be used (when each booster powers a section of the track), a small addition is necessary to provide adequate overload protection. The circuit for this is shown in Fig. 78. It is basically a composite OR gate that detects overloads in up to five booster units. If any one booster unit becomes overloaded, the entire system is placed in the STOP mode.


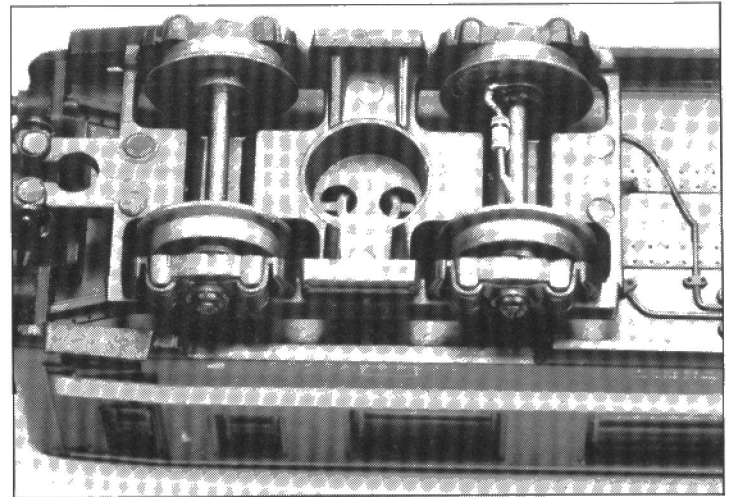


Fig. 76. Providing non-powered rolling stock with a 10 kΩ resistor enables it to be detected with the aid of the circuit in Fig. 75.
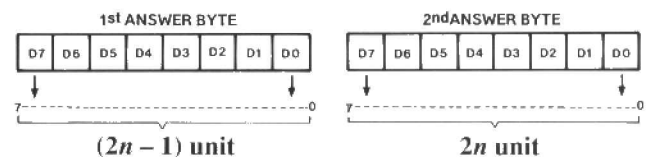
### Request instruction <192+n> (n = 1–31)



2nd answer byte only with Märklin emulation (default at power-up and reset)

Fig. 77. Composition of bytes sent by the system in response to a status request via the RS232 interface.

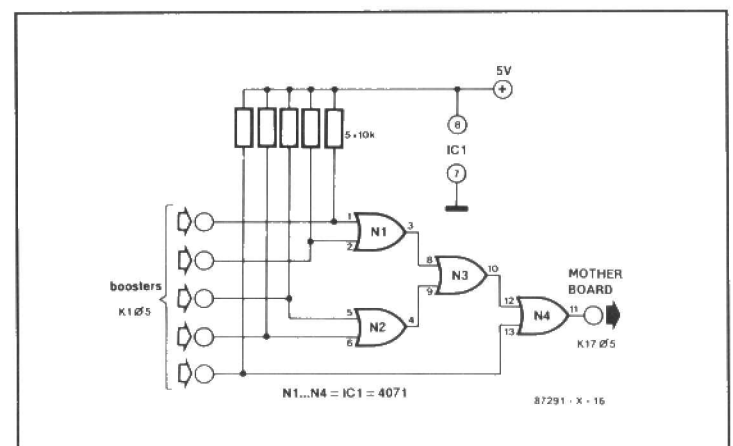


Fig. 78. Additional circuit for obtaining proper overload protection when more than one booster is used.

### Parts published so far.

- Part 1. Märklin system (description).
- Part 2. Loc decoder (description).
- Part 3. Loc decoder (construction).
- Part 4. Universal signal and switching decoder.
- Part 5. Description of Elektor Electronics system.
- Part 6. Booster unit.
- Part 7. Mother board (description).
- Part 8. Mother board (construction).
- Part 9. Keyboards.
- Part 10. RS232 Interface.



# INTERMEDIATE PROJECT

A series of projects for the not-so-experienced constructor. Although each article will describe in detail the operation, use, construction and, where relevant, the underlying theory of the project, constructors will, none the less, require an elementary knowledge of electronic engineering. Each project in the series will be based on inexpensive and commonly available parts.

## 8. Reflex MW AM receiver

J. Bareford

Radio techniques even at the most fundamental level will continue to fascinate electronics enthusiasts because a handful of components work the miracle of wireless reception. This month we save a once popular circuit from oblivion. The radio fascination catches on with this reflex AM receiver, sporting one tuned circuit for medium-wave reception.

The so-called direct conversion receiver forms the basis of all radio receivers. In its most rudimentary form, it provides an aerial input, a tuned circuit to select the wanted RF signal from many others transmitting in the same band, and a detector to extract the modulation signal (i.e., the information) from the carrier. In a more elaborate design, an RF- and an AF-amplifier may be used before and after the detector respectively. The direct conversion receiver differs from the superheterodyne receiver in that it does not use frequency conversion of the received RF signal at any stage. Although the direct conversion receiver can not stand com-

parison with the selectivity of the superhet, it is none the less interesting to build as a first ever electronics project. Again making the comparison with the superheterodyne receiver, the direct conversion type is inexpensive, uncritical, and free of interference effects. What is more, it provides quite acceptable sound quality.

### Flashback or start

The circuit diagram of the simplest of receivers, the direct conversion type without RF or AF amplification, is shown in Fig. 1. The combination of an inductor in parallel with a variable capacitor forms a tuned circuit that resonates at the transmit frequency of the station to be received. One side of the tuned circuit is connected to ground, the other side to a small capacitor that takes the RF signals from a long-wire aerial. The detector, a semiconductor diode, is connected to a tap on the inductor. This is done to reduce the loading (damping) effect on the tuned circuit, which would degrade the selectivity. The RF component, i.e., the carrier, is shorted to ground by a capacitor at the anode of the diode. The resulting AF component can be heard in the high-impedance earpiece connected across the capacitor. The one advantage of the circuit in Fig. 1 is that it does not require a supply voltage. The disadvantages, however, are more important: sensitivity is poor, and the AF output signal is too small in many cases.

The addition of a FET (field-effect transistor) and a resistor as shown in Fig. 2 results in a better receiver. The FET provides considerable AF amplification and at the same time, by virtue of its high input impedance, allows the detector to be connected to the 'top' of the tuned circuit. This makes this type of receiver fairly sensitive.

It is definitely worth while to build the circuit of Fig. 2. A few hints: use a wire aerial of at least 5 metres, and connect ground of the circuit to the water supply

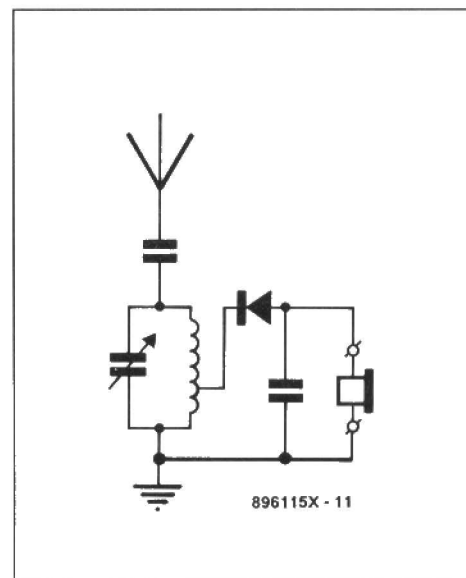


Fig. 1. The one advantage of the diode receiver is that it does not need a power supply. The circuit is, however, useless without a large aerial and an earth connection.


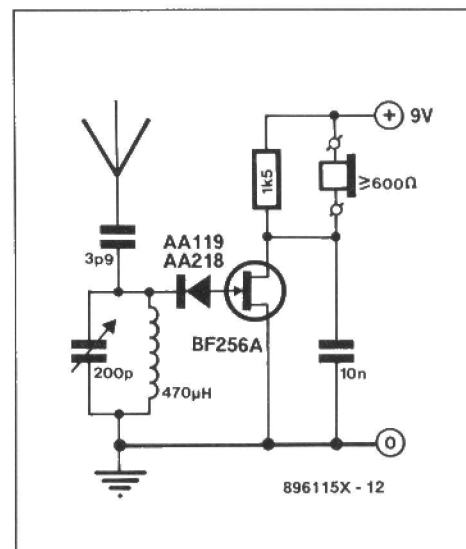


Fig. 2. The amplifier in this modified diode receiver raises the sensitivity of the basic design considerably.

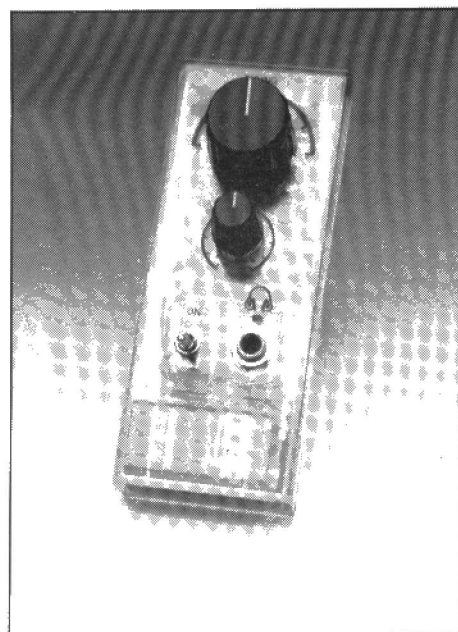

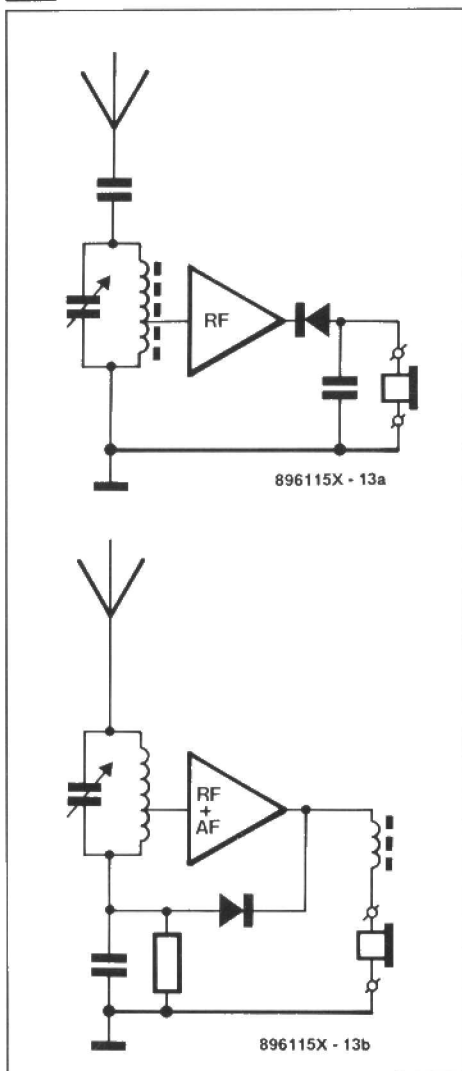


Fig. 3. Extending the direct-conversion receiver with an amplifier for RF signals only (3a) and one that provides gain for RF as well as AF signals (3b).

or the central heating system. The inductor is made by winding 85 turns of 0.2 mm diameter (SWG36) enamelled copper wire on a 10-cm long ferrite rod. The receiver draws about 4 mA from the 9 V battery.

## RF amplification

It will be clear that an RF amplifier as drawn in Fig. 3 is required if the receiver in Fig. 2 is to work with a much smaller (shorter) aerial, and without the connection to earth via the water supply or the domestic CH system. Also note that the germanium diode has a threshold voltage of about 200 mV, which makes reception of signals below this level impossible — weaker signals are simply not detected. If the RF amplification is high enough, the tuned circuit may double as an aerial, obviating the long wire. A second tuned circuit, identical to the one already used, may be added to improve the selectivity. A further improvement that requires no extra components is shown in Fig. 3b. A choke is connected to the output of the RF amplifier, and the detector is not connected to the headphones, but fed back to the 'cold' side of the tuned circuit. The result of this configuration is that the am-

plified RF signal is 'forced' towards the detector because it is blocked by the choke. After detection, it is applied to the input of the amplifier. Since the choke does not present a high reactance to AF frequencies, the amplifier raises the demodulated signal to a level suitable for driving earphones. In other words: RF and AF amplification are provided by a single amplifier. This forms the principle of the reflex receiver.

## Enter two MOSFETs

Transistors are available today that improve the performance of the good old reflex receiver considerably. Figure 4 shows the circuit diagram of a receiver based on the reflex principle and developed as a result of many experiments. Dual-gate MOSFETs Type BF981 are used. One functions as an AF amplifier that obviates passive components, and the other as an AF/RF amplifier with very high input impedance.

The heart of the receiver is formed by T1. Resistors R3 and R5 provide the gate-2 bias voltage, which is decoupled by C4. Capacitor C5 similarly decouples the drain voltage. The tuned circuit of the receiver is formed by L1-C1. The inductor is wound on a small ferrite rod which forms the aerial. The RF signal at the 'top' of the tuned circuit is fed to gate-1 of the MOSFET via C1. The extremely high gate impedance of the transistor eliminates all likelihood of damping, and obviates a tap connection or a coupled winding. All this simplifies the construction of the inductor and increases the sensitivity of the receiver because at the same (high) load resistance, the voltage at the top of the tuned

circuit is higher than at a tap towards the earthy side. The RF signal amplified by T1 is blocked by L2 and consequently arrives at detector D1-D2-C3-R2 via coupling capacitor C3. The detector also functions as a voltage doubler circuit. Resistor R1 feeds the rectified signal back to gate-1 of the MOSFET, which functions as an AF amplifier. The amplified AF signal passes through L2 and is coupled out via C7 to the volume control, P1. Transistor T2 raises the AF signal to a level suitable for driving lightweight headphones.

## Compact

The low number of components and the use of a small ferrite rod enables the reflex

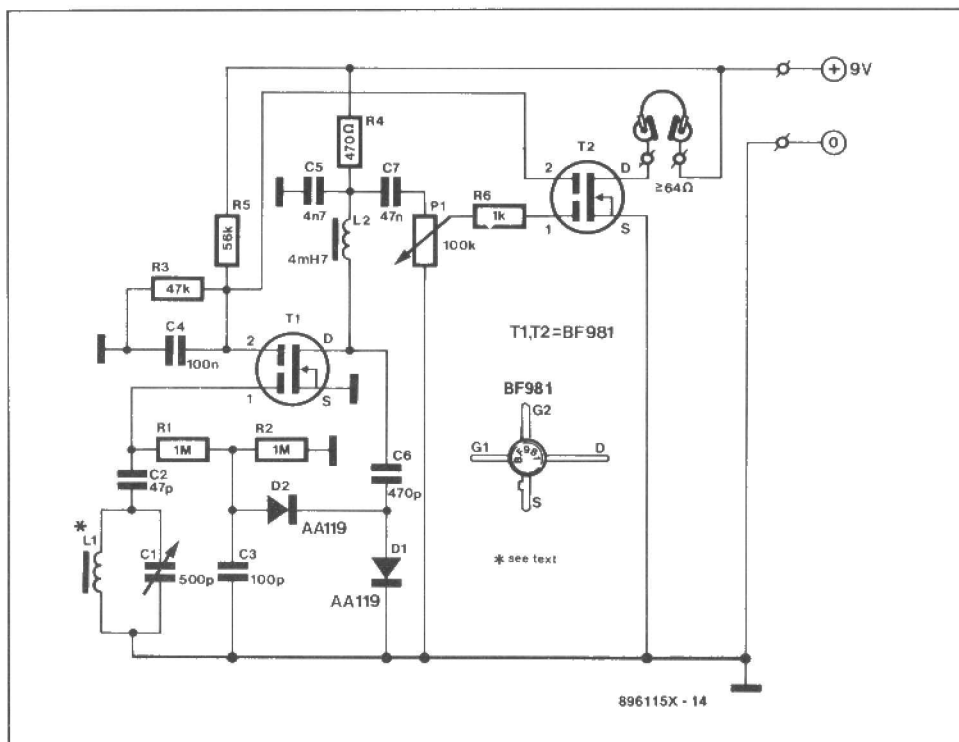


Fig. 4. Circuit diagram of the reflex receiver based on dual-gate MOSFETs. The L-C tuned circuit at the input doubles as a compact aerial for medium-wave reception.

receiver and the 9 V battery to be built into a miniature enclosure of the size of, say, two match boxes.

If you consider size less important and at the same time want to go round constructional problems, build the circuit on Universal Prototyping Board Size-1 as shown in Fig. 5. Pay attention to the orientation of the MOSFETs: when in doubt look at the pinning given in the circuit diagram (transistor viewed from the top). Choke  $L_2$  is a ready-made type. The aerial is made from 70 turns of 0.2 mm diameter (36SWG) enamelled copper wire wound on a 4-cm long, 10-mm diameter ferrite rod. The rod is secured on to the PCB with the aid of plastic ties as shown in the photograph. The two diodes may be replaced by almost any other small-signal germanium type such as the OA90 or OA95. Do not use silicon types: their threshold voltage is too high for this application.

The receiver is connected to a pair of headphones with a minimum impedance of 64  $\Omega$ . This perhaps less usual value is simple to achieve by connecting the two 32  $\Omega$  earpieces of the headphones in series.

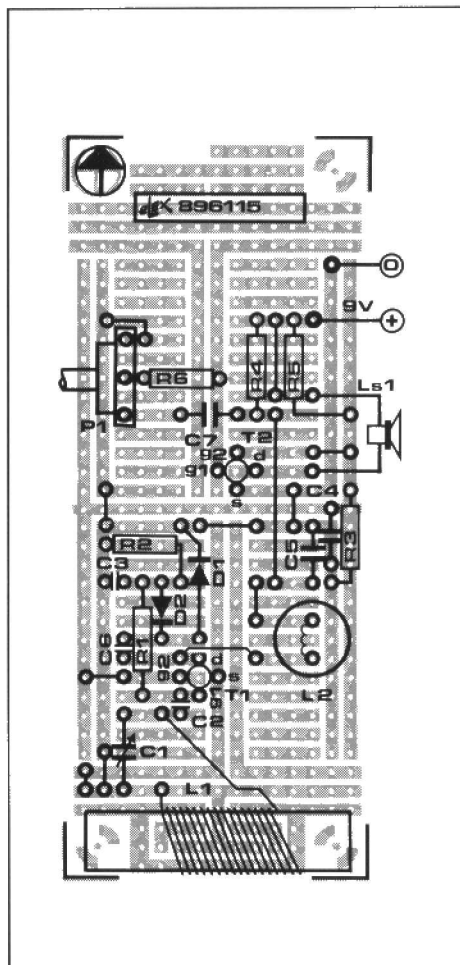


Fig. 5. Suggested construction of the receiver on ready-made PCB Type UPBS-1.

#### Parts list

##### Resistors:

$R_1, R_2 = 1M\Omega$   
 $R_3 = 47k$   
 $R_4 = 470\Omega$   
 $R_5 = 56k$   
 $R_6 = 1k\Omega$   
 $P_1 = 100k$  logarithmic potentiometer

##### Capacitors:

$C_1 = 500p$  mica foil tuning capacitor +  
 $C_2 = 47p$   
 $C_3 = 100p$   
 $C_4 = 100n$   
 $C_5 = 4n7$   
 $C_6 = 470p$   
 $C_7 = 47n$

##### Semiconductors:

$D_1, D_2 = AA119$   
 $T_1, T_2 = BF981$  +

##### Inductors:

$L_1 =$  wound on ferrite rod + (see text)  
 $L_2 = 4mH7$  choke, e.g., Toko 181LY-472 +

##### Miscellaneous:

$S_1 =$  miniature on/off switch.  
 Headphones; impedance  $\geq 64\Omega$  ( $2 \times 32\Omega$ )  
 PCB Type UPBS-1 (see Readers Services page).

+ Suggested supplier: Cirkuit, Park Lane, BROXBORNE EN10 7NQ. Telephone (0992) 441306. Fax (0992) 464457.

## Hard disk monitor

December 1989, p. 54

The parts list is not in agreement with the circuit diagram, and should be modified to read:

$R_1 - R_7; R_{11}; R_{13} - R_{16}; R_{20} = 100k$   
 $C_1 - C_{11} = 22n$

## Simple transmission line experiments

September 1989, p. 38

The value of  $R_2$  in the experiment should be 225  $\Omega$ , not 43  $\Omega$ .

## Logic analyser with Atari ST

October 1989, p. 30

Please add to the parts list:

$R_3; R_4; R_5 - R_{12} = 100k$   
 $C_6 = 100n$

The control program (ESS111) is suitable for monochrome systems only.

## LF/HF signal tracer

December 1989, p. 22

The resistor next to preset  $P_3$  on the printed-circuit board should be labelled

## CORRECTIONS

$R_{23}$ , not  $R_{36}$ .

### I/O extension for Archimedes

November 1989, p. 14-15

The parts list should be modified to read:  
 $IC_3 = 6522-2$

The circuit diagram in Fig. 2 contains an error:  $R_4$  should be connected between ground and the +input of  $IC_1$ . The printed-circuit board is all right and requires no modification.

### Intruder alarm

November 1989, p. 45-47

The references to  $C_3$  in lines 6 and 7 of the last full paragraph on page 45 should read  $C_1$ .

The reference to  $R_5$  in the third paragraph under Alarm sensing should read  $R_9$ .

The first full sentence in the centre column on page 47 should read

'Two assurance beeps are generated:

one at the instant of switch-on, and one as the exit door is opened for departure before the end of the 15-s switch-on delay.'

In the circuit diagram, Fig. 2, the diode across  $B_{z1}$  should be numbered  $D_{10}$ , not  $D_{12}$ . Capacitor  $C_2$  is missing: it is an 10  $\mu F$  electrolytic type connected between the +12 V and ground rail. Finally, the inset text ' $D_1...D_8 = 1N4148$ ' should read  $D_1, D_2, D_3, D_5, D_6, D_7, D_8, D_{10}, D_{12} = 1N4148$ .

### 3 1/2-digit SMD voltmeter

November 1989, p. 37-41

The obsolete half-digit LED display Type HD1108 from Siemens may be replaced by Telefunken's Type D29xPK, where 'x' indicates the colour: 0 for red, 1 for amber, 2 for green and 3 for yellow. These displays are also available under new type indications as TDSR3120, TDSO3120, TDSG3120 and TDSY3120 respectively. Telefunken also manufactures equivalents for the HD1105: the type numbers are TDSR3150, TDSO3150, TDSG3150 and TDSY3150.

Distributor information on Telefunken components from AEG (UK) Ltd. • 217 Bath Road • SLOUGH SL1 4AW. Telephone: (0753) 872101. Fax: (0753) 872176.

(X) = CORRECTION NOTES ADDED TO MAGAZINES CONCERNED




# READERS' FORUM


## LETTERS

Dear Sir — With reference to the December 1989 issue of *Elektor Electronics*, I would like to comment on two of the projects.


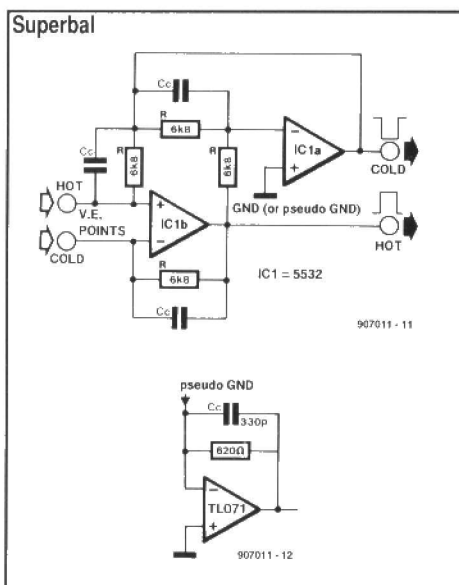
1. "Solid-state preamplifier". This project is very good as far as it goes. The virtual earth CMOS switches have been used for some years on audio mixing consoles to great effect.



## CMOS switches

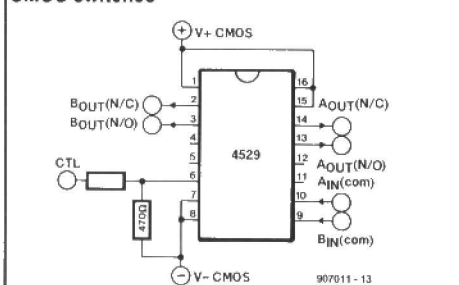

## and their functional equivalent

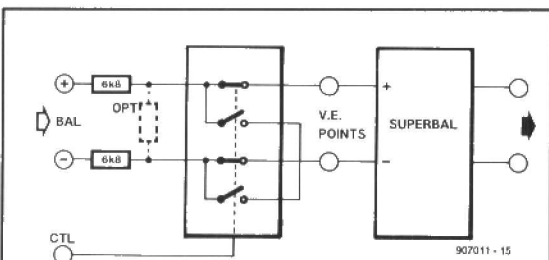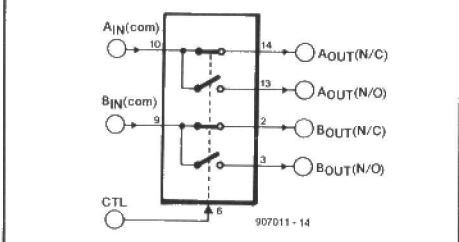

CMOS powered from  $\pm 6$  V; opamp powered from  $\pm 20$  V. This gives several 10s of dB headroom!

An enhancement that I would personally like to see is the inclusion of active, symmetrical balanced inputs and outputs — I have for some time been toying with a theoretical design based on a circuit element called a 'superbal'.

I can lay no claim to originating this circuit (in fact, it came from Messrs Stancoil, the manufacturers of Alice mixers, who are no longer in business), but I have several circuits roughed out that incorporate this element.

I enclose the following sketch of the element together with the proposed CMOS switch circuit.

2. "IC tester for the IBM PC". I have recently constructed this project with no problems at all. A few hardware enhancements were incorporated as follows:

(i) the address selection links were replaced by a four-pole DIP switch to facilitate later changing of the base address;

(ii) the ZIF socket and LED were built into a small plastic box along with another 25-pin D-connector to tidy up the test PCB;

(iii) the ribbon cable from the main board to the test PCB was discarded in favour of a standard 25-way D-connector computer cable.

While the hardware cannot be faulted, the software supplied is not quite so bug free.

As far as I can tell, there are no problems with the interpreter, but the library files contain several errors. I have since had two further copies of the software; although these correct some omissions, other errors still exist.

Perhaps you might consider an occasional article on listings for test routines for ICs other than those contained in my list attached.

A.G. Crane, Kings Lynn.

Your sketches are reproduced here, since I feel that these will of interest to a number of other readers (they certainly were to me). Also, all your comments have been forwarded to the designer of the "All-solid-state preamplifier". Any comments from him will be published in a future issue.

As regards the software bugs, your list has been forwarded to ELV, the designers of the IC tester. As soon as we have their comments, we will publish your list and their response, if any. [Ed]

Dear Sir — I have just received the October 1989 issue of *Elektor Electronics* and am surprised to note that you are charging £2.00 for

a paper copy of a PCB pattern to addresses outside Europe. This is rather unfair on readers like me. I like to keep records of PCBs for future use and have tried to do so from issue 1 of *Elektor Electronics*.

1988 was a bad year for PCB patterns. Many articles did not have a PCB pattern, only a component layout diagram. If I have to pay out £2.00 for every PCB pattern, I may have to dish out £40–£60!

Even copies of articles are £2.50 per article, not per page. Why can't a similar standard be used for PCBs? Most PCBs don't even fill half a page!

Again, what you are doing is unfair and painful — please be more reasonable.

K.G. Vergis, Likas, Malaysia.

*First, it appears as if you think that the basic prices charged to customers outside Europe are different from those to customers in the UK or Europe: this is not so — the differences in prices are caused by the different postage rates for these areas.*

*The processing of a PCB layout on paper costs about £1.20 (internal handling of order, placing order on central computer store, packing, and so on). Surface mail postage is the same the world over and amounts (on average) to £0.35; airmail charges outside Europe amount (on average) to £0.75.*

*The processing of a PCB layout on film costs about £5.00 (making of the film is around £4.00, the rest is as for the paper layout, although the packing is slightly more expensive). Postage rates are as for the paper layouts.*

*We have no desire of making a profit on this service to our readers and other customers.*

*The reason that in general we do not publish the PCB track layout in the magazine is that it serves no purpose to the constructor who is only interested in the component layout. It is impossible to produce a PCB from the track layout published in the magazine (because of the printing on the reverse page).*

*I do sympathize with your feelings, but unfortunately we all live in a harsh commercial world: we wish we could supply these track layouts free of charge, but it's just not feasible without increasing the cost of the magazine. None the less, in some special cases, such as schools and colleges, I may be able to make special arrangements.* [Ed]

Dear Sir — Regarding "DC-DC power converter" (November 1989, p. 54), don't you think it is irresponsible to publish a power supply circuit that is not short-circuit protected. A car battery will easily

provide a hundred or more amps, quite sufficient to destroy this circuit and most of anything that had the misfortune to be connected to it.

The author claims that power rises exponentially with current. When I went to school, power was directly proportional to the square of the current. I do not believe this has changed.

Is skin effect really significant at the audio frequencies which the author suggests are used? At 20 kHz, the skin depth might be of the order of 0.5 mm. If this is significant, the author should justify his claim.

B.A. Jones, Cheltenham.

*Mr Jones has further pointed out that the point of his constructive criticism was that many of those attempting to construct projects published in Elektor Electronics are beginners who need everything explained in detail, a sentiment with which I agree wholeheartedly, and which will certainly be borne in mind in future.*

*The author comments: "The article states clearly that the converter is not protected against short-circuits and that a 16 A fuse must be inserted between it and the battery. On reading Mr Jones' comments, it might perhaps have been better to have shown this fuse in the circuit diagram but, as a rule, parts that are not on the PCB are not shown (to maintain the proper relation between parts list, board and circuit). Moreover, the provision of short-circuit protection would have increased the cost and complexity of the converter".*

*"It is true that a car battery can supply very high currents, but long before these have risen to unacceptable levels, the 16 A fuse, and possibly resistors R2 and R3, choke L1 and diode D1, would have given up the ghost. Moreover, 'anything which had the misfortune to be connected to it (the converter)' will not be damaged by a short-circuit at the output terminals of the converter, since its input voltage is then zero".*

*"What you have learned at school about the relationship between current and power and what I say about it are not in disagreement. I feel you may have confused the adjectival and noun uses of the word 'exponential'. Any parameter that varies in accordance with the power of a quantity does so 'exponentially', whether that power is 2, 5 or  $e$  ( $\approx 2.72$ ). Only when the power is 1 do we speak of direct (linear) proportionality". (Note: I agree with Mr Jones (in a follow up letter) that the words 'exponent' and 'exponentially' are well defined in mathematics and should not be changed 'at the drop of a hat'. Ed).*

*"As explained in the article, the pulse repetition rate is a function of the current demand of the load and has a maximum value of 30–50 kHz. The reason that the skin effect is significant is that the charge pulses have a fixed duration of 100  $\mu$ s or so, which means that they give rise to a large number of harmonics. These harmonics must be passed by the inductor wire without attenuation to maintain the pulse rise and fall times. Fourier analysis is required to establish the actual skin depth, but this would be a superfluous luxury in this kind of article. The recommendation to use a number of thin parallel-connected wires rather than one thick one ensues from a series of practical experiments on my prototypes". [Ed]*

## SWITCHBOARD

Switchboard allows all PRIVATE READERS of *Elektor Electronics* one FREE advertisement of up to 108 characters, including spaces, commas, numerals, etc. per month.

Write the advertisement, which must relate to electronics, in the coupon on this page; it **MUST INCLUDE** a private telephone number or name and address; post office boxes are not acceptable.

Elektor Electronics (Publishing) can not accept responsibility for any correspondence or transaction as a result of a free advertisement or of any inaccuracy in the text of such an advertisement.

Advertisements will be placed in the order in which they are received.

Elektor Electronics (Publishing) reserve the right to refuse advertisements without giving reasons or without returning them.

**PEN FRIENDS.** I am an electronics engineer and am interested in pen friends on electronics, computers and other allied subjects. **Mohammed Granfar, Damavand Ave, 15 Metri 4th, 8 Metri 6th, No. 10 Post code 17318 Tehran, Iran.**

**WANTED.** Sweep function generator up to 150 kHz to include triangle to ramp wave output. **Phone (0267) 275437.**

**FOR SALE.** New 12 inch black and white video monitor with sound input; takes 1 V composite; £50. **Phone (0704) 214594.**

**FOR SALE.** Tektronix 545 oscilloscope plug-in unit style in good working order. £90. **Phone (0732) 350691** any time.

**FOR SALE.** Elektor Electronics nos 24, 43, 45, 49, June '81-Dec '83 (except April '82); 31 copies £20 plus post. **J. Brown, 74 Humber Ave, South Ockendon, Essex, RM15 5JN.**

**FOR SALE.** Computers IBM XT £490 ono up to AT386 £1290 ono. Many accessories also available.

Phone (08444) 3953 for details.

**WANTED.** Circuit diagram for Telequipment Serviscope. H.L. Earnshaw, 58 Prices Lane, REIGATE RH2 8AY, Telephone (0737) 221480.

**WANTED.** Elektor Electronics  $\mu$ P Frequency meter, Capacitance meter and Inductance meter. **Phone 01-594 7754 after 6 p.m.**

**WANTED.** English manual for NEC PC6001 series; also exchange software for IBM PS/2 on disks.  
**Hamidreza Madjdabadi, No 30 Western 194 St., Tehranpars, TEHRAN 16538, Iran.**

**FOR SALE.** Components owing to giving up hobby. Too numerous to list so ring for details. Offers invited for the whole lot. **Gordon Brown, 72 Bury Hill, WOODBRIDGE IP12 1JD, Telephone (0394) 385652.**

**FOR SALE.** Tektronix 575 curve tracer, Hartley scope 13 A, Creed 444 silent cover (free 444). Best offers. 13A spare manuals £2.50 incl. **R.A. Lord, 22 Elizabeth Crescent, EAST GRINSTEAD RH19 3JA.**

**DESIGN SERVICE.** Low-cost PCB CAD and manufacture, single- or double-sided, to your design. Small or large quantities. **Phone Dave at (0463) 790006.**

**WANTED.** Manual or circuit diagram for Tektronix oscilloscope Type 317. **Phone Howard at (0272) 658191.**

**PEN FRIENDS.** I am interested in pen friends from all over West Germany. **Mohammed Etmnan, Shiraz University, School of Engineering, SHIRAZ, Iran.**

Send this coupon to: **Elektor Electronics  
(Publishing), Down House, Broomhill  
Road, LONDON SW18 4JQ.**

Block capitals please – one character to each box

A blank 10x10 grid for graphing, consisting of 10 columns and 10 rows of squares.

ELEKTOR ELECTRONICS FEBRUARY 1990


Name and address MUST be given here

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

# DARK-ROOM CLOCK

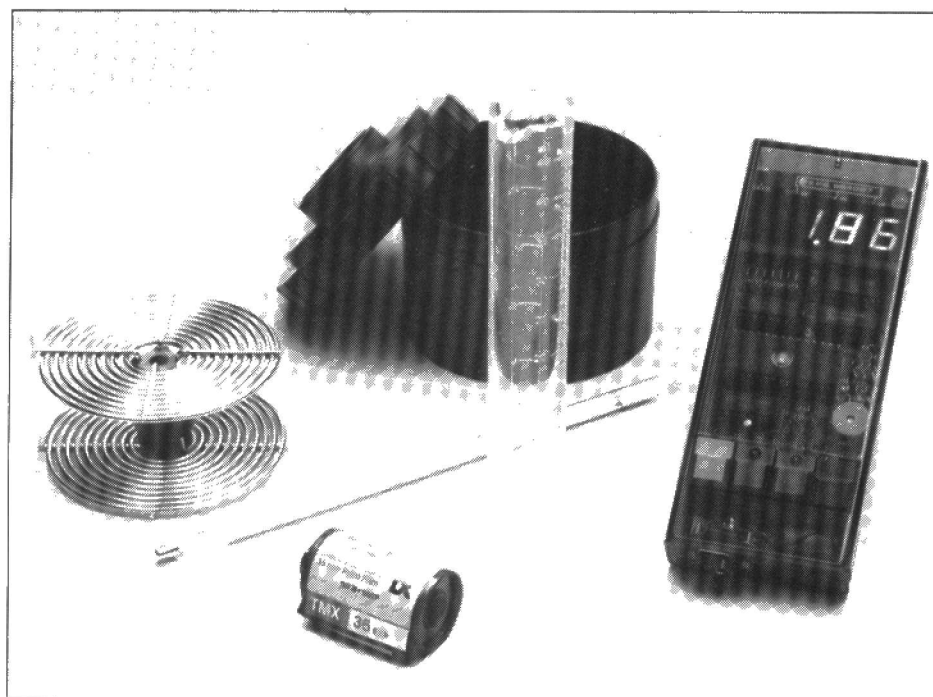

A. Rigby

**Timing is an essential factor in any dark-room. Keeping a constant eye on the clock while the photograph is being developed, however, is a nuisance, and makes it impossible to attend to other activities.**

**The low-cost timer described here can be programmed to give accurately timed audible signals as a reminder to flip the development tank, add the fixative, remove PE paper, and so on.**

The quality of photographic reproductions can be kept constant only if the development tanks are flipped, and baths are changed or stirred in good time. A timing error of a couple of seconds can be tolerated in some cases, but longer delays, caused by other activities in the dark-room, may result in an unusable print.

The present clock offers a number of selectable alarm functions and a maximum time lapse of 30 minutes, which is ample for most dark-room activities. The clock is a compact unit to prevent it taking up too much space in the dark-room.

The block schematic diagram in Fig. 1 shows the general structure of the dark-room clock. The 2 Hz clock generator affords simple selection of a number of differently timed alarm sounds. The 2 Hz clock signal is applied to a binary counter whose (non-used) least-significant output bit counts half-seconds. The 11 other output lines of the counter are connected to the address inputs of an EPROM that converts the 11-bit counter value into control signals for a 4-digit multiplexed LED display. This function requires 7 of the 8

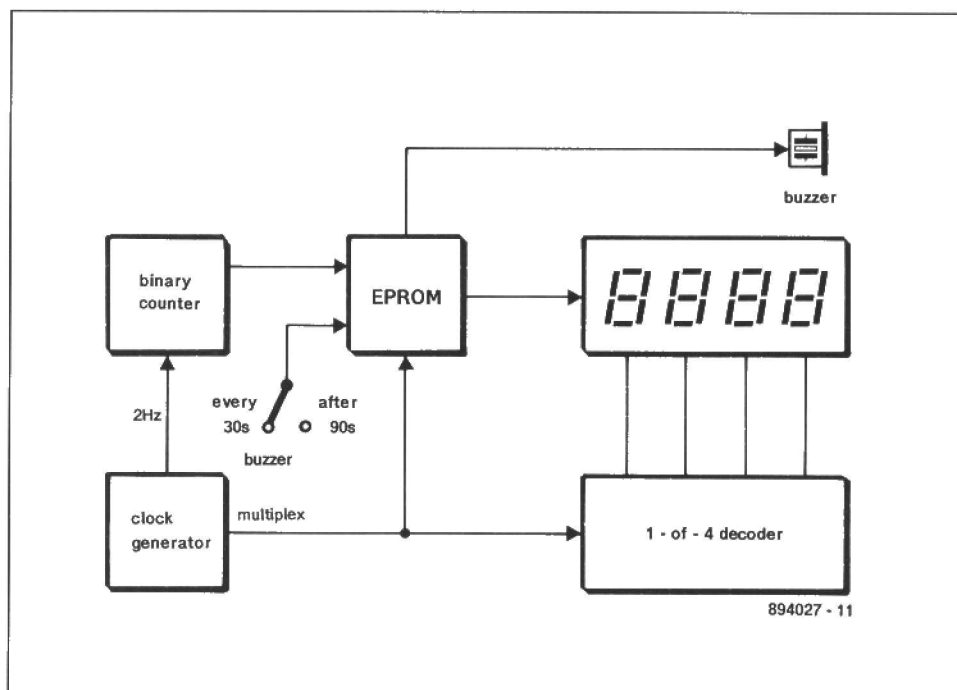


Fig. 1. Block diagram of the dark-room clock.



Bit	D6	D5	D4	D3	D2	D1	D0	HEX
segment	g	f	e	d	c	b	a	
read-out								
none	0	0	0	0	0	0	0	00
0	1	1	1	1	1	1	1	3F
1	0	0	0	0	1	1	0	06
2	1	0	1	1	0	1	1	5B
3	1	0	0	1	1	1	1	4F
4	1	1	0	0	1	1	0	66
5	1	1	0	1	1	0	1	6D
6	1	1	1	1	1	0	1	7D
7	0	0	0	0	1	1	1	07
8	1	1	1	1	1	1	1	7F
9	1	1	0	1	1	1	1	6F

ELEKTOR ELECTRONICS FEBRUARY 1990

buzzer	lapsed time	digit	address (hex)	data (hex)
every 30 s	0 minutes, 0 seconds	seconds (units)	0000	BF
		seconds (tens)	0001	BF
		minutes (units)	0002	BF
		minutes (tens)	0003	80
	0 minutes, 1 second	seconds (units)	0004	06
		seconds (tens)	0005	3F
		minutes (units)	0006	3F
		minutes (tens)	0007	00
	17 minutes, 30 seconds	seconds (units)	1068	BF
		seconds (tens)	1069	CF
		minutes (units)	106A	87
		minutes (tens)	106B	86
	29 minutes, 58 seconds	seconds (units)	1C18	7F
		seconds (tens)	1C19	6D
		minutes (units)	1C1A	6F
		minutes (tens)	1C1B	5B
	29 minutes, 59 seconds	seconds (units)	1C1C	6F
		seconds (tens)	1C1D	6D
		minutes (units)	1C1E	6F
		minutes (tens)	1C1F	5B
after 90 s	0 minutes, 0 seconds	seconds (units)	1C20	FF
		seconds (tens)	1C21	FF
		minutes (units)	1C22	FF
		minutes (tens)	1C23	FF
	1 minute, 30 seconds	seconds (units)	2168	BF
		seconds (tens)	2169	CF
		minutes (units)	216A	86
		minutes (tens)	216B	80
	29 minutes, 59 seconds	seconds (units)	3C1C	6F
		seconds (tens)	3C1D	6D
		minutes (units)	3C1E	6F
		minutes (tens)	3C1F	5B
	248 bytes, not programmed	seconds (units)	3C10	FF
		seconds (tens)	3C11	FF
		minutes (units)	3C12	FF
		minutes (tens)	3C13	FF
A13	A12.....A2	A1, A0	3FFF	FF

Table 1. EPROM organization.

grammed to supply a single alarm after 90 seconds, which is useful for the development of PE (*poly-ethylene*) paper. The development time of PE paper is normally stated as about 60 seconds, but 90 seconds is often found to give better darkening and quality of reproduction.

The time in seconds is applied as an 11-bit binary number to EPROM inputs A2 through A12. This arrangement results in four bytes that hold the segment patterns for the LED displays to be selected every second. Address lines A0 and A1 are driven by two signals that control the multiplexing of the 4 displays. Summarizing the above, the EPROM functions as a circuit that decodes binary time information into a multiplexed 7-segment control signal.

## The circuit

The circuit diagram of Fig. 2 shows that the clock generator is formed by IC<sub>2</sub>, a Type 4060 14-bit counter with on-board oscillator. The oscillator signal is divided by 2<sup>14</sup>, so that output Q13 supplies a 2 Hz signal. Outputs Q6 and Q7 supply the multiplex signals that cause each display to be turned on and off at a rate of 128 times per second.

The 2 Hz signal is fed to the clock input of binary counter IC<sub>1</sub>. This 12-bit counter/divider counts the seconds lapsed since the circuit was started. The use of binary counting in combination with an EPROM allows such a simple seconds counter to be used — the perhaps more conventional alternative would have required at least 8 standard ICs, or two or three specialized ones. The EPROM used in this circuit is available ready-programmed.

The reset circuit of IC<sub>1</sub> has 3 inputs with an OR function provided by D1-D2-D3. The counter is cleared (reset to zero) either when RESET key S<sub>2</sub> is actuated (D<sub>1</sub>), or when the circuit is switched to the stand-by mode by S<sub>1</sub> (D<sub>2</sub>), or when 1800 seconds have lapsed since the last reset (D<sub>3</sub>). The last function is realized with the aid of D4-D7 that reset the counter within a few nanoseconds after it reaches state 1800 (11100001000<sub>2</sub>).

The lapsed time is passed to EPROM IC<sub>4</sub>, whose function has been detailed earlier. The decoded and multiplexed 7-segment signals on datalines D0-D6 are buffered by Darlington array IC<sub>5</sub> before being applied to the cathodes of the LED displays.

The signal on EPROM dataline D7 controls sounder Bz<sub>1</sub> via driver T<sub>5</sub>. The sound of the piezoelectric buzzer is made a little less disagreeable by interrupting it with the aid of T<sub>6</sub>. A wire link, JP<sub>1</sub>, is fitted to provide 3 sounder options:

- position 'C' for two pips of a quarter of a second each;
- position 'D' for a single pip of half a second;
- no wire link for a single pip of one second.



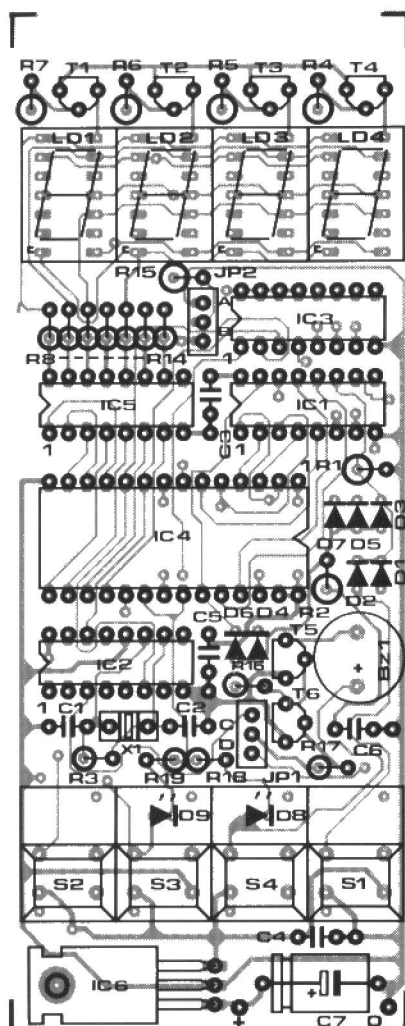


Fig. 3. Printed-circuit board for the dark-room clock. The board is double-sided, but not through-plated.

For reasons of safety, and to keep its overall cost down, the dark-room clock is powered by a mains adapter with a direct, unregulated output voltage of 8–12 V. Regulator IC<sub>6</sub> reduces this voltage to 5 V. A real on/off switch is not provided. Rather, the circuit is switched to stand-by with S<sub>1</sub>. The counter is reset to zero, the displays and LEDs are turned off, and the EPROM is switched to its low-power standby mode. The clock is not re-actuated until S<sub>1</sub> is switched on again.

## Construction

The dark-room clock is built on the double-sided, not through-plated, printed-circuit board shown in Fig. 3. This board is available ready-made.

Figure 4 shows the locations of the holes that must be through-contacted by

## Parts list

### Resistors:

R<sub>1</sub> = 100k  
R<sub>2</sub> = 10k  
R<sub>3</sub> = 10M  
R<sub>4</sub> – R<sub>7</sub>, R<sub>16</sub>, R<sub>17</sub> = 1kΩ  
R<sub>8</sub> – R<sub>15</sub> = 47Ω  
R<sub>18</sub>, R<sub>19</sub> = 470Ω

### Capacitors:

C<sub>1</sub>, C<sub>2</sub> = 220p  
C<sub>3</sub> – C<sub>6</sub> = 100n  
C<sub>7</sub> = 100μ; 25 V

### Semiconductors:

D<sub>1</sub> – D<sub>7</sub> = 1N4148  
D<sub>8</sub>, D<sub>9</sub> = LED, red; 3 mm  
LD<sub>1</sub> – LD<sub>4</sub> = 7751 (common anode)  
T<sub>1</sub> – T<sub>4</sub> = BC557B  
T<sub>5</sub>, T<sub>6</sub> = BC547B  
IC<sub>1</sub> = 4040  
IC<sub>2</sub> = 4060  
IC<sub>3</sub> = 74HCT139  
IC<sub>4</sub> = EPROM 27128. Available ready-programmed under order number ESS 583 (see Readers Services page)  
IC<sub>5</sub> = ULN2004  
IC<sub>6</sub> = 7805

### Miscellaneous:

S<sub>1</sub> = locking SPDT switch with black key cap. ITW Type 61-2010400+  
S<sub>2</sub> = SPDT switch with red key cap. ITW Type 61-1010000+  
S<sub>3</sub>, S<sub>4</sub> = locking SPDT switch with integral LED and black key cap. ITW Type 61-2030401+  
X<sub>1</sub> = quartz crystal 32.768 kHz.  
PCB Type 894027 (see Readers Services page).  
Enclosure: Heddic Type 222\*.

\* ITW Switches • Division of ITW Limited • Norway Road • Hilsea • PORTSMOUTH PO3 5HT. Telephone: (0705) 694971.

\* Emtek Electronic Products Limited • Unit 19a • Industrial Estate • Stanton • BURY ST. EDMUNDS IP31 2AR. Telephone: (0359) 511155.

inserting a short piece of wire, and soldering it at both the component side *and* the track side of the board. This arrangement obviates having to solder the ICs direct on to the board, although this is perfectly permissible in this case. Note that the white overlay print must be removed at the component side before the spots can be soldered properly.

The 3 exclamation marks shown in Fig. 4 indicate PCB design errors that are, fortunately, simple to correct. The holes near pins 22 and 28, towards the 'IC4' mark on the overlay, must be connected to the associated holes that receive the IC pins (or IC socket pins) *at both sides of the PCB*. In the case of pin 22, the missing connection is at the track (EPS) side of the board: a little extra solder tin applied during the mounting of IC<sub>4</sub> will bridge the gap between the spots. The extra connec-

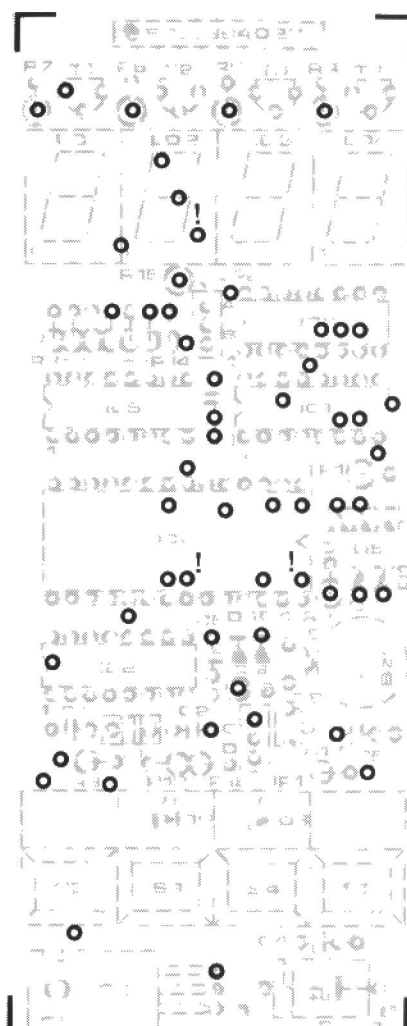


Fig. 4. Showing the locations of the holes that must be through-plated before any components can be fitted.

tion for pin 28 is made at the component side of the board with the aid of a piece of thin wire that connects the holes. Before fitting this wire, remove the white overlay printed on the hole for IC pin 28. Insert the tip of a sharp pencil in the hole to ensure that it remains open when the wire is soldered to the spot.

Make the connection between R<sub>15</sub> and LD<sub>2</sub> with a short length of insulated wire fitted at the track (EPS) side of the board. A track is provided at the component side, but this makes fitting LD<sub>2</sub> rather difficult if the centre pin in the right-hand row of the display is to function as a through contact.

The fitting of the remainder of the components should not present problems.

If the Heddic Type 222 enclosure stated in the Parts List is used, the switches must be raised by mounting them on IC sockets



```

program clock;

var
count : word;
i, j, k, l : integer;
g : file of byte;
displayandsound : array[0..9] of byte;

const
(The display array contains the databyte for each display value)
display : array[0..9] of byte = ($3f,$06,$5b,$4f,$66,$6d,$7d,$7f,$6f);
hexff : byte = $ff;      (used for a blank position in the eeprom)
hex80 : byte = $80;      (used for a blank display segment with sound output)
hex0 : byte = $0;        (used for a blank display segment without sound output)

begin
  assign (g,'clock.dat');           (Open the desired filename)
  rewrite (g);
  for i:=0 to 9 do displayandsound[i]:=display[i]+$80;    (Include sound bit)

  count:=0;                         (Calculate a readout in minutes and seconds)
  for i:=0 to 2 do                   (Reset the displaycount)
    for j:=0 to 9 do                (Maximum count is 29 minutes and 59 seconds)
      for k:=0 to 5 do
        for l:=0 to 9 do
          if count mod 30 = 0        (Check if count is a multiple of 30)
          then
            begin (Calculate the four display bytes including the sound bit)
              write (g,displayandsound[l]);
              write (g,displayandsound[k]);
              write (g,displayandsound[j]);
              (Leading-zero blanking)
              if displayandsound[i]<>displayandsound[0]
                then write (g,displayandsound[i])
                else write (g,hex80);
              count:=count+1;
            end
          else
            begin (Calculate the four displaybytes)
              write (g,display[l]);
              write (g,display[k]);
              write (g,display[j]);
              (Leading-zero suppression)
              if display[i]<>display[0] then write (g,display[i])
              else write (g,hex0);
              count:=count+1;
            end;
          (Fill the remaining part with $FF)
        for i:=1800*4 to $1fff do
          begin
            write (g,hexff);
          end;
          (Calculate a readout in seconds)
          count:=0; (Reset the display count)
          (Maximum count is 1999 seconds)
          for i:=0 to 1 do
            for j:=0 to 9 do
              for k:=0 to 9 do
                for l:=0 to 9 do
                  (Check if count is a multiple of 90 and smaller than 91)
                  if (count mod 90 = 0) and (count<=90)
                  then
                    begin (Calculate the four display bytes including the sound bit)
                      write (g,displayandsound[l]);
                      if count < 10 then write (g,hex80) (Leading-zero blanking)
                      else write (g,displayandsound[k]);
                      if count < 100 then write (g,hex80) (Leading-zero blanking)
                      else write (g,displayandsound[j]);
                      if count < 1000 then write (g,hex80) (Leading-zero blanking)
                      else write (g,displayandsound[i]);
                      count:=count+1;
                    end
                  else
                    begin (Calculate the four display bytes)
                      write (g,display[l]);
                      if count < 10 then write (g,hex0) (Leading-zero blanking)
                      else write (g,display[k]);
                      if count < 100 then write (g,hex0) (Leading-zero blanking)
                      else write (g,display[j]);
                      if count < 1000 then write (g,hex0) (Leading-zero blanking)
                      else write (g,display[i]);
                      count:=count+1;
                    end;
                  (Fill the remaining part with $FF)
                for i:=$2000+2000*4 to $3fff do
                  begin
                    write (g,hexff);
                  end;
                end;
              close (g); (Close the file)
            end.
            894027-13

```

Fig. 5. Listing of the Turbo-Pascal program used to compile the content of the EPROM. The IF COUNT statements allow you to change the timing intervals to individual requirement. Like the EPROM content, the program is divided in two parts: the first provides the data for the minutes and seconds read-out, and the second the data for the seconds read-out (0–1800 s). These blocks may be interchanged. EPROM data is written to file CLOCK.DAT.

(cut off the non-used pins of 14-way low-profile types). Also note that the LEDs in the key caps are best removed and replaced by types with long terminals that can be soldered direct to the PCB. Use a drill or a small file to modify the IC socket if a part of it is in the way of the LED terminals.

The switches are 'Digitast'-like SPDT (single-pole, double-throw) models with an integral LED. With the exception of S<sub>2</sub>, they remain locked in both positions. If difficult to obtain locally, the switches may, of course, be replaced by suitable equivalents with the same electrical function, mounted on to the front panel of the enclosure, and connected to the circuit by short wires.





**ORDER  
YOUR COPY  
OF THE NEW  
MAPLIN CATALOGUE  
ON SALE NOW**

Pick up a copy from any W.H. Smith for just £2.25 or post this coupon now to receive your copy for just £2.25 + 50p p & p. If you live outside the U.K. send £4 or 17 International Reply Coupons. I enclose £2.75.

Name.....  
Address.....

Send to Maplin Electronics, P.O. Box 3, Rayleigh, Essex SS6 8LR.  
Post Code.....

**AVAILABLE FROM 10th NOVEMBER 1989 IN ALL W.H. SMITH STORES**

E 90



**OVER 580 PAGES WITH HUNDREDS OF NEW PRODUCTS AT SUPER LOW PRICES  
THE NEW MAPLIN CATALOGUE – WORLDS APART!  
1990 BUYER'S GUIDE TO ELECTRONIC COMPONENTS SEND FOR YOUR COPY TODAY**